


Introduction to CMOS VLSI Design

Lecture 13: SRAM


Outline

- ❑ Memory Arrays
- ❑ SRAM Architecture
 - SRAM Cell
 - Decoders
 - Column Circuitry
 - Multiple Ports
- ❑ Serial Access Memories

Memory Arrays

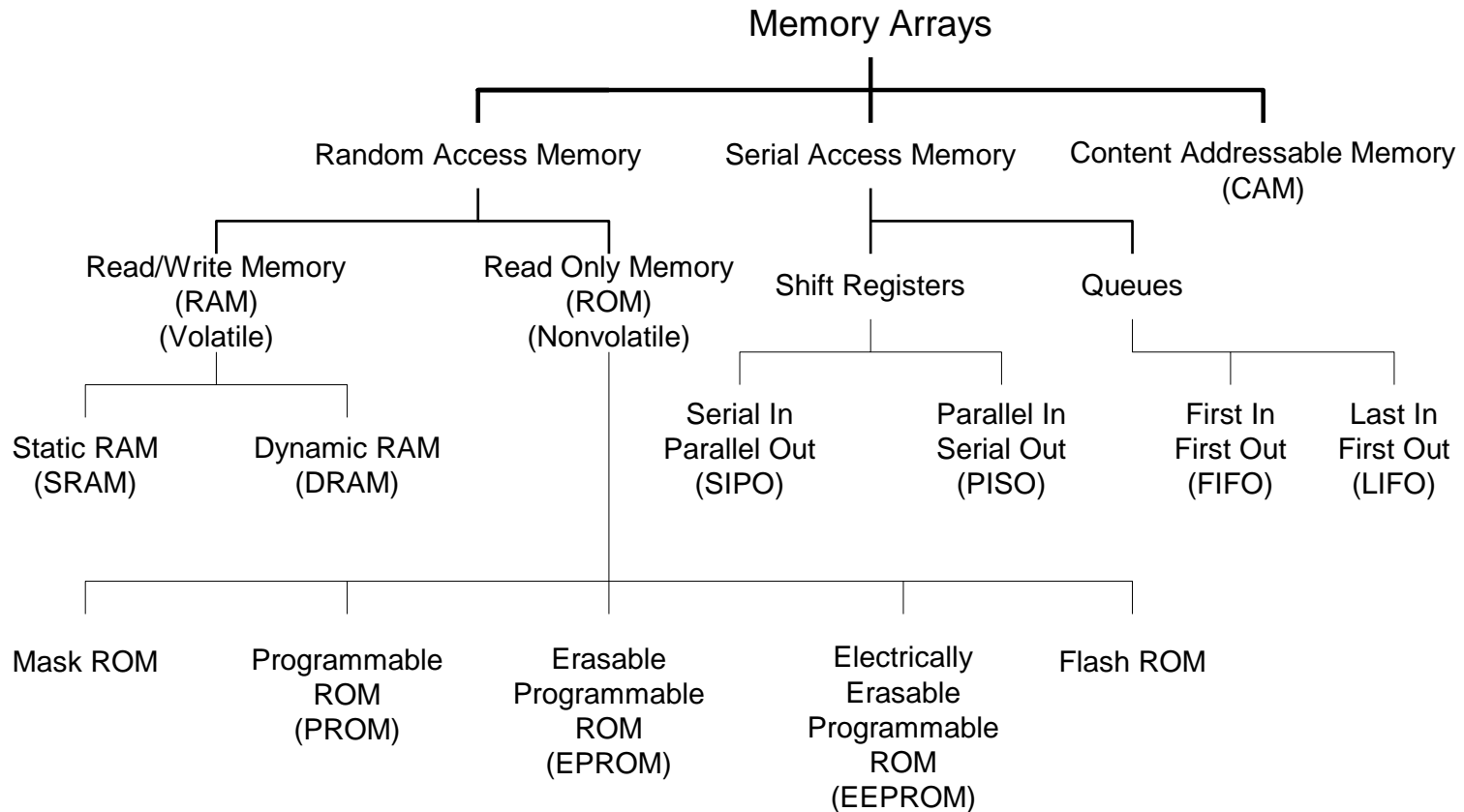

Levels of the Memory Hierarchy

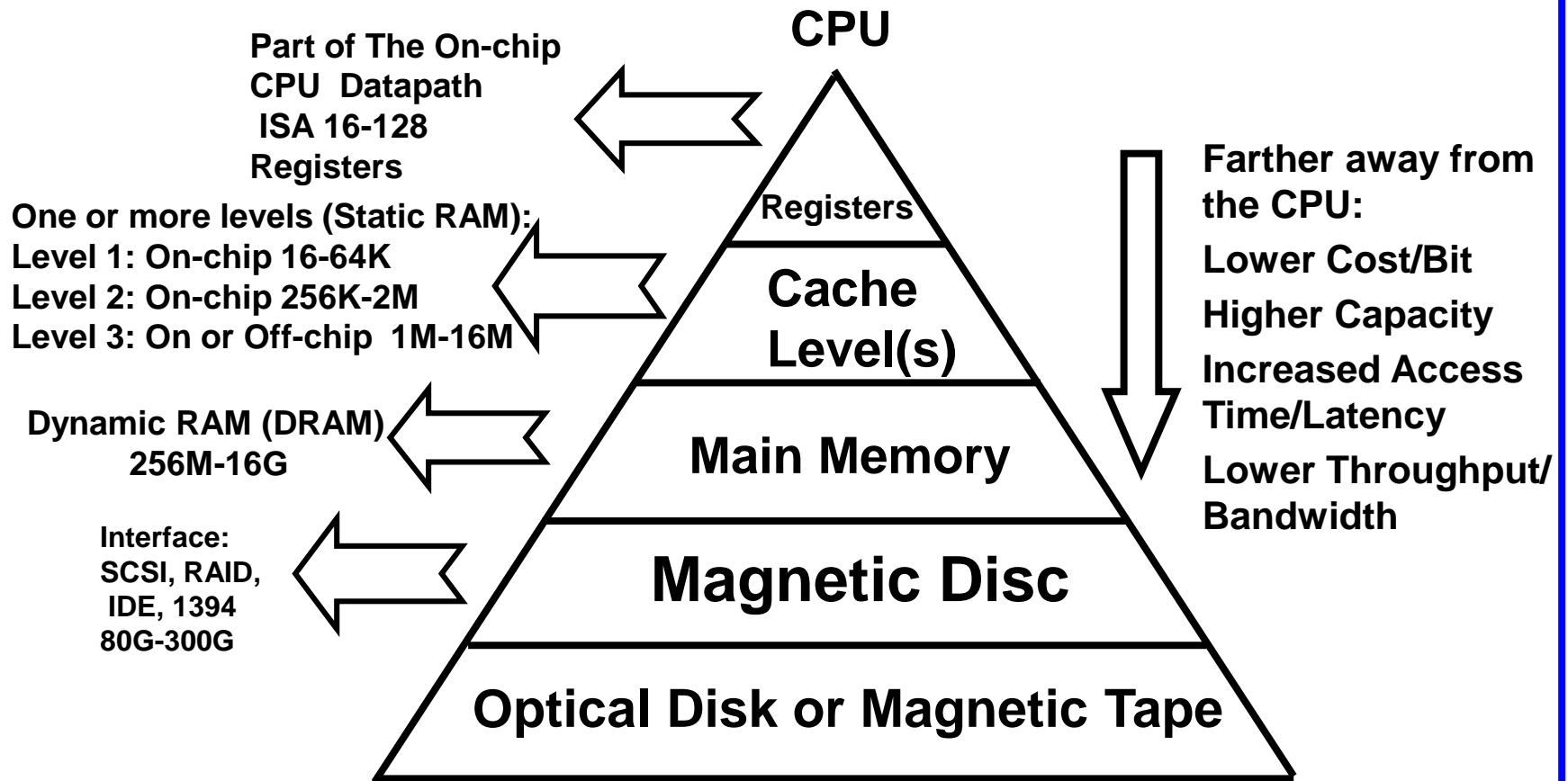

Memory Hierarchy Comparisons

Capacity
Access Time
Cost


CPU Registers
100s Bytes
<10s ns

Cache
K Bytes
10-100 ns
1-0.1 cents/bit


Main Memory
M Bytes
200ns- 500ns
\$.0001-.00001 cents /bit

Disk
G Bytes, 10 ms
(10,000,000 ns)
-5 -6
10 - 10 cents/bit

Tape
infinite
sec-min
10⁻⁸

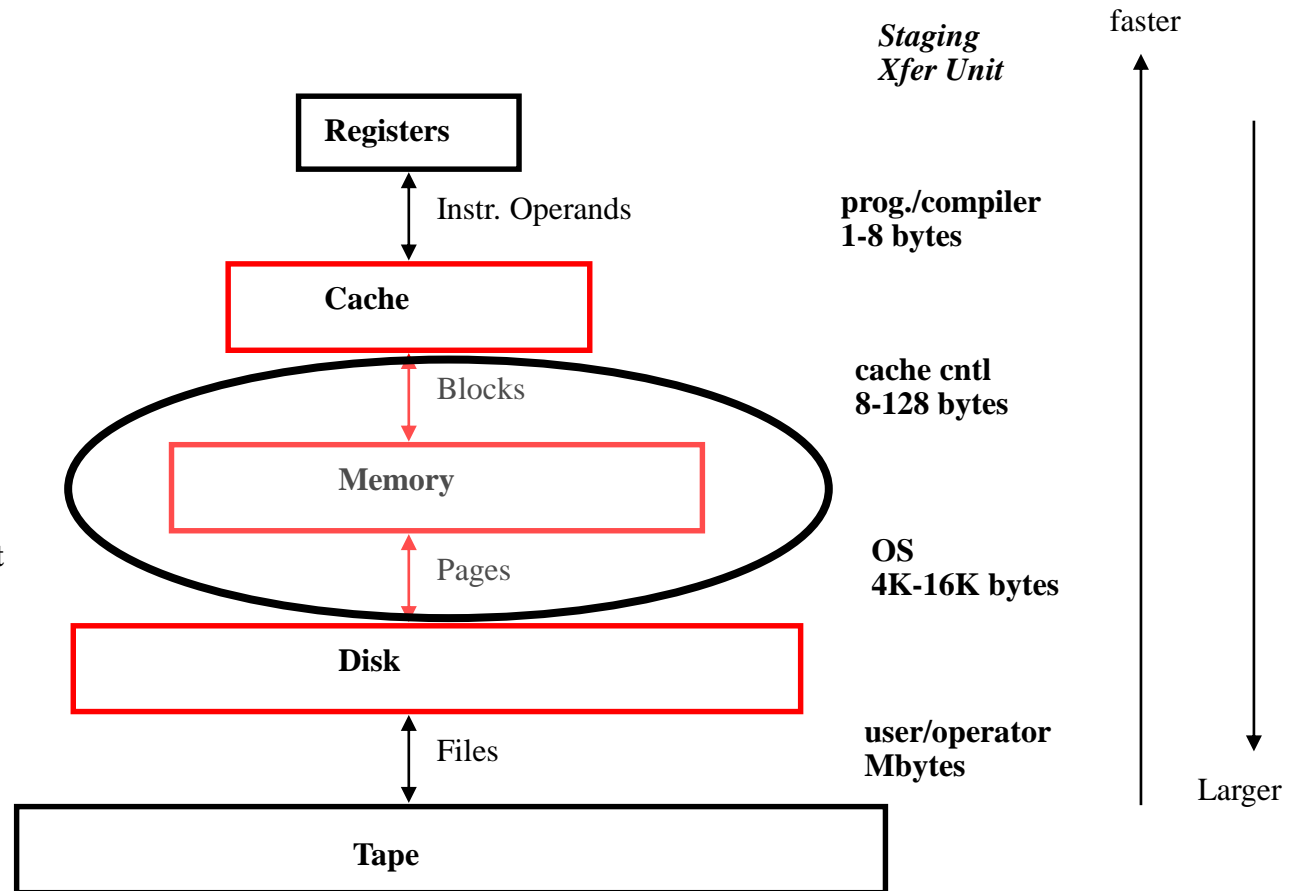


Connecting Memory

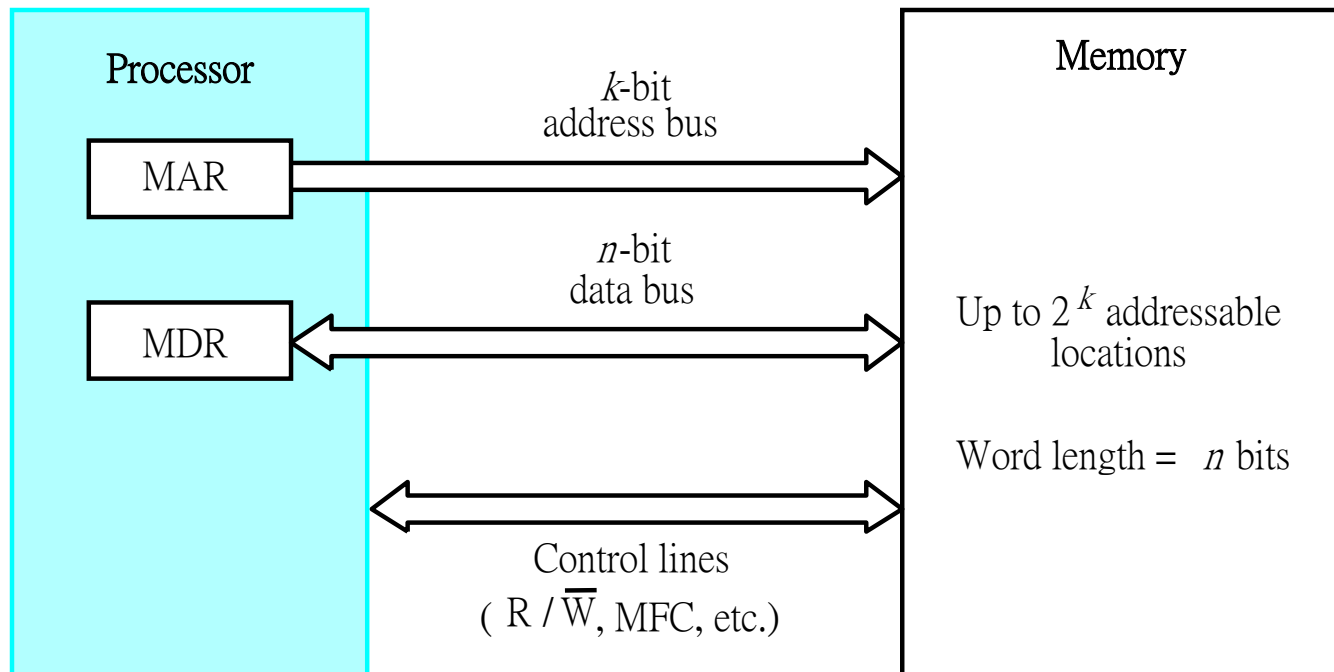


Array Architecture

 - ❑ 2^n words of 2^m bits each
- ❑ If $n \gg m$, fold by 2^k into fewer rows of more columns



- ❑ Good regularity – easy to design
- ❑ Very high density if good cells are used

Hierarchical Memory Architecture

 

Advantages:

1. Shorter wires within blocks
2. Block address activates only 1 block => power savings


Array Organization Design Issues

- ❑ aspect ratio should be relative square
 - Row / Column organization (matrix)
 - $R = \log_2(N_{\text{rows}})$; $C = \log_2(N_{\text{columns}})$
 - $R + C = N$ ($N_{\text{address_bits}}$)
- ❑ number of rows should be power of 2
 - number of bits in a row need not be...
- ❑ sense amplifiers to speed voltage swing
- ❑ 1 \rightarrow 2^R row decoder
- ❑ 1 \rightarrow 2^C column decoder
 - M column decoders (M bits, one per bit)
 - M = output word width

SRAM Read Timing (typical)


- ❑ t_{AA} (access time for address): time for stable output after a change in address.
- ❑ t_{ACS} (access time for chip select): time for stable output after CS is asserted.
- ❑ t_{OE} (output enable time): time for low impedance when OE and CS are both asserted.
- ❑ t_{OZ} (output-disable time): time to high-impedance state when OE or CS are negated.
- ❑ t_{OH} (output-hold time): time data remains valid after a change to the address inputs.

SRAM Read Timing (typical)

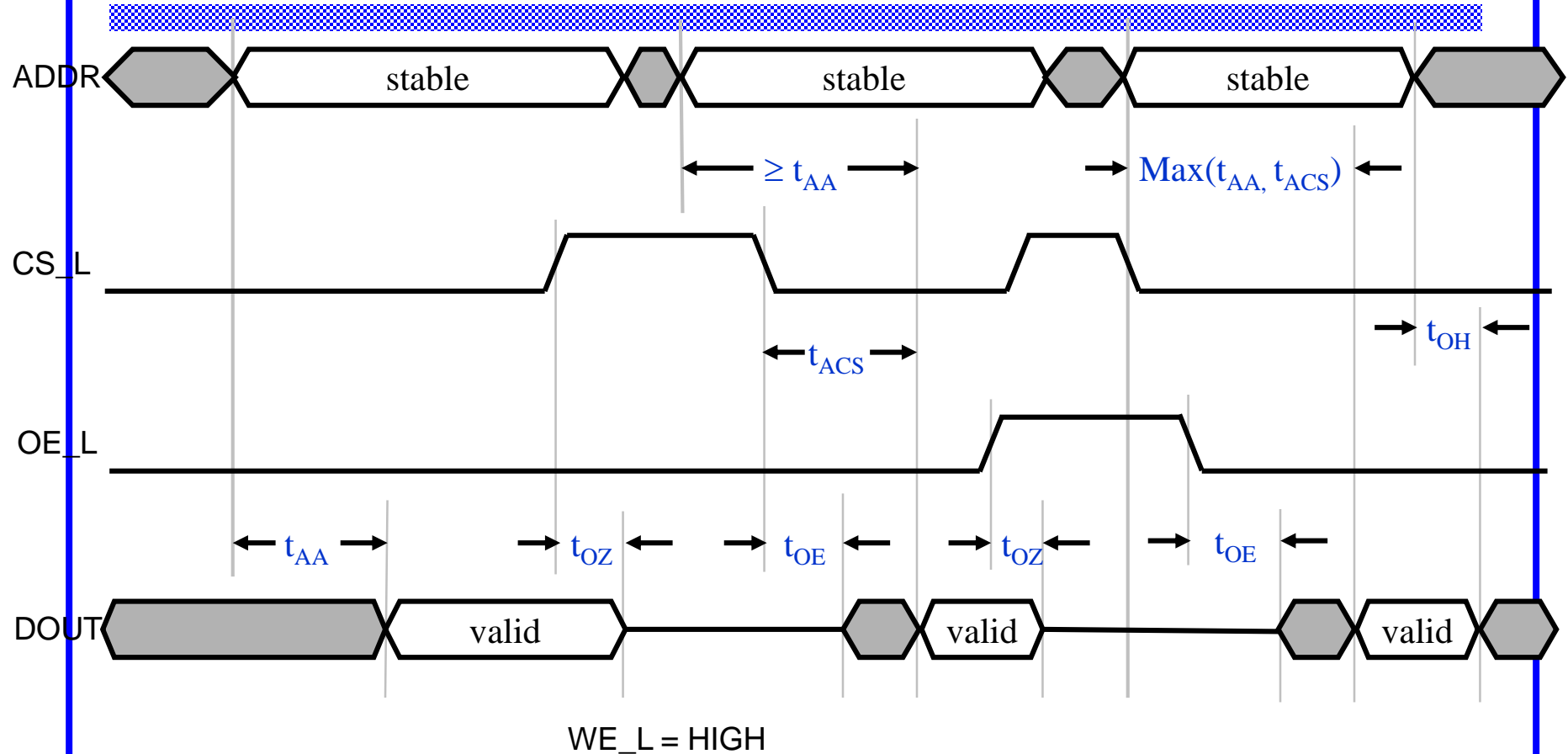


SRAM write cycle timing


~WE controlled

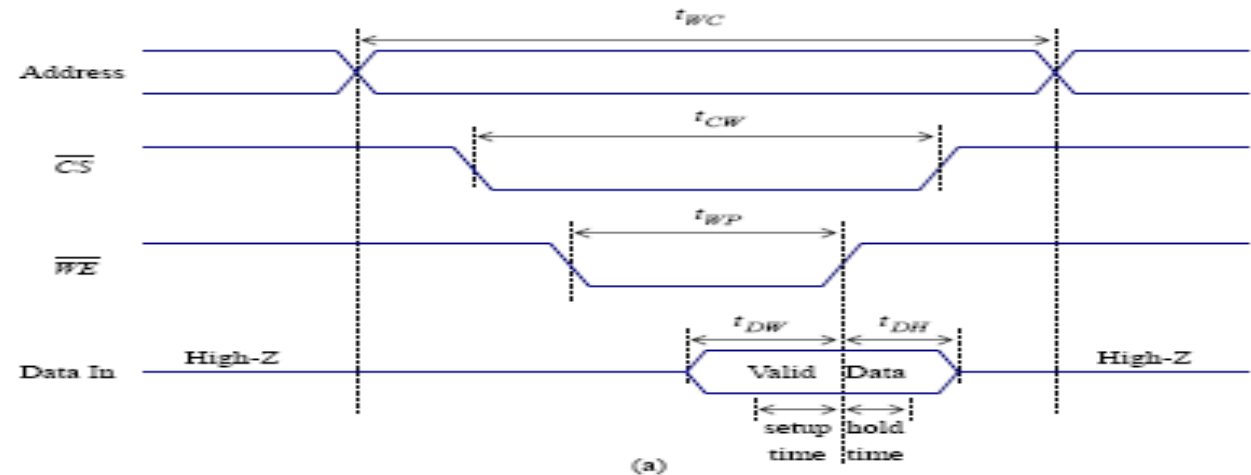


~CS controlled

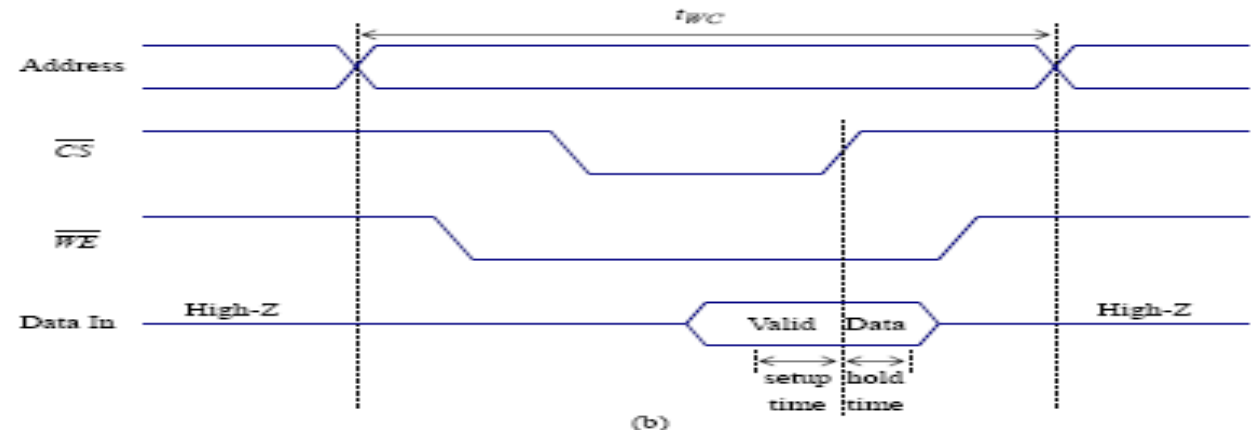

SRAM Architecture and Read Timings

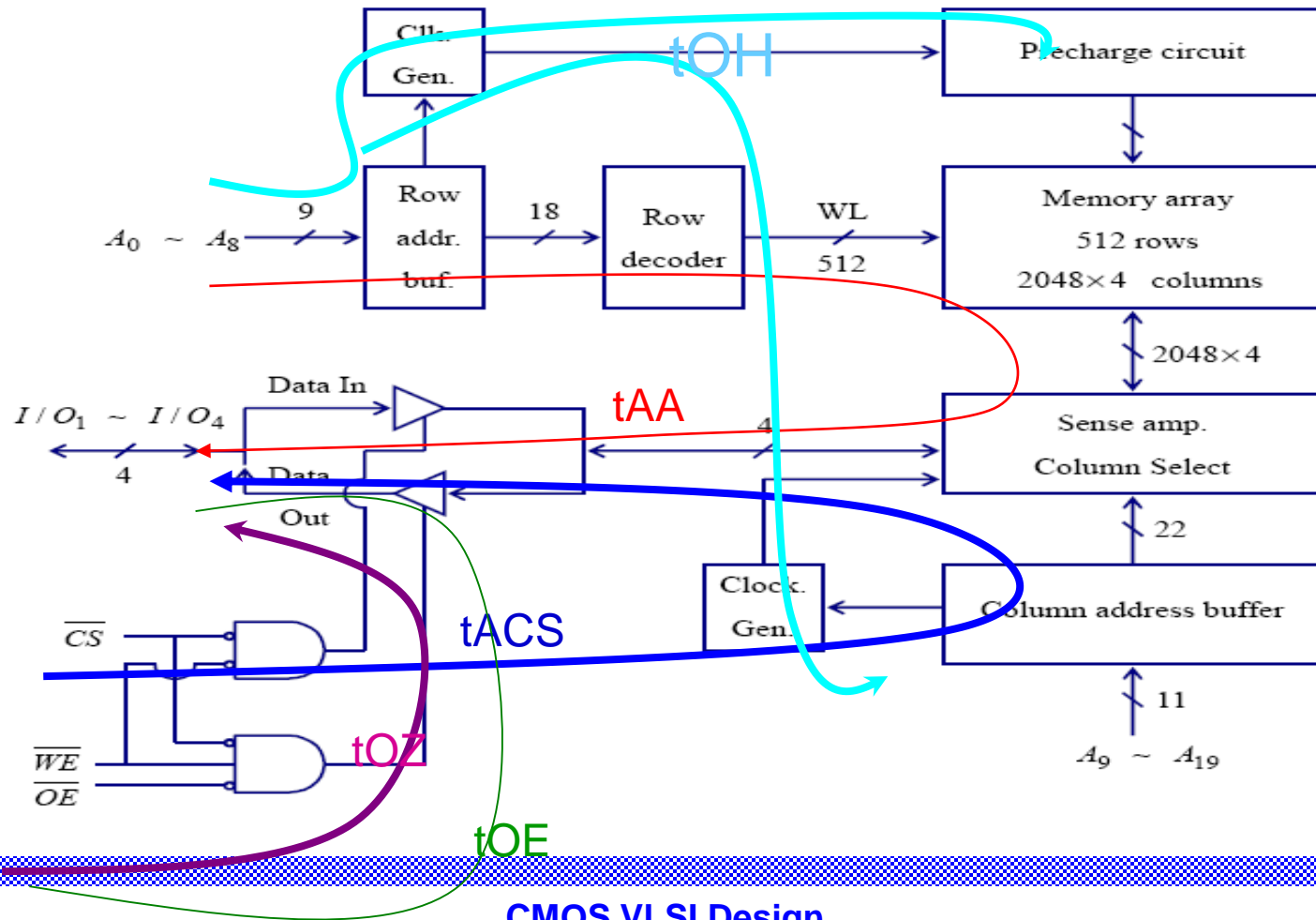

SRAM Architecture and Write Timings


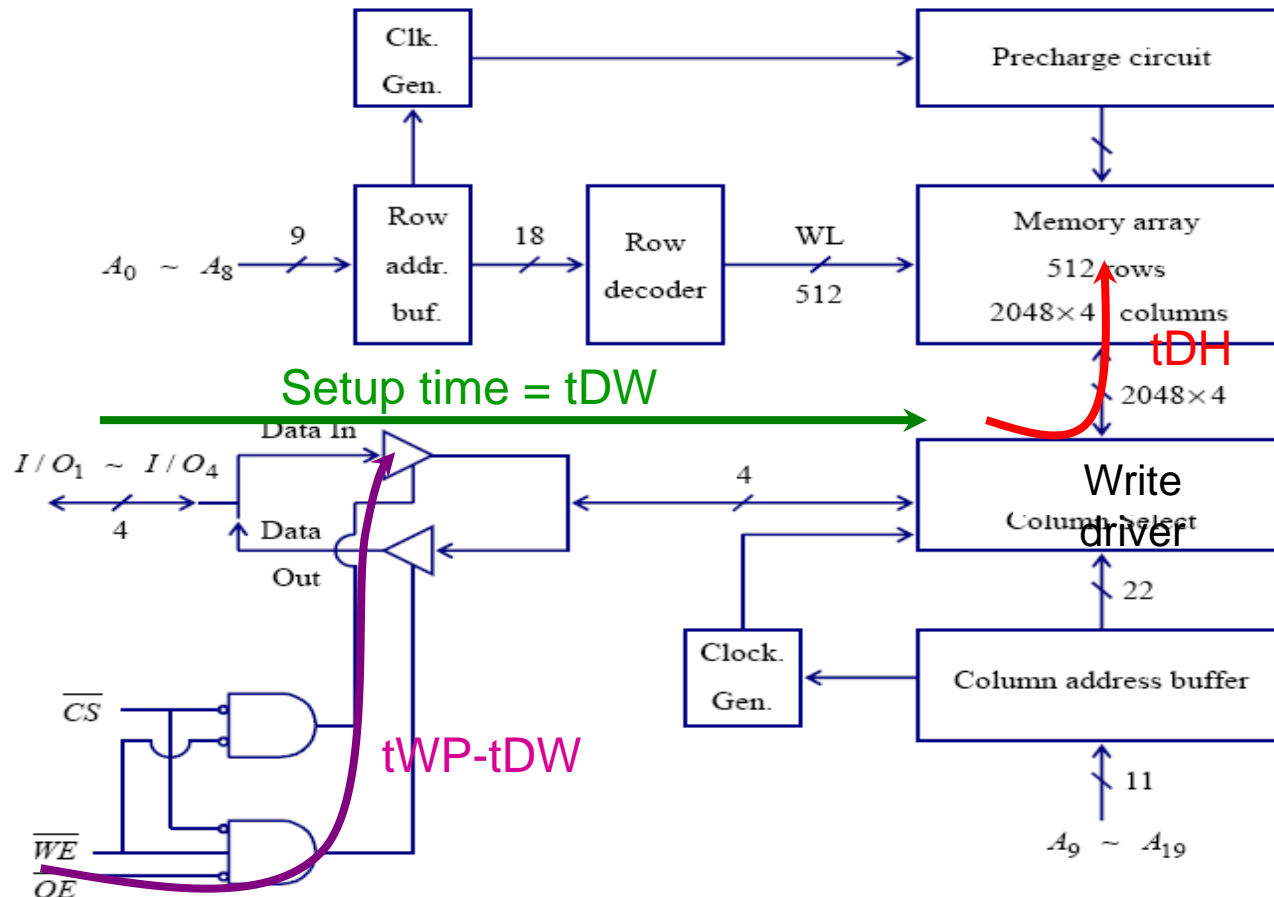


nMOS I-V Summary

$$I_{ds} = \begin{cases} 0 & V_{gs} < V_t & \text{cutoff} \\ \beta \left(V_{gs} - V_t - \frac{V_{ds}}{2} \right) V_{ds} & V_{ds} < V_{dsat} & \text{linear} \\ \frac{\beta}{2} (V_{gs} - V_t)^2 & V_{ds} > V_{dsat} & \text{saturation} \end{cases}$$


12T SRAM Cell

  - ❑ Basic building block: SRAM Cell
 - Holds one bit of information, like a latch
 - Must be read and written
- ❑ 12-transistor (12T) SRAM cell
 - Use a simple latch connected to bitline
 - $46 \times 75 \lambda$ unit cell




6T SRAM Cell

 - ❑ Cell size accounts for most of array size
 - Reduce cell size at expense of complexity
- ❑ 6T SRAM Cell
 - Used in most commercial chips
 - Data stored in cross-coupled inverters
- ❑ Read:
 - Precharge bit, bit_b
 - Raise wordline
- ❑ Write:
 - Drive data onto bit, bit_b
 - Raise wordline





6T SRAM Cell

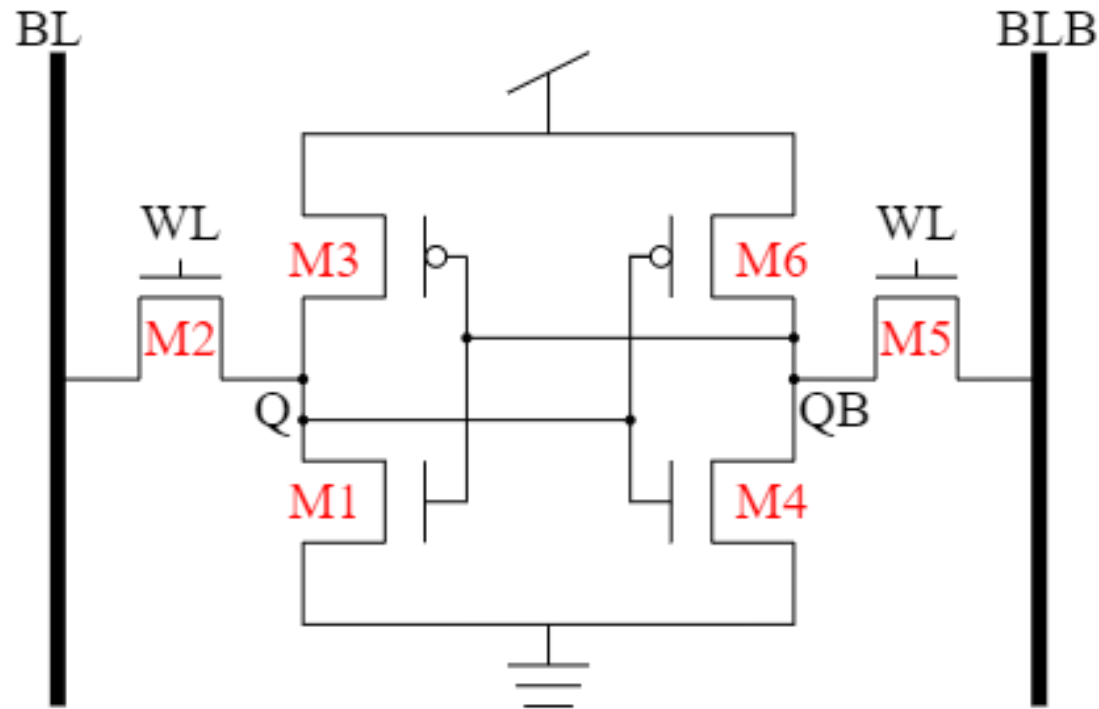



SRAM Read

  - ❑ Precharge both bitlines high
- ❑ Then turn on wordline
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0$, $A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip





SRAM Read

  - ❑ Precharge both bitlines high
- ❑ Then turn on wordline
- ❑ One of the two bitlines will be pulled down by the cell
- ❑ Ex: $A = 0$, $A_b = 1$
 - bit discharges, bit_b stays high
 - But A bumps up slightly
- ❑ *Read stability*
 - A must not flip
 - $N1 \gg N2$




SRAM Read

 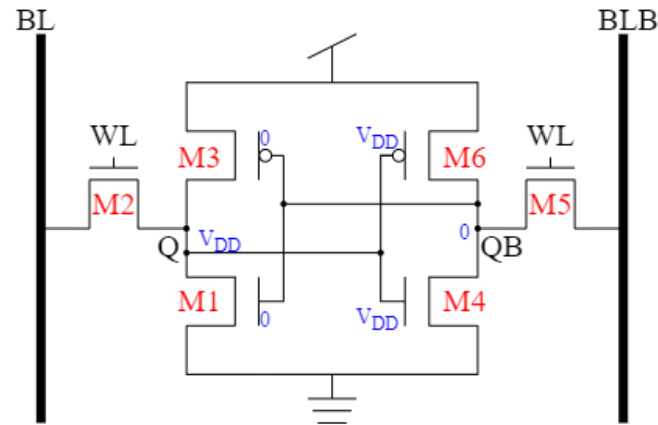


Left Side:
Nothing Changes

 Right Side:
“nMOS” inverter –
QB voltage rises



SRAM Read

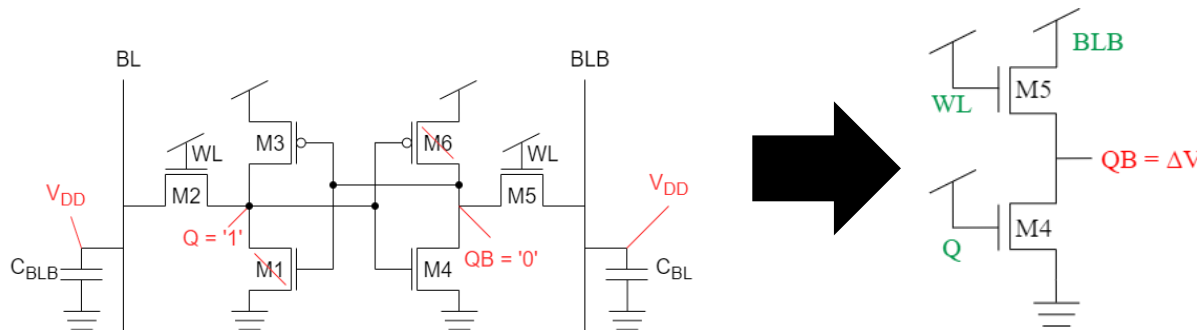



Cell Ratio:

$$CR \equiv \frac{W_4/L_4}{W_5/L_5}$$

$$k_{M5} \left[(V_{DD} - \Delta V - V_{T,n}) V_{DSat,n} - \frac{V_{DSat,n}^2}{2} \right] = k_{M4} \left[(V_{DD} - V_{T,n}) \Delta V - \frac{\Delta V^2}{2} \right]$$

$$\Delta V = \frac{V_{DSat,n} + CR(V_{DD} - V_{T,n}) - \sqrt{V_{DSat,n}^2(1 + CR) + CR^2(V_{DD} - V_{T,n})^2}}{CR}$$


SRAM Read

 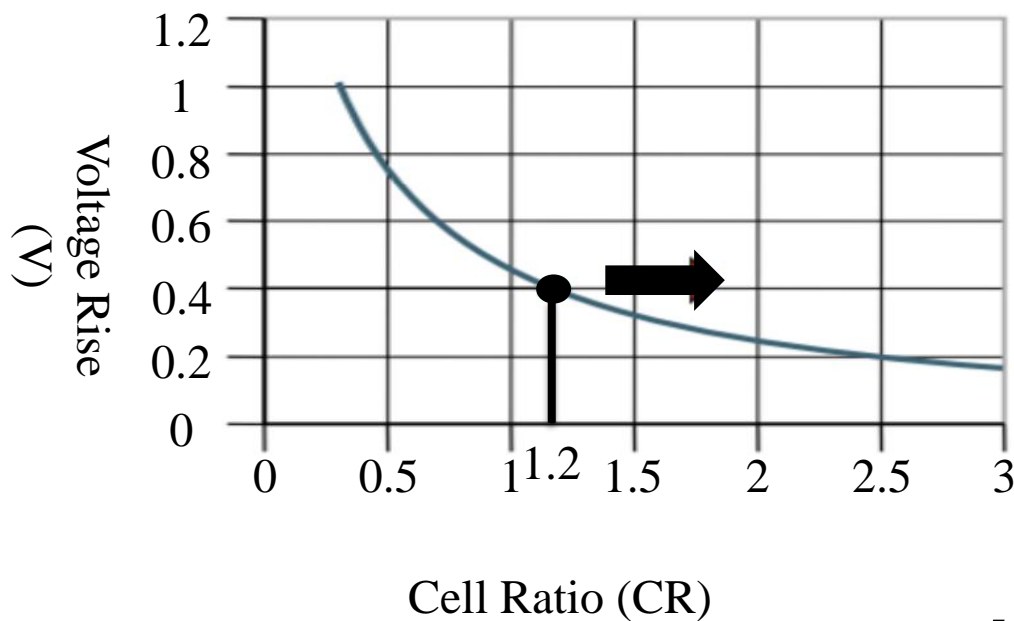

$$CR \equiv \frac{W_4/L_4}{W_5/L_5}$$



SRAM Write

 - ❑ Drive one bitline high, the other low
- ❑ Then turn on wordline
- ❑ Bitlines overpower cell with new value
- ❑ Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- ❑ *Writability*
 - Must overpower feedback inverter





SRAM Write

  - ❑ Drive one bitline high, the other low
- ❑ Then turn on wordline
- ❑ Bitlines overpower cell with new value
- ❑ Ex: $A = 0$, $A_b = 1$, $\text{bit} = 1$, $\text{bit}_b = 0$
 - Force A_b low, then A rises high
- ❑ *Writability*
 - Must overpower feedback inverter
 - $N2 \gg P1$



SRAM Write

  


Left Side:


Same as doing read –
designed so $\Delta V < V_M$

Right Side:

Pseudo nMOS
inverter!

 



SRAM Write

 

$$k_{M6} \left[(V_{DD} - |V_{T,p}|) V_{DSat,p} - \frac{V_{DSat,p}^2}{2} \right] = k_{M5} \left[(V_{DD} - V_{T,n}) \Delta V_{QB} - \frac{\Delta V_{QB}^2}{2} \right]$$

$$V_{QB} = V_{DD} - V_{T,n} - \sqrt{(V_{DD} - V_{T,n})^2 - 2 \frac{\mu_p}{\mu_n} PR \left[(V_{DD} - |V_{T,p}|) V_{DSat,p} - \frac{V_{DSat,p}^2}{2} \right]}$$


SRAM Write

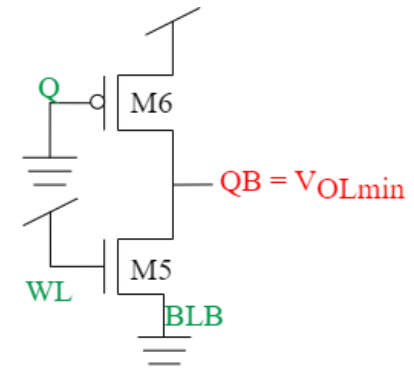 

$$PR \equiv \frac{W_6/L_6}{W_5/L_5}$$

SRAM Sizing

Read Constraint

 

$$CR \equiv \frac{W_1/L_1}{W_2/L_2} = \frac{W_4/L_4}{W_5/L_5} = \frac{PDN}{access}$$




$$K_{PDN} > K_{access}$$



$$K_{PDN} > K_{access} > K_{PUN}$$

Write Constraint

 


$$PR \equiv \frac{W_3/L_3}{W_2/L_2} = \frac{W_6/L_6}{W_5/L_5} = \frac{PUN}{access}$$

$$K_{access} > K_{PUN}$$



Simplified CMOS SRAM Analysis (Read)

 

Simplified CMOS SRAM Analysis (Read)

\bar{Q} node voltage can not over the transition voltage of M3 and M4 inverter i.e. $V_{\bar{Q}} < \text{transition voltage (assume } V_{DD} / 2 \text{) or } < V_{TN0}$. So, the marginal condition

is:

$$\frac{K_5}{2} (V_{DD} - V_{\bar{Q}} - V_{TN} |_{|V_{BS}| = V_{\bar{Q}}})^2 = K_1 \left[(V_{DD} - V_{TN0}) V_{\bar{Q}} - \frac{V_{\bar{Q}}^2}{2} \right]$$


$$\text{,where } V_{\bar{Q}} < V_t \text{ or } V_{\bar{Q}} < V_{TN0}$$

Assume that $V_{DD} = 3.3V$ and $V_{TN0} = 0.59V$


$$V_{TN} |_{V_{BS} = 0.5V_{DD}} = 0.93V \text{ and } V_{TN} |_{V_{BS} = V_{TN0}} = 0.75V$$

We obtain $K_5 < 12K_1$ or $K_5 < 0.8K_1$, so we select $W_5 < 0.8W_1$

Simplified CMOS SRAM Analysis (Write)

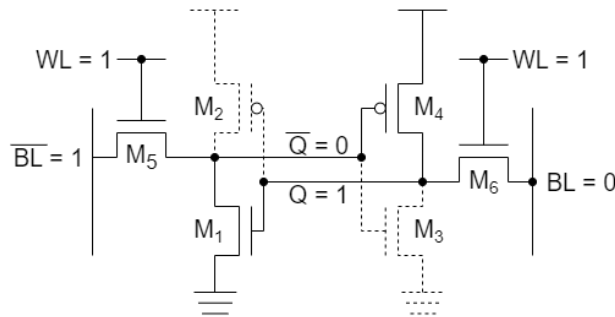

(a)

 

(b)

$$K_4 \left[(V_{DD} - |V_{TP0}|)(V_{DD} - V_Q) - \frac{(V_{DD} - V_Q)^2}{2} \right] = K_6 \left[(V_{DD} - V_{TN0})V_Q - \frac{V_Q^2}{2} \right]$$

$V_Q < V_t$



$$\frac{K_5}{2} (V_{DD} - V_{TN0} - V_{TN} |_{V_{BS}=V_{TN0}})^2 = K_1 \left[(V_{DD} - V_{TN0})V_{\bar{Q}} - \frac{V_{\bar{Q}}^2}{2} \right]$$

$$V_{DD} = 3.3V, V_{TN0} = 0.59V, V_{TP0} = -0.72V, V_Q < V_t, K_4 \leq 0.73K_6$$

$$\mu_p C_{ox} \left(\frac{W}{L} \right)_4 \leq 0.73 \mu_n C_{ox} \left(\frac{W}{L} \right)_6 \quad \left(\frac{W}{L} \right)_4 \leq 0.73 \frac{\mu_n}{\mu_p} \left(\frac{W}{L} \right)_6 \quad or \quad \left(\frac{W}{L} \right)_4 \leq 1.8 \left(\frac{W}{L} \right)_6$$



6T-SRAM — Layout

  - ❑ Extremely dense
- ❑ Modern processes can fit a 6T SRAM cell in $\sim 1.3\mu\text{m}^2$



SRAM Layout

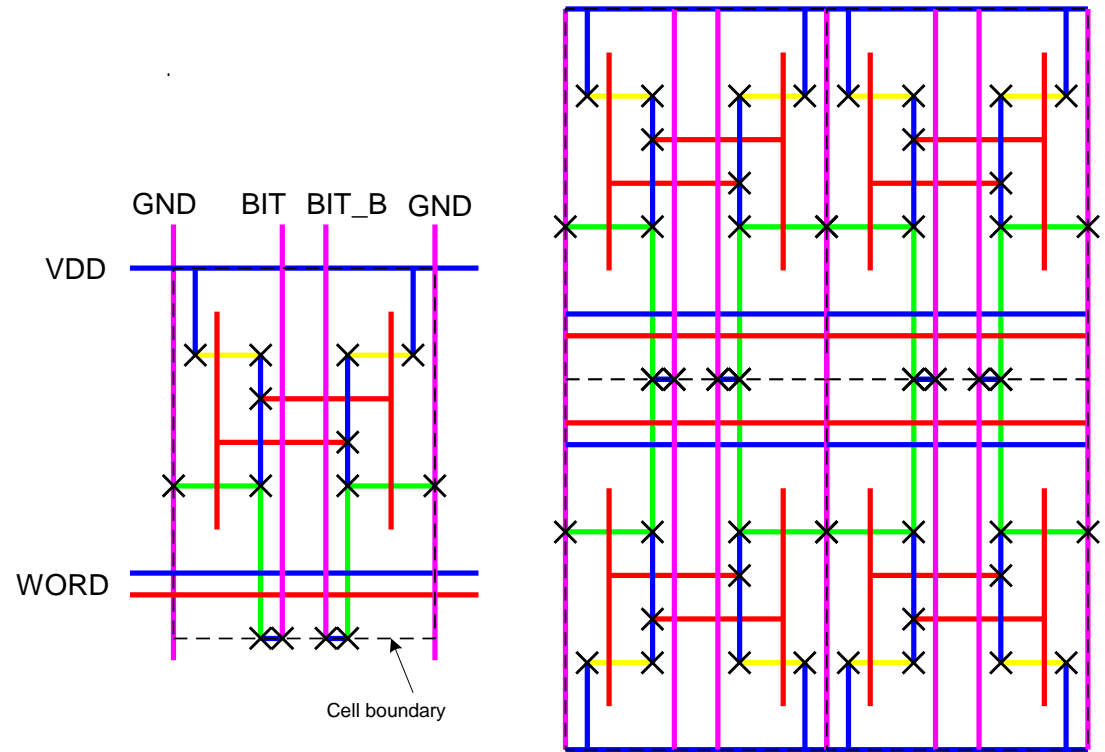 
- ❑ Cell size is critical: $26 \times 45 \lambda$ (even smaller in industry)
- ❑ Tile cells sharing V_{DD} , GND, bitline contacts




Decoders

- ❑ $n:2^n$ decoder consists of 2^n n -input AND gates
 - One needed for each row of memory
 - Build AND from NAND or NOR gates

Static CMOS

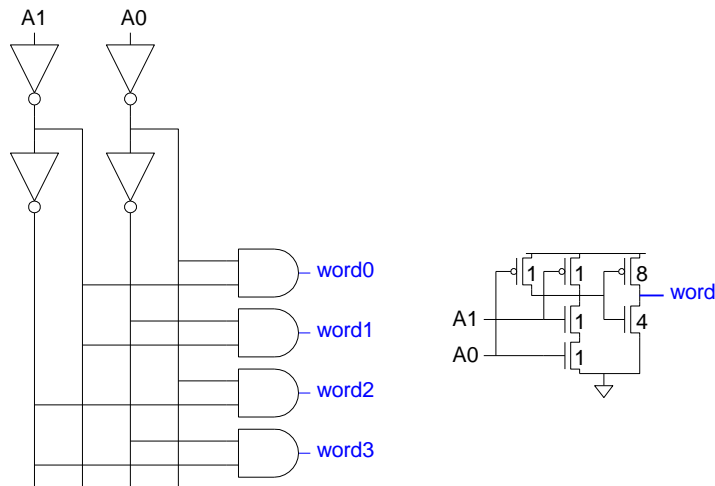

Pseudo-nMOS

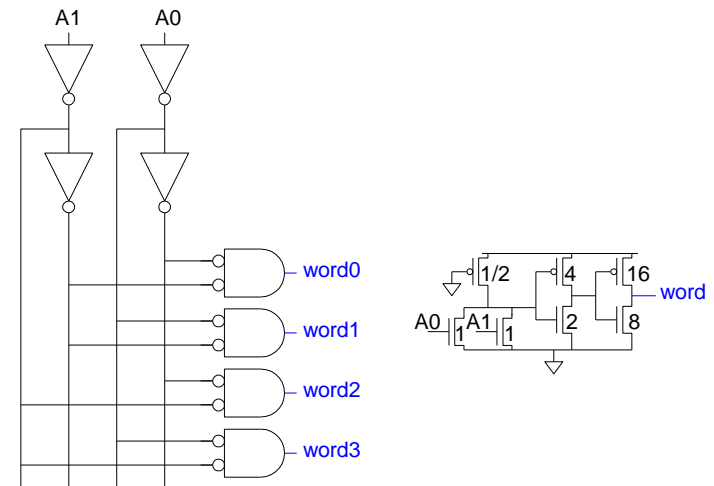


ROW Decoder

- Standard Decoder Design
 - Each output row is driven by an AND gate has a unique combination of address inputs
 - For example, an 8-bit row address has 256 8-input AND gates
$$WL0 = \overline{A7} \overline{A6} \overline{A5} \overline{A4} \overline{A3} \overline{A2} \overline{A1} \overline{A0}$$
$$WL255 = A7 A6 A5 A4 A3 A2 A1 A0$$
- NOR decoder
 - DeMorgan will provide a nor decoder
$$WL0 = \overline{(A7 + A6 + A5 + A4 + A3 + A2 + A1 + A0)}$$


How Should We Build It

 - Let's build a row decoder for a 256x256 SRAM Array
 - We need 256 8-input AND gates
 - Each gate drives 256 bit cells
- Various options:




$$LE = \frac{10}{3} \cdot 1 = \frac{10}{3}$$

$$P = 8 + 1 = 9$$

 


$$LE = \frac{5}{3} \cdot 2 = \frac{10}{3}$$

$$P = 4 + 2 = 6$$

 

$$LE = \frac{4}{3} \cdot \frac{5}{3} \cdot \frac{4}{3} = \frac{80}{27}$$

$$P = 2 + 2 + 2 + 1 = 7$$

 

$$LE = \left(\frac{4}{3}\right)^3 = 2.37$$

$$P = 2 \times 3 + 1 \times 3 = 9$$

- Which one is best?

Discussion


- What is the Branching Effort?
 - Let's take a look at the Boolean expression :

$$WL0 = \overline{A7} \overline{A6} \overline{A5} \overline{A4} \overline{A3} \overline{A2} \overline{A1} \overline{A0}$$

$$WL255 = A7 A6 A5 A4 A3 A2 A1 A0$$

- Each address driver drives 128 8-input AND gates

Discussion

 

Number of Stages

- The path effort:
 $PE = LE * B * F = LE * 128 * (256/4) = LE * 2^{13}$
- The best case logical effort: $LE = 1$
- The minimum number of stages for the optimal delay: $N = LE * \log_{3.6} 2^{13} = 7$

Which Implementation

- The one with the minimum Logical Effort:


$$PE = 2.37 * 2^{13} = 19.418K$$

$$N = \log_{3.6} 19.418K = 7.7$$

- So now we can calculate the actual path effort
- We could add another inverter to get closer to the optimal number of stages

Predecoding Concept

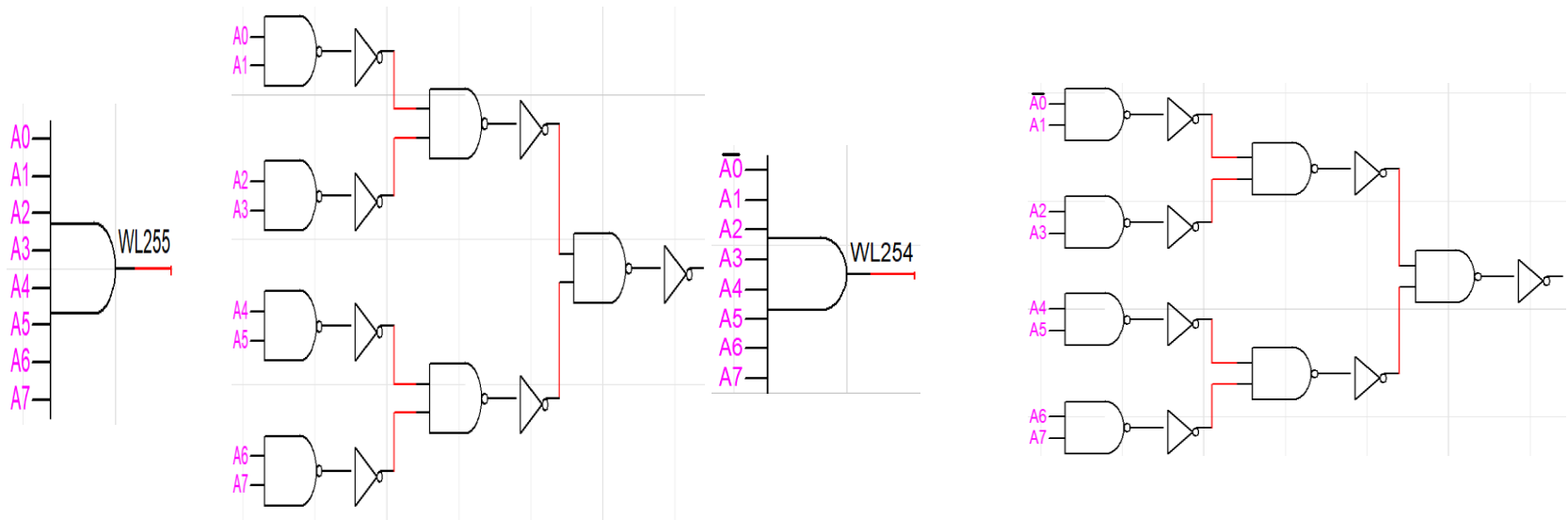- Let's look at two decoder paths: WL254 WL255



- We see there are many shared gate .
So why not share them?

Predecoding Method

- Look at the final Boolean expression with combinations of groups of inputs.
- We actually create a small decoder by grouping together a few inputs.
- Then we just AND the outputs of all predecoder
For example Two 4:16 predecoders

$$D = \text{dec}(A_0, A_1, A_2, A_3) \text{ , } E = \text{dec}(A_4, A_5, A_6, A_7)$$

$$WL_0 = D_0 * E_0 ; WL_{255} = D_{15} * E_{15} ; WL_{254} = D_{14} * E_{15} ;$$

Predecoding Example


- Look at the example:
- What is the new branching effort?
 - Each address drives half the lines of the small decoder
 - Each predecoder output drives $256/16$ post-decoder gates
 - In summary, the branching effort is:
$$B = \text{baddr driver} \cdot \text{bpredecoder} = 16/2 \cdot 256/16 = 128$$
- Same as before

Precoding Example

- We can try using four 2-input predecoders:
 - This will require us to use 256 4-input NAND gates


Decoder Layout

 - ❑ Decoders must be pitch-matched to SRAM cell
 - Requires very skinny gates




Large Decoders

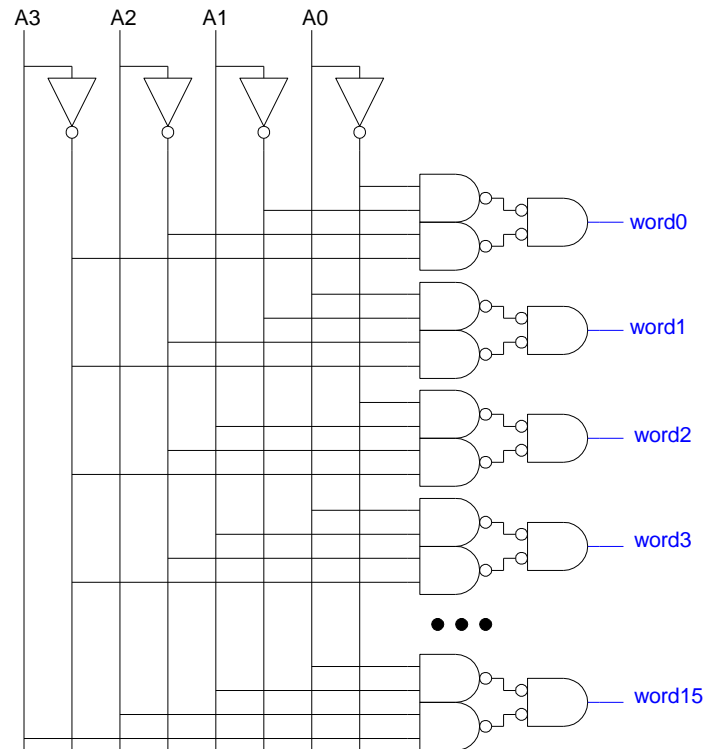- ❑ For $n > 4$, NAND gates become slow
 - Break large gates into multiple smaller gates



Predecoding

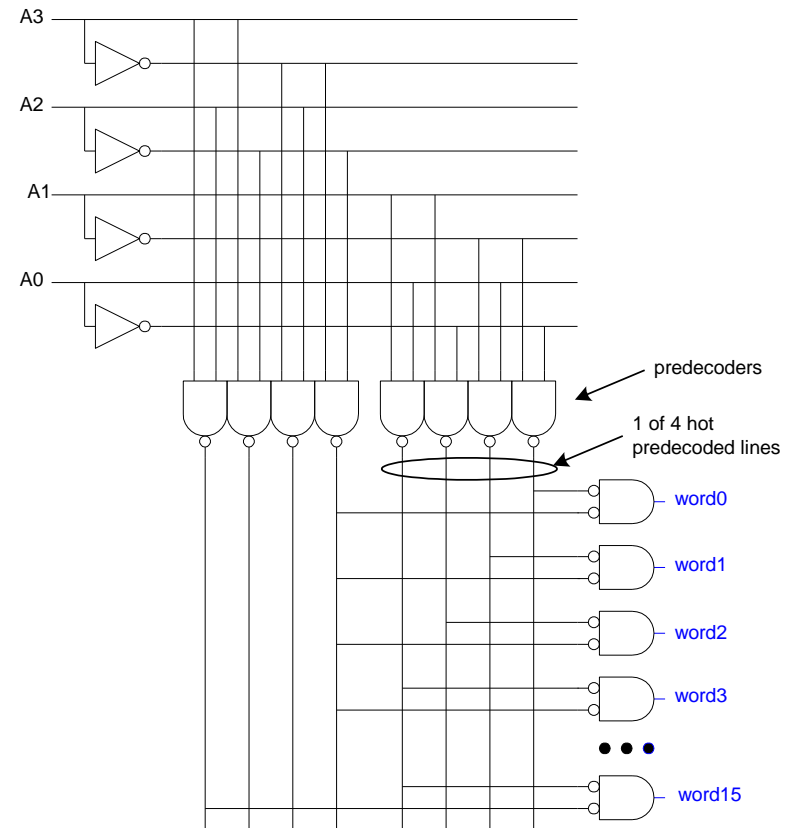- ❑ Many of these gates are redundant
 - Factor out common gates into predecoder
 - Saves area
 - Same path effort





How to Choose A Configuration


There are several factors to be considered-

- Pitch Fitting
- Switching Capacitance:
How many switch at each transition?
- Stage before the large capacitor:
Distribution of the load along the delay
- We usually do as much predecoding as possible

How to Choose A Configuration

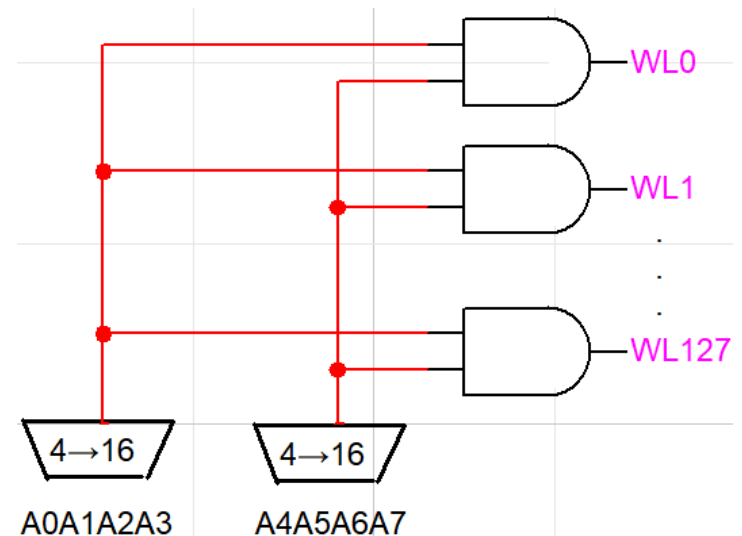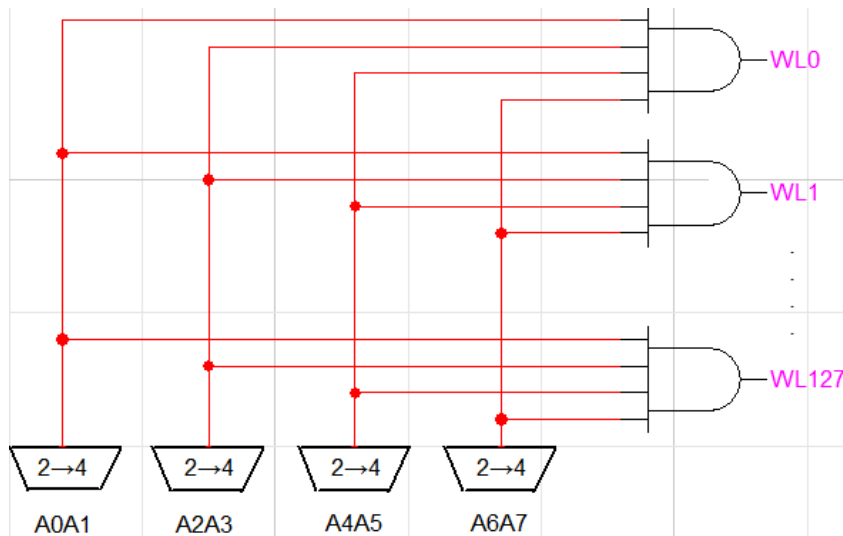

Alternative Circuit Dynamic Decoder

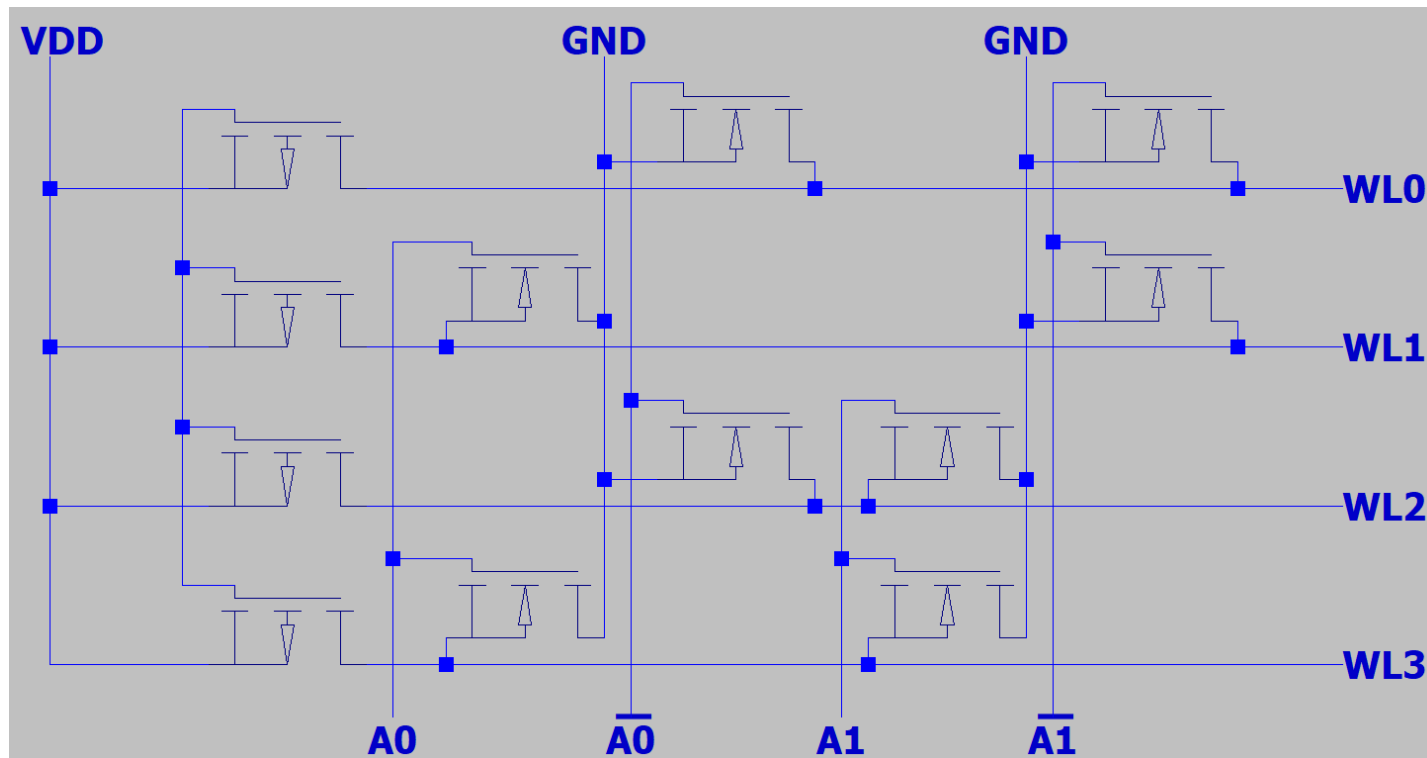


Column Circuitry


- ❑ Some circuitry is required for each column
 - Bitline conditioning
 - Sense amplifiers
 - Column multiplexing

Bitline Conditioning

- ❑ Precharge bitlines high before reads

 

 - ❑ Equalize bitlines to minimize voltage difference when using sense amplifiers



Sense Amplifier: Why?

- ❑ Bit line cap significant for large array
 - If each cell contributes 2fF,
 - for 256 cells, 512fF plus wire cap
 - Pull-down resistance is about 15K
 - $RC = 7.5\text{ns!}$ (assuming $\Delta V = V_{dd}$)
- ❑ Cannot easily change R , C , or V_{dd} , but **can** change ΔV i.e. smallest sensed voltage
 - Can reliably sense ΔV as small as $<50\text{mV}$

Cell pull down resistance

$$\tau = \frac{RC\Delta V}{V_{dd}}$$


Cell current

Sense Amplifiers

- ❑ Bitlines have many cells attached
 - Ex: 32-kbit SRAM has 256 rows x 128 cols
 - 128 cells on each bitline
- ❑ $t_{pd} \propto (C/I) \Delta V$
 - Even with shared diffusion contacts, 64C of diffusion capacitance (big C)
 - Discharged slowly through small transistors (small I)
- ❑ *Sense amplifiers* are triggered on small voltage swing (reduce ΔV)


Differential Pair Amp

 - ❑ Differential pair requires no clock
- ❑ But always dissipates static power




Clocked Sense Amp

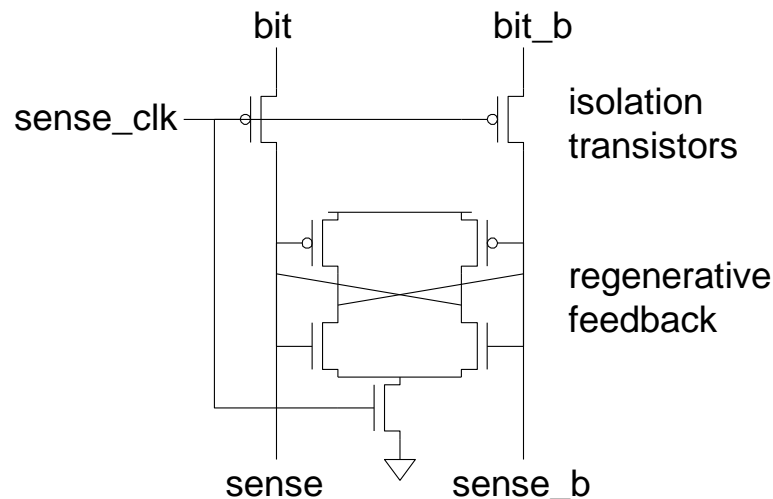- ❑ Clocked sense amp saves power
- ❑ Requires sense_clk after enough bitline swing
- ❑ Isolation transistors cut off large bitline capacitance



Twisted Bitlines

 - ❑ Sense amplifiers also amplify noise
 - Coupling noise is severe in modern processes
 - Try to couple equally onto bit and bit_b
 - Done by *twisting* bitlines




Column Multiplexing

- ❑ Recall that array may be folded for good aspect ratio
- ❑ Ex: 2 kword x 16 folded into 256 rows x 128 columns
 - Must select 16 output bits from the 128 columns
 - Requires 16 8:1 column multiplexers


Tree Decoder Mux

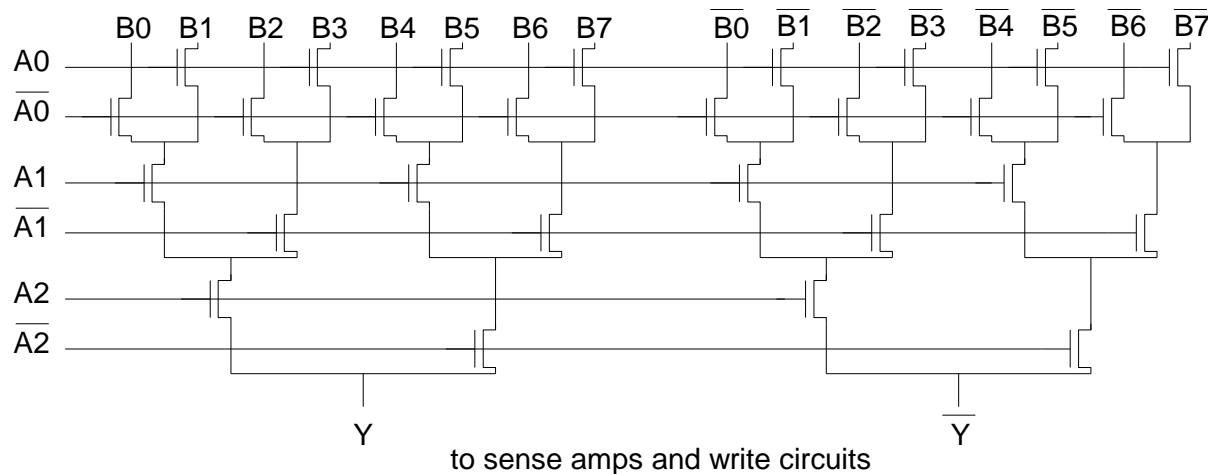- ❑ Column mux can use pass transistors
 - Use nMOS only, precharge outputs
- ❑ One design is to use k series transistors for $2^k:1$ mux
 - No external decoder logic needed (big area reduction)




Single Pass-Gate Mux

 
- ❑ Or eliminate series transistors with separate decoder




Ex: 2-way Muxed SRAM

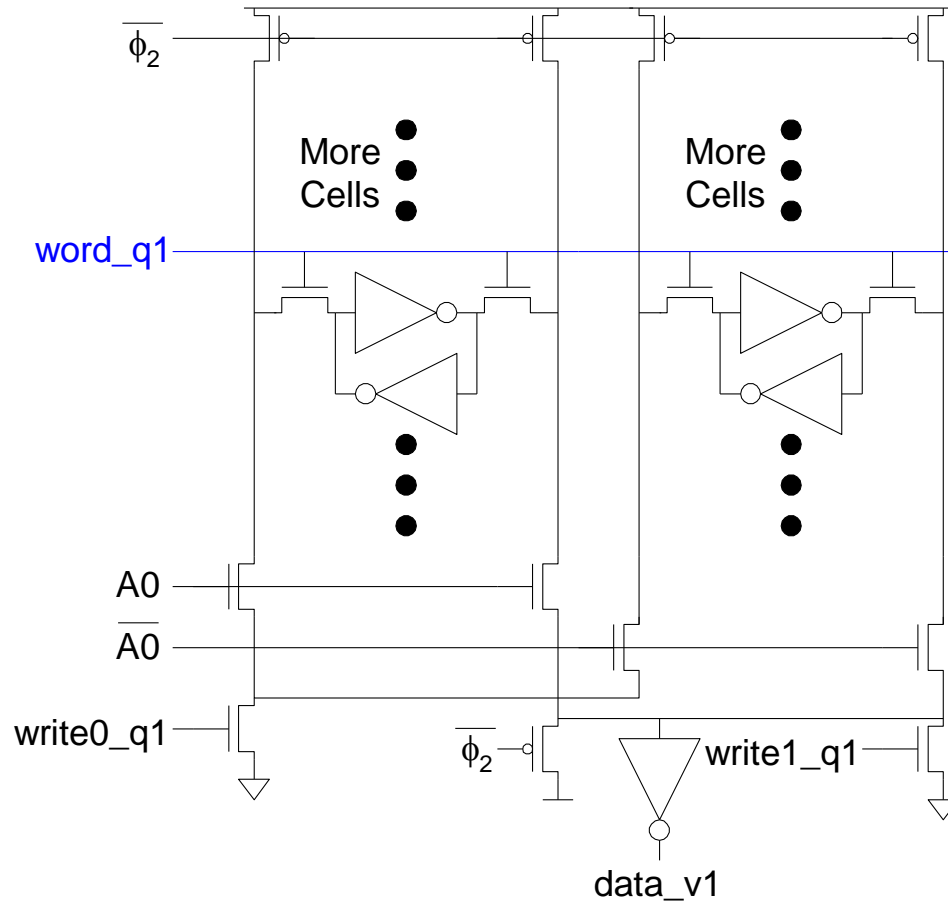


High-level view of an SRAM

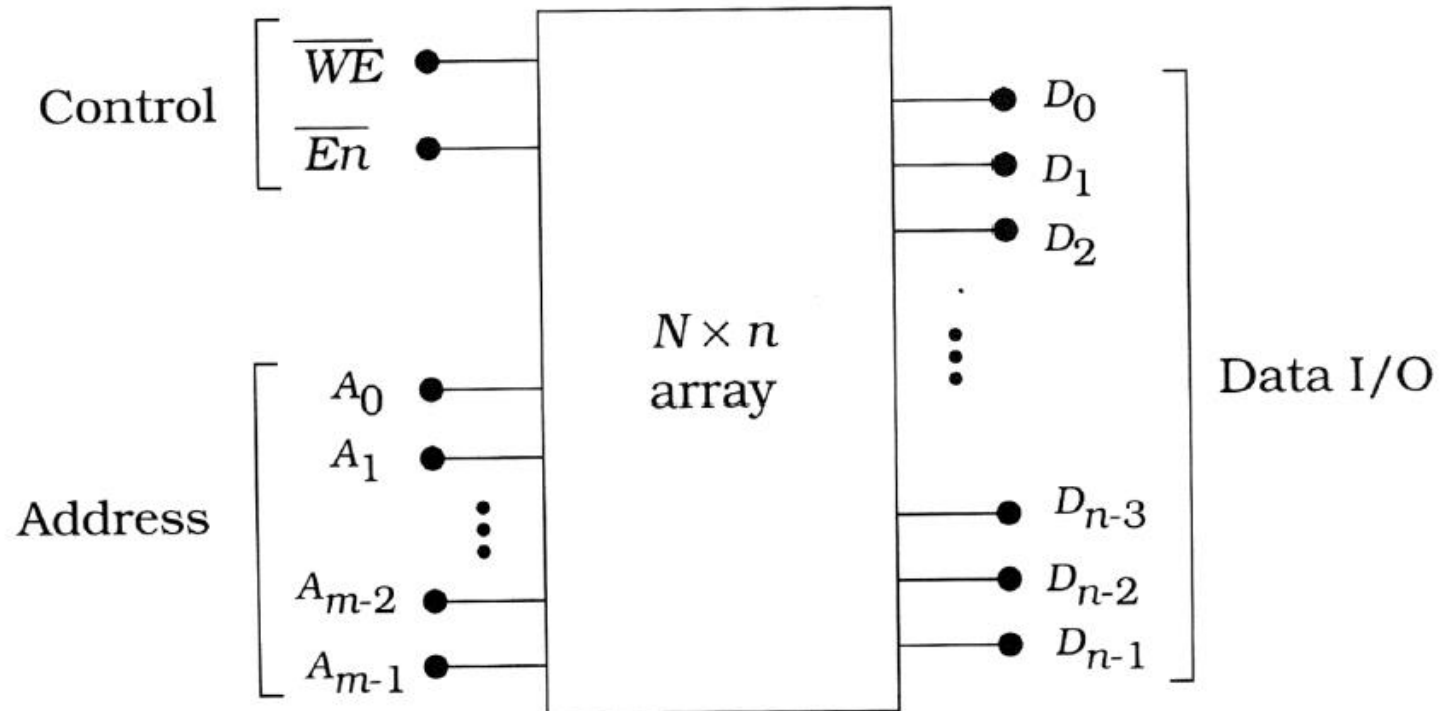


Cell Arrangement in a Core Region

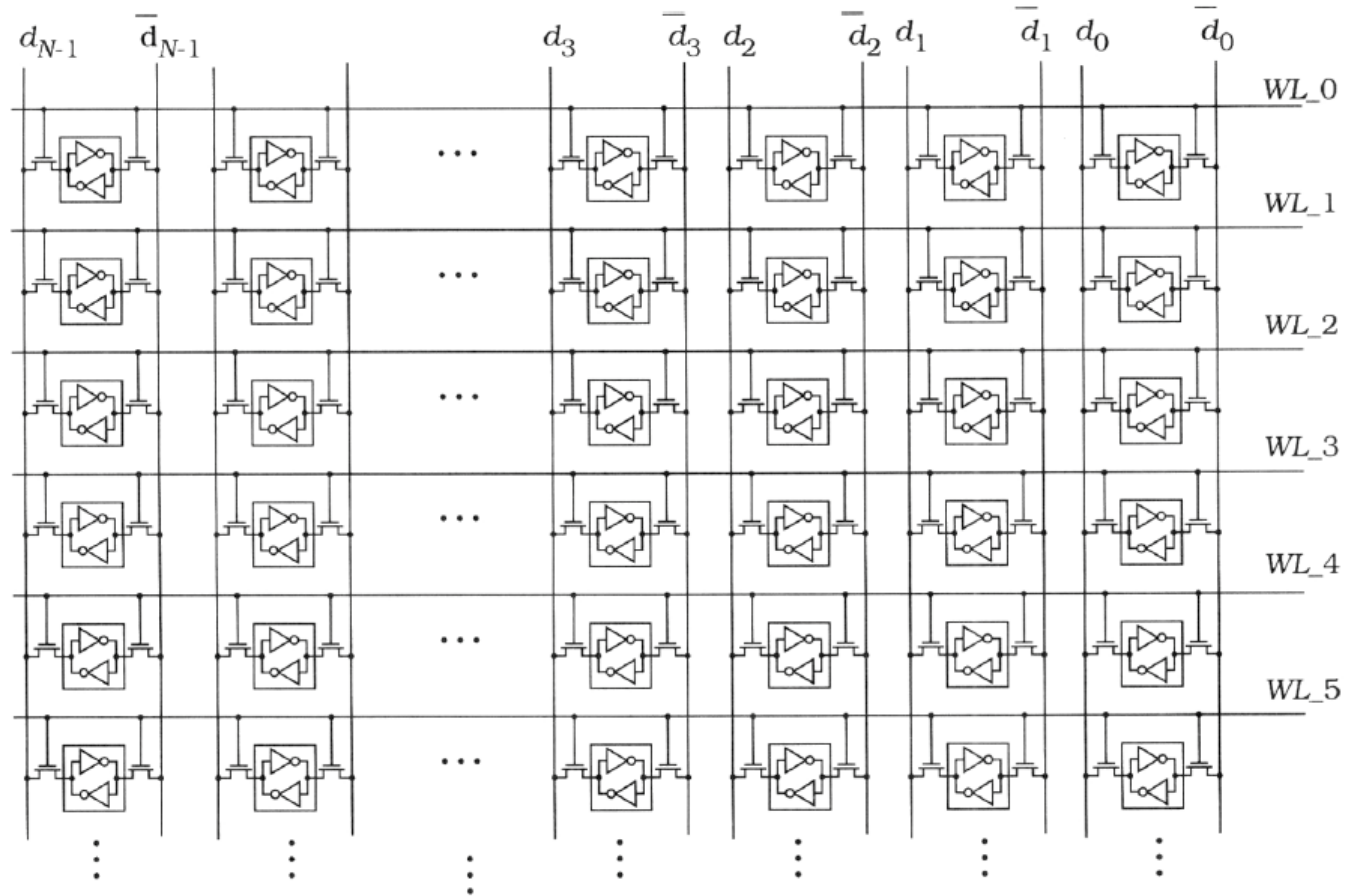


Column MUX/DeMUX network for 8-bit Words

 


Basic Address Scheme

 

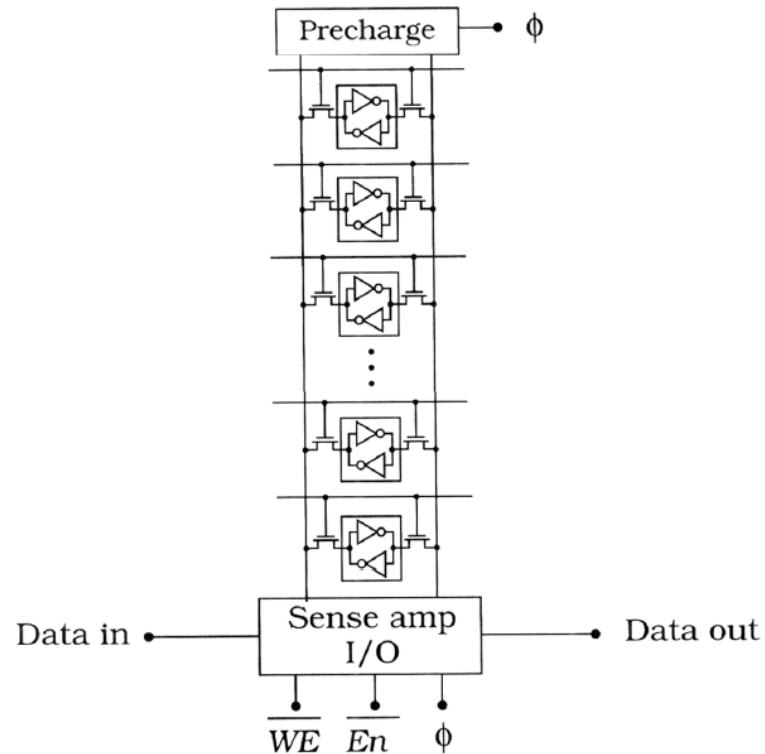Precharge and I/O Circuits for a Single Column



Example View of Column Circuitry

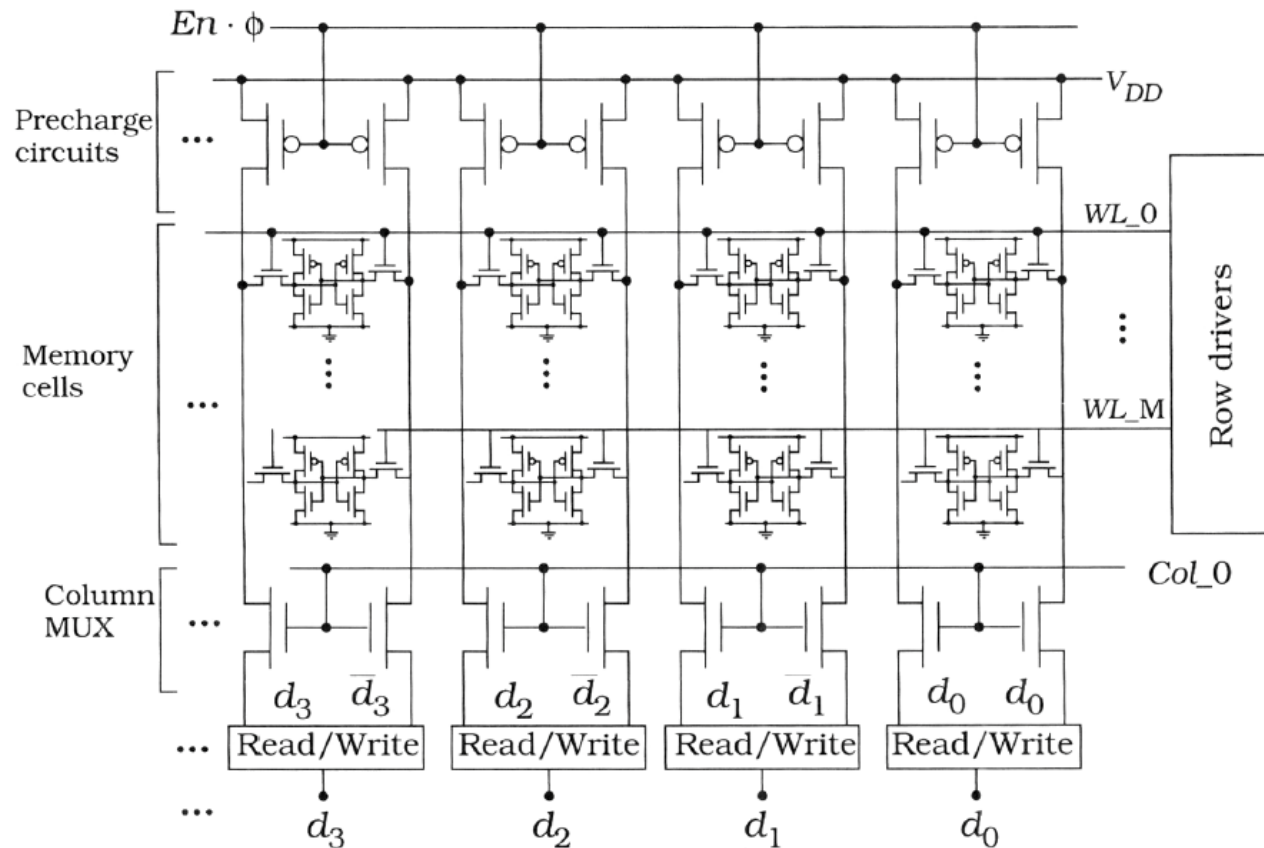


Multiple Ports

- ❑ We have considered single-ported SRAM
 - One read or one write on each cycle
- ❑ *Multiported* SRAM are needed for register files
- ❑ Examples:
 - Multicycle MIPS must read two sources or write a result on some cycles
 - Pipelined MIPS must read two sources and write a third result each cycle
 - Superscalar MIPS must read and write many sources and results each cycle

Dual-Ported SRAM

 
- ❑ Simple dual-ported SRAM
 - Two independent single-ended reads
 - Or one differential write



- ❑ Do two reads and one write by time multiplexing
 - Read during ph1, write during ph2

Multi-Ported SRAM

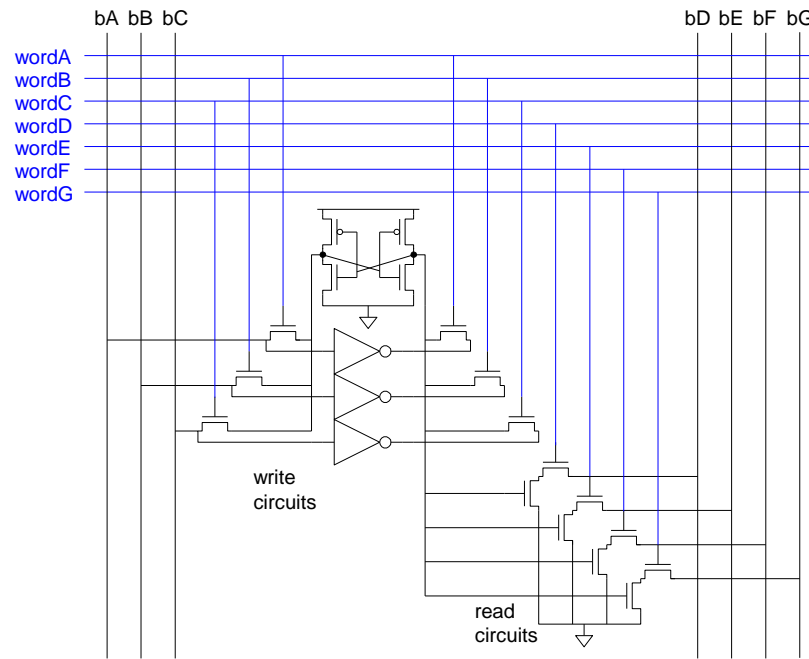- ❑ Adding more access transistors hurts read stability
- ❑ Multiported SRAM isolates reads from state node
- ❑ Single-ended design minimizes number of bitlines




Serial Access Memories

- ❑ Serial access memories do not use an address
 - Shift Registers
 - Tapped Delay Lines
 - Serial In Parallel Out (SIPO)
 - Parallel In Serial Out (PISO)
 - Queues (FIFO, LIFO)


Shift Register

 - ❑ *Shift registers* store and delay data
- ❑ Simple design: cascade of registers
 - Watch your hold times!




Denser Shift Registers

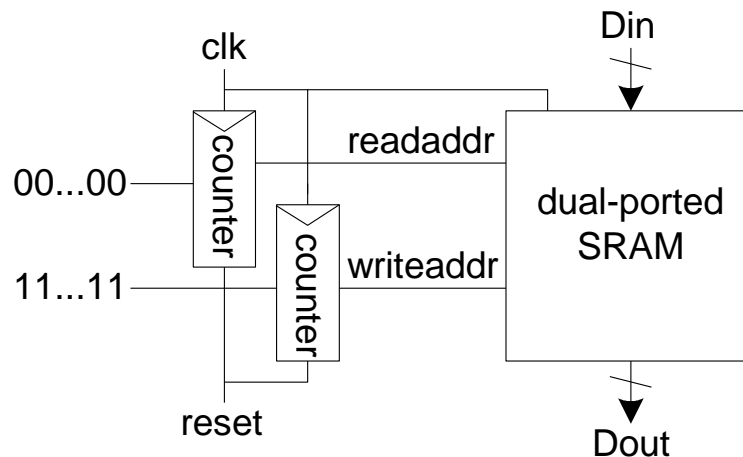- ❑ Flip-flops aren't very area-efficient
- ❑ For large shift registers, keep data in SRAM instead
- ❑ Move read/write pointers to RAM rather than data
 - Initialize read address to first entry, write to last
 - Increment address on each cycle




Tapped Delay Line

 - ❑ A *tapped delay line* is a shift register with a programmable number of stages
- ❑ Set number of stages with delay controls to mux
 - Ex: 0 – 63 stages of delay




Serial In Parallel Out

 - ❑ 1-bit shift register reads in serial data
 - After N steps, presents N-bit parallel output




Parallel In Serial Out

 - ❑ Load all N bits in parallel when shift = 0
 - Then shift one bit out per cycle



Queues

 - ❑ *Queues* allow data to be read and written at different rates.
- ❑ Read and write each use their own clock, data
- ❑ Queue indicates whether it is full or empty
- ❑ Build with SRAM and read/write counters (pointers)



FIFO, LIFO Queues

❑ *First In First Out* (FIFO)

- Initialize read and write pointers to first element
- Queue is EMPTY
- On write, increment write pointer
- If write almost catches read, Queue is FULL
- On read, increment read pointer

❑ *Last In First Out* (LIFO)

- Also called a *stack*
- Use a single *stack pointer* for read and write