

Fault Modeling

- **Some Definitions**
- **Why Modeling Faults**
- **Various Fault Models**
- **Fault Detection**
- **Fault Collapsing**

Some Real Defects in Chips

- **Processing Faults**
 - missing contact windows
 - parasitic transistors
 - oxide breakdown
- **Material Defects**
 - bulk defects (cracks, crystal imperfections)
 - surface impurities (ion migration)
- **Time-Dependent Failures**
 - dielectric breakdown
 - Electromigration (open, short)
- **Packaging Failures**
 - contact degradation
 - seal leaks

Faults, Errors and Failures

- **Fault: A physical defect within a circuit or a system**
 - May or may not cause a system failure
- **Error: Manifestation of a fault that results in incorrect circuit (system) outputs or states**
 - Caused by faults
- **Failure: Deviation of a circuit or system from its specified behavior**
 - Fails to do what it should do
 - Caused by an error
- **Fault ---> Error ---> Failure**


Why Model Faults ?

- **Fault model identifies target faults**
 - Model faults most likely to occur
- **Fault model limits the scope of test generation**
 - Create tests only for the modeled faults
- **Fault model makes effectiveness measurable by experiments**
 - Fault coverage can be computed for specific test patterns to reflect its effectiveness
- **Fault model makes analysis possible**
 - Associate specific defects with specific test patterns

Fault Models

- **Stuck-At Faults**
- **Bridging Faults**
- **Transistor Stuck-On/Open Faults**
- **Functional Faults**
- **Memory Faults**
- **PLA Faults**
- **Delay Faults**
- **State Transition Faults**

Single Stuck-At Faults

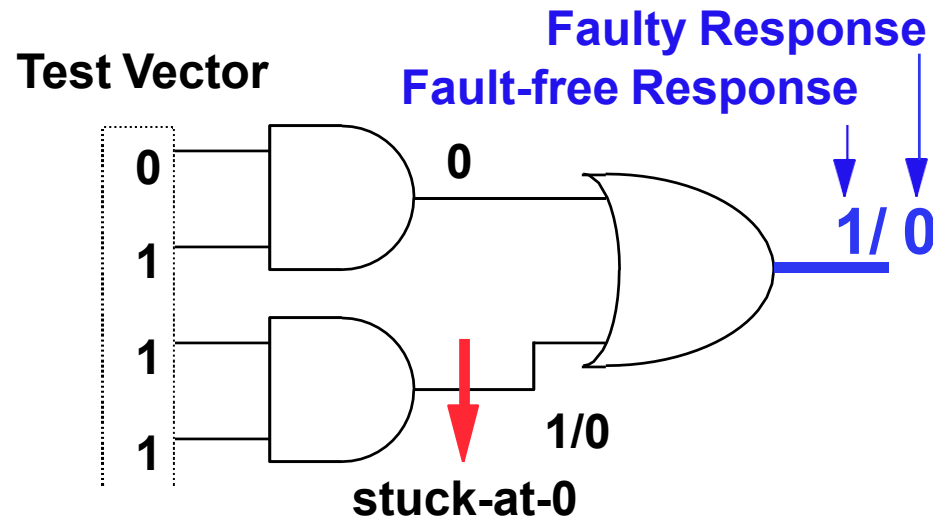

- Assumptions:
- Only one line is faulty.
 - Faulty line permanently set to 0 or 1.
 - Fault can be at an input or output of a gate.

Multiple Stuck-At Faults

- **Several stuck-at faults occur at the same time**
 - Important in high density circuits
- **For a circuit with k lines**
 - there are $2k$ single stuck-at faults
 - there are $3^k - 1$ multiple stuck-at faults

Why Single Stuck-At Fault Model?


- **Complexity is greatly reduced.**
Many different physical defects may be modeled by the same logical single stuck-at fault.
- **Single stuck-at fault is technology independent.**
Can be applied to TTL, ECL, CMOS, etc.
- **Single stuck-at fault is design style independent.**
Gate Arrays, Standard Cell, Custom VLSI
- **Even when single stuck-at fault does not accurately model some physical defects, the tests derived for logic faults are still valid for most defects.**
- **Single stuck-at tests cover a large percentage of multiple stuck-at faults.**

Bridging Faults


- **Two or more normally distinct points (lines) are shorted together**

- Logic effect depends on technology

- **Wired-AND for TTL**

 


- **Wired-OR for ECL**

 


- **CMOS ?**

CMOS Transistor Stuck-ON

 


- **Transistor stuck-on may cause ambiguous logic level.**
 - depends on the relative impedances of the pull-up & pull-down networks
- **When input is low, both P and N transistors are conducting causing increased quiescent current, called I_{DDQ} fault.**

CMOS Transistor Stuck-OPEN

 

- Transistor stuck-open may cause output floating.

CMOS Transistor Stuck-OPEN (Cont.)

 

- Can turn the circuit into a sequential one
- Stuck-open faults require two-vector tests

Functional Faults

- **Fault effects modeled at a higher level than logic for function modules, such as**


**Decoders
Multiplexers
Adders
Counters
RAMs
ROMs**

Functional Faults of Decoder

$f(L_i/L_j)$: Instead of line L_i , Line L_j is selected

$f(L_i/L_i+L_j)$: In addition to L_i , L_j is selected

 $(L_i/0)$: None of the lines are selected



Memory Faults

- **Parametric Faults**
 - Output Levels
 - Power Consumption
 - Noise Margin
 - Data Retention Time
- **Functional Faults**
 - Stuck Faults in Address Register, Data Register, and Address Decoder
 - Cell Stuck Faults
 - Adjacent Cell Coupling Faults
 - Pattern-Sensitive Faults

Memory Faults (Cont.)

- **Pattern-sensitive faults: the presence of a faulty signal depends on the signal values of the nearby points**
 - Most common in DRAMs

0	0	0
0	d	b
0	a	0

$a=b=0 \longrightarrow d=0$

$a=b=1 \longrightarrow d=1$

- **Adjacent cell coupling faults**
 - Pattern sensitivity between a pair of cells


PLA Faults

- **Stuck Faults**
- **Crosspoint Faults**
 - **Extra/Missing Transistors**
- **Bridging Faults**
- **Break Faults**

Missing Crosspoint Faults in PLA


- Missing crosspoint in AND-array
 - Growth fault
- Missing crosspoint in OR-array
 - Disappearance fault

Equivalent stuck fault representation

 


Gate-Delay-Fault

 - **Slow to rise, slow to fall**
 - \bar{x} is slow to rise when channel resistance R1 is abnormally high




Gate-Delay-Fault

 

- Disadvantage:
Delay faults resulting from the sum of several small incremental delay defects may not be detected.


Path-Delay-Fault

 - Propagation delay of the path exceeds the clock interval.
- The number of paths grows exponentially with the number of gates.




Path-Delay-Fault

 - Assume clock period = 15ns and good gate delay = 3ns
Its path delay fault is :
 - $5 + 3.5 + 4 = 12.5 < 15 \rightarrow \text{pass}$
 - $5 + 3.5 + 4 + 5 = 17.5 > 15 \rightarrow \text{fail}$




Path Delay Fault

 - Two polarity (rising, falling) for each path
- Example:
 - 5 paths (AGI, BDEGI, BDFHI, CDEGI, CDFHI)
 - 10 Delay faults
 - Two-pattern for testing falling case of BDFHI




State Transition Graph

 - Each state transition is associated with a 4-tuple: (source state, input, output, destination state)




Single State Transition Fault Model

 - A fault causes a single state transition to a wrong destination state.



Fault Detection

 - A test (vector) t detects a fault f iff $z(t) \oplus z_f(t) = 1$
 - t detects $f \iff z_f(t) \neq z(t)$
- Example



$$z_1 = x_1 x_2$$


$$z_2 = x_2 x_3$$

$$z_{1f} = x_1$$

$$z_{2f} = x_2 x_3$$

The test 001 detects f because $z_1(001)=0$ while $z_{1f}(001)=1$

Sensitization

 

$$z(1011)=0$$

$$z_f(1011)=1$$

1011 detects the fault f (G_2 stuck-at 1)

v/v_f : v = signal value in the fault free circuit

v_f = signal value in the faulty circuit

Sensitization

- **A test t that detects a fault f**
 - **Activates f (or generate a fault effect) by creating different v and v_f values at the site of the fault**
 - **Propagates the error to a primary output w by making all the lines along at least one path between the fault site and w have different v and v_f values**
- **A line whose value in the test changes in the presence of the fault f is said to be sensitized to the fault f by the test**
- **A path composed of sensitized lines is called a sensitized path**


Detectability

- A fault f is said to be detectable if there exists a test t that detects f ; otherwise, f is an undetectable fault
- For an undetectable fault f

$$z_f(x) = z(x)$$

- No test can simultaneously activate f and create a sensitized path to a primary output

Undetectable Fault

 

- ***G*₁ output stuck-at-0 fault is undetectable**
 - Undetectable faults do not change the function of the circuit
 - The related circuit can be deleted to simplify the circuit

Test Set

- **Complete detection test set:** A set of tests that detect any detectable faults in a class of faults
- **The quality of a test set is measured by fault coverage**
- **Fault coverage:** Fraction of faults that are detected by a test set
- **The fault coverage can be determined by fault simulation**
 - **>95% is typically required for single stuck-at fault model in a complex system such as a CPU**

Fault Equivalence

- **A test t distinguishes between faults α and β if $z_{\alpha}(t) \neq z_{\beta}(t)$**
- **Two faults, α & β are said to be equivalent in a circuit , iff the function under α is equal to the function under β for any input combination (sequence) of the circuit.**
 - $z_{\alpha}(t) = z_{\beta}(t)$ for all t
 - No test can distinguish between α and β
 - Any test which detects one of them detects all of them

Fault Equivalence

- AND gate: all *s-a-0* faults are equivalent
- OR gate: all *s-a-1* faults are equivalent
- NAND gate: all the input *s-a-0* faults and the output *s-a-1* faults are equivalent
- NOR gate: all input *s-a-1* faults and the output *s-a-0* faults are equivalent
- Inverter: input *s-a-1* and output *s-a-0* are equivalent
input *s-a-0* and output *s-a-1* are equivalent


Fault Equivalent Case for AND gate

A/0 C/0 B/0 are fault equivalent

Input		Output						
A	B	good	A/0	C/0	B/0	A/1	C/1	B/1
0	0	0	0	0	0	0	<u>1</u>	0
0	1	0	0	0	0	<u>1</u>	<u>1</u>	0
1	0	0	0	0	0	0	<u>1</u>	<u>1</u>
1	1	1	<u>0</u>	<u>0</u>	<u>0</u>	1	1	1

Fault Equivalence




 
- SSF on fanout stem is not equivalent to SSF on fanout branch
- D is fanout stem; E and F are fanout branch



Input			Output						
A	B	C	good	D/0	F/0	E/0	D/1	F/1	E/1
0	0	0	0	0	0	0	<u>1</u>	<u>1</u>	0
0	0	1	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	0	1	<u>0</u>	<u>0</u>	1	1	1	1
0	1	1	1	<u>0</u>	<u>0</u>	1	1	1	1
1	0	0	0	0	0	0	0	<u>1</u>	0
1	0	1	0	0	0	<u>1</u>	0	0	0
1	1	0	0	0	0	<u>1</u>	0	0	0
1	1	1	0	0	0	<u>1</u>	0	0	0

Equivalence Fault Collapsing

    - $n+2$ instead of $2n+2$ faults need to be considered for an n -input gate.




Fault Dominance

- A fault β is said to *dominate* another fault α in an irredundant circuit, iff every test (sequence) for α is also a test (sequence) for β .

$$T_\alpha \subseteq T_\beta$$

 
- No need to consider fault β for fault detection



Fault Dominance

- **AND gate:** Output *s-a-1* dominates any input *s-a-1*
- **NAND gate:** Output *s-a-0* dominates any input *s-a-1*
- **OR gate:** Output *s-a-0* dominates any input *s-a-0*
- **NOR gate:** Output *s-a-1* dominates any input *s-a-0*
- **Dominance fault collapsing:** The reduction of the set of faults to be analyzed based on dominance relation

Fault Dominance

 

- **Detect A sa1:**

$$z(t) \oplus z_f(t) = (CD \oplus CE) \oplus (D \oplus CE) = D \oplus CD = 1$$

$$\Rightarrow (C = 0, D = 1)$$

- **Detect C sa1:**

$$z(t) \oplus z_f(t) = (CD \oplus CE) \oplus (D \oplus E) = 1$$

$$\Rightarrow (C = 0, D = 1) \text{ or } (C = 0, E = 1)$$

$$C \text{ sa1} \rightarrow A \text{ sa1}$$





- **Similarly** $C \text{ sa1} \rightarrow B \text{ sa1}$

$$C \text{ sa0} \rightarrow A \text{ sa0}$$

$$C \text{ sa0} \rightarrow B \text{ sa0}$$

Fault Collapsing

    - For each n -input gate, we only need to consider $n+1$ faults



Fault Collapsing Example


Fault Equivalent :

1. { A/0, B/0, H/0}
2. { C/1, D/1, F/1, G/0}
3. { E/0, G/0, V/0}
4. { H/1, V/1, Z/1}
5. { F/0, G/1}


Fault Dominance:

6. A/1 \rightarrow H/1
7. C/0 \rightarrow F/0
8. V/0 \rightarrow Z/0
9. B/1 \rightarrow H/1
10. D/0 \rightarrow F/0
11. E/1 \rightarrow V/1

{A/0, A/1, B/1, C/0, C/1, D/0, E/1}

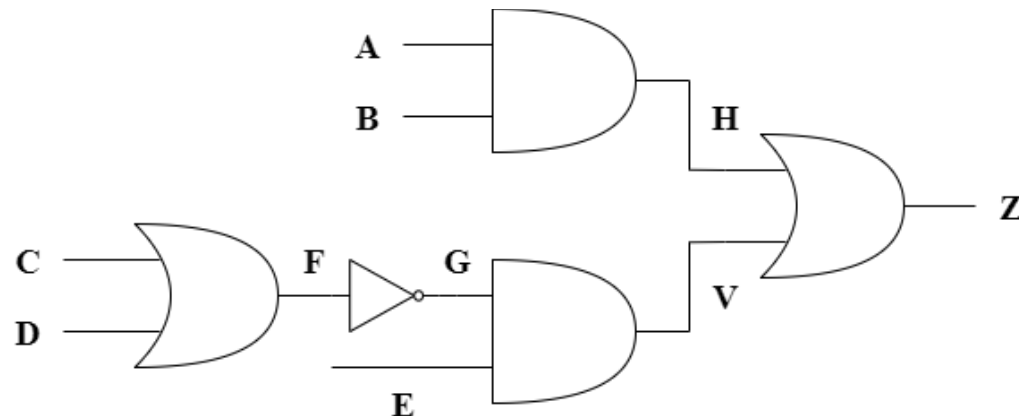

Minimum Test Vector Example

 

Minimum Test Vector Example






































A	B	C	FF	A ₀	A ₁	B ₀	B ₁	C ₀	C ₁	D ₀	D ₁	E ₀	E ₁	F ₀	F ₁	G ₀	G ₁	H ₀	H ₁
0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1
0	0	1	0	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
0	1	0	0	0	1	0	0	0	1	0	0	0	0	0	1	0	1	0	1
0	1	1	1	1	1	0	1	0	1	0	1	0	1	1	1	0	1	0	1
1	0	0	0	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
1	0	1	0	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	0	1	1	1	0	1	0	1	0	1	1	1	0	1
1	1	1	1	1	1	0	1	1	1	0	1	0	1	1	1	1	1	0	1

Minimum Test Vector Example (cont')

A	B	C	A ₀ '	A ₁ '	B ₀ '	B ₁ '	C ₀ '	C ₁ '	D ₀ '	D ₁ '	E ₀ '	E ₁ '	F ₀ '	F ₁ '	G ₀ '	G ₁ '	H ₀ '	H ₁ '
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1
0	0	1	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
0	1	0	0	1	0	0	0	1	0	0	0	0	0	1	0	1	0	1
0	1	1	0	0	1	0	1	0	1	0	1	0	0	0	1	0	1	0
1	0	0	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
1	0	1	0	0	0	1	0	0	0	1	0	1	0	1	0	1	0	1
1	1	0	1	0	1	0	0	0	1	0	1	0	1	0	1	0	1	0
1	1	1	0	0	1	0	0	0	1	0	1	0	0	0	1	0	1	0

(110, 010, 011) + (001 or 100 or 101)

Minimum Test Vector Example (cont')

A	B	C	 A ₀ '	 A ₁ '	 B ₀ '	 B ₁ '	 C ₀ '	 C ₁ '	 D ₀ '	 D ₁ '	 E ₀ '	 E ₁ '	 F ₀ '	 F ₁ '	 G ₀ '	 G ₁ '	 H ₀ '	 H ₁ '
0	0	0	0	0	0	0	0	0	0	0	0	0	0	1	0	1	0	1
 0	 0	1	0	0	0	 1	0	0	0	 1	0	 1	0	 1	0	 1	0	 1
0	1	0	0	1	0	0	0	1	0	0	0	0	0	1	0	1	0	1
0	1	1	0	0	1	0	1	0	1	0	1	0	0	0	1	0	1	0
 1	 0	0	0	0	0	 1	0	0	0	 1	0	 1	0	 1	0	 1	0	 1
 1	 0	1	0	0	0	 1	0	0	0	 1	0	 1	0	 1	0	 1	0	 1
1	1	0	1	0	1	0	0	0	1	0	1	0	1	0	1	0	1	0
1	1	1	0	0	1	0	0	0	1	0	1	0	0	0	1	0	1	0

(110, 010, 011) + (001 or 100 or 101)

A₀' = A₀ XOR FF