

Introduction to CMOS VLSI Design


Lecture 14: CAMs, ROMs, and PLAs

Outline

- ❑ Content-Addressable Memories
- ❑ Read-Only Memories
- ❑ Programmable Logic Arrays



CAMs

 - ❑ Extension of ordinary memory (e.g. SRAM)
 - Read and write memory as usual
 - Also *match* to see which words contain a *key*



10T CAM Cell

  - Add four match transistors to 6T SRAM
 - 56 x 43 λ unit cell



CAM Cell Operation


- ❑ Read and write like ordinary SRAM

- ❑ For matching:

- Leave wordline low
- Precharge matchlines
- Place key on bitlines
- Matchlines evaluate

- ❑ Miss line

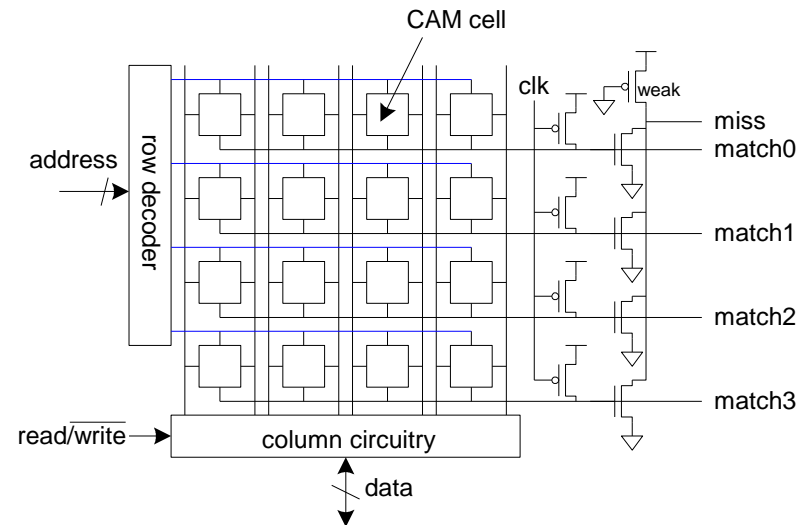- Pseudo-nMOS NOR of match lines
- Goes high if no words match



Read-Only Memories

- ❑ Read-Only Memories are nonvolatile
 - Retain their contents when power is removed
- ❑ Mask-programmed ROMs use one transistor per bit
 - Presence or absence determines 1 or 0

ROM Example

❑ 4-word x 6-bit ROM



- Represented with dot diagram
- Dots indicate 1's in ROM

Word 0: 010101

Word 1: 011001

Word 2: 100101


Word 3: 101010

  

Looks like 6 4-input pseudo-nMOS NORs


ROM Array Layout

 - Unit cell is $12 \times 8 \lambda$ (about 1/10 size of SRAM)




Row Decoders

 - ❑ ROM row decoders must pitch-match with ROM
 - Only a single track per word!




Complete ROM Layout

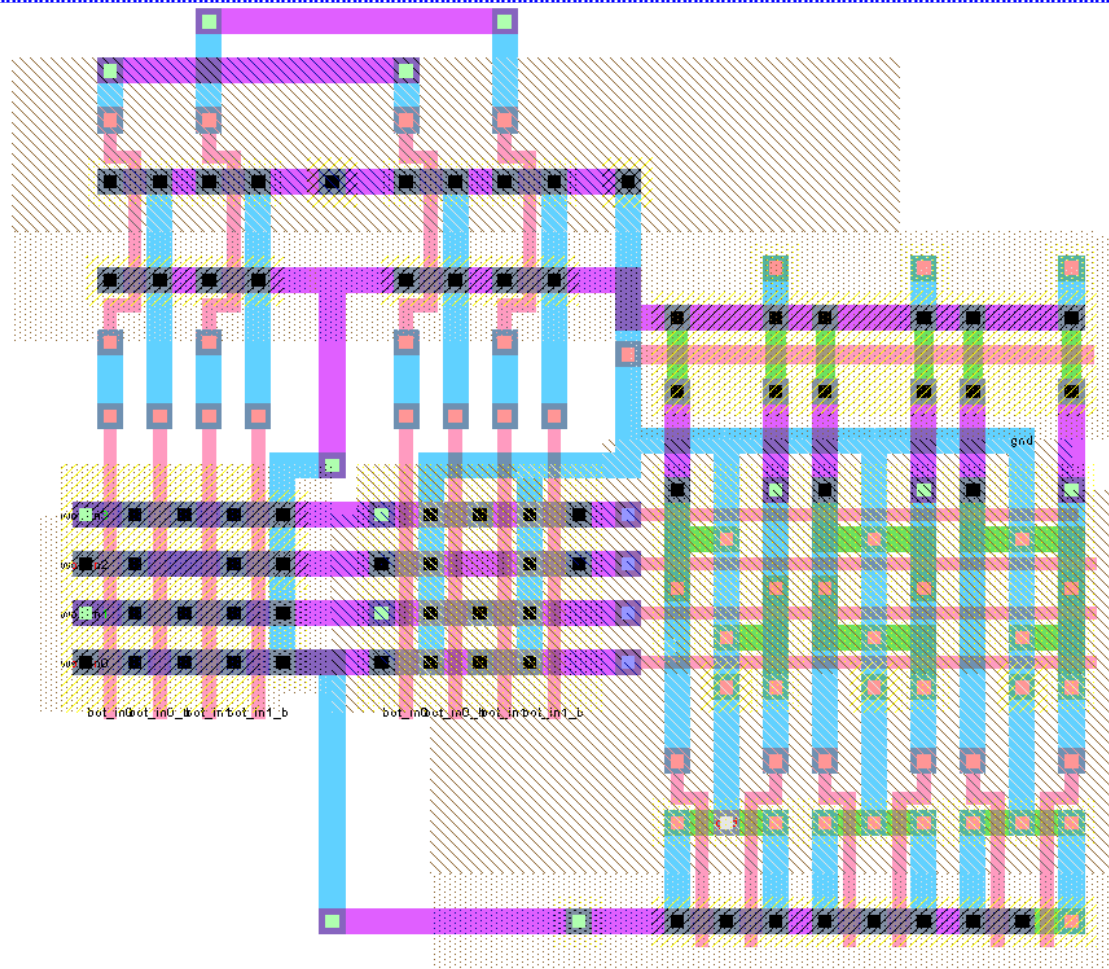

PROMs and EPROMs

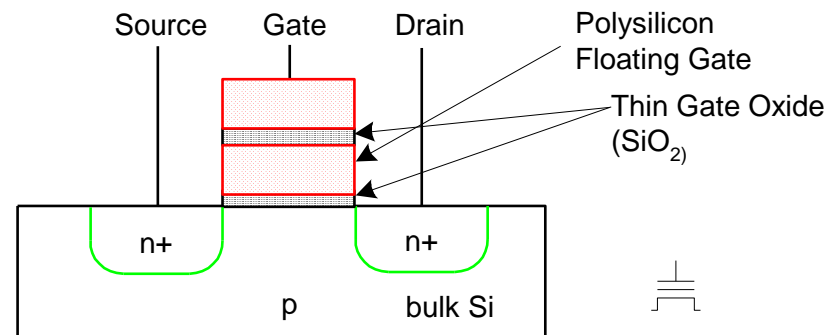- ❑ Programmable ROMs
 - Build array with transistors at every site
 - Burn out fuses to disable unwanted transistors
- ❑ Electrically Programmable ROMs
 - Use floating gate to turn off unwanted transistors
 - EPROM, EEPROM, Flash




PLAs

- ❑ A *Programmable Logic Array* performs any function in sum-of-products form.
- ❑ *Literals*: inputs & complements
- ❑ *Products / Minterms*: AND of literals
- ❑ *Outputs*: OR of Minterms

- ❑ Example: Full Adder



$$s = a\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c + abc$$

$$c_{\text{out}} = ab + bc + ac$$


 


NOR-NOR PLAs

  - ❑ ANDs and ORs are not very efficient in CMOS
- ❑ Dynamic or Pseudo-nMOS NORs are very efficient
- ❑ Use DeMorgan's Law to convert to all NORs



PLA Schematic & Layout

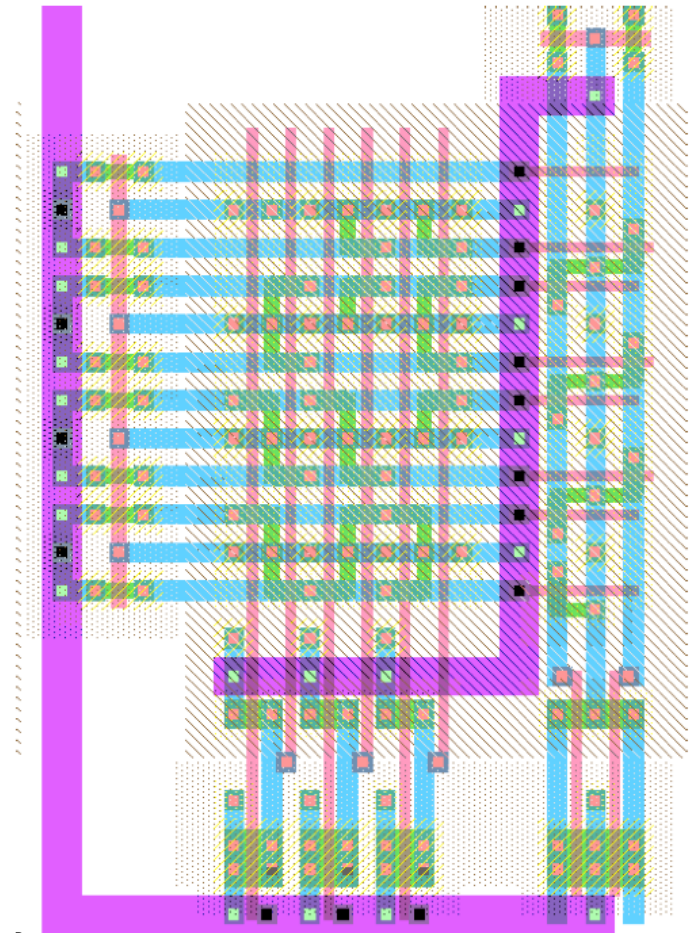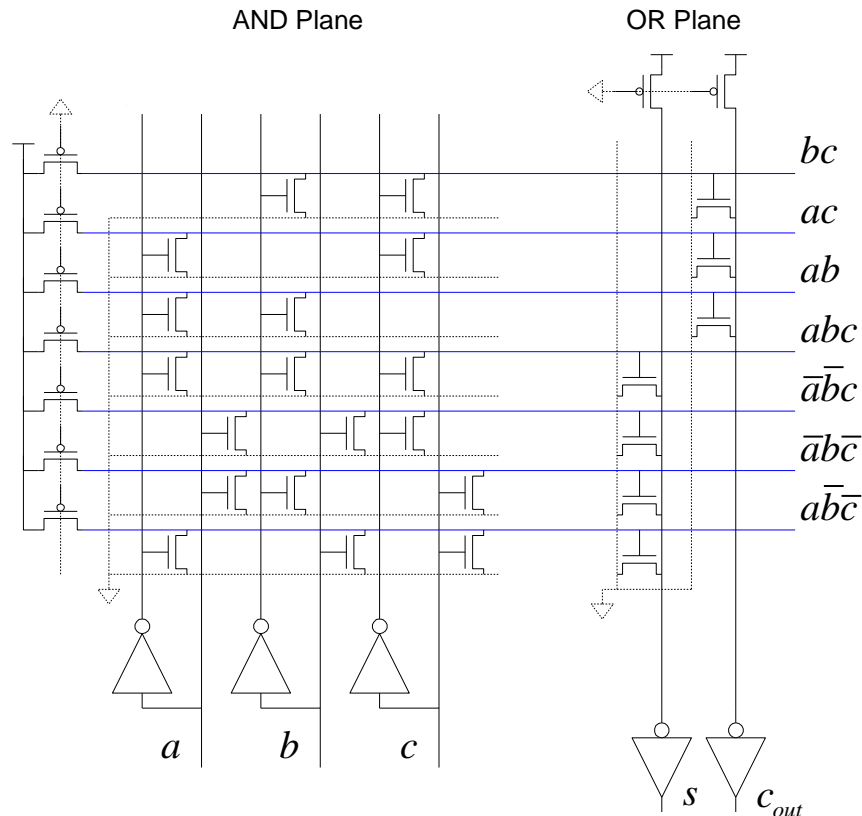

PLAs vs. ROMs

- ❑ The OR plane of the PLA is like the ROM array
- ❑ The AND plane of the PLA is like the ROM decoder
- ❑ PLAs are more flexible than ROMs
 - No need to have 2^n rows for n inputs
 - Only generate the minterms that are needed
 - Take advantage of logic simplification