

Design for Testability

- **Introduction**
- **Testability Measurement**
- **DFT Basics**
- **DFT Techniques**
 - **ad hoc**
 - **Scan design**
 - **Boundary scan**

Introduction

- **Improve Testability (Controllability and Observability)**
- **Reduce ATPG Efforts**
 - **ATPG Development More Efficient**
- **Improve Test Quality**
 - **High Fault Coverage**
- **Reduce Test Cost**
 - **Decrease Test Pattern Length and Test Time**
- **Reduce Time to Market**
 - **Easy Debug and Diagnosis**

Testability

- **Controllability:** The ability to set some circuit nodes to a certain states or logic values.
- **Observability:** The ability to observe the state or logic values of internal nodes.

Usage of Testability Measures

- **Speed up test generation**
- **Improve the design testability**
- **Guide the DFT insertion**

Testability Measurement

- TMEAS [Stephenson & Grason, 1976]
- SCOAP [Goldstein, 1979]
- TESTSCREEN [Kovijanic 1979]
- CAMELOT [Bennetts *et al.*, 1980]
- VICTOR [Ratiu *et al.*, 1982]

SCOAP

- Sandia Controllability Observability Analysis Program.
- Using integers to reflect the difficulty of controlling and observing the internal nodes.
- Higher numbers indicate more difficult to control or observe.
- Applicable to both combinational & sequential circuits.

Measurement in SCOAP

- For a node A:

$CC^0(A)$: Combinational 0-controllability

$CC^1(A)$: Combinational 1-controllability

$SC^0(A)$: Sequential 0-controllability


$SC^1(A)$: Sequential 1-controllability

$CO(A)$: Combinational observability

$SO(A)$: Sequential observability

Combinational Components in SCOAP

Ex:

 

$$CC^0(x) = CC^0(A) + CC^0(B) + 1;$$

$$CC^1(x) = \min\{CC^1(A), CC^1(B)\} + 1.$$


$$SC^0(x) = SC^0(A) + SC^0(B) ;$$

$$SC^1(x) = \min\{SC^1(A), SC^1(B)\}.$$

- CC implies the distance from PI
- SC implies the number of time frames needed to provide a 0 or 1.


Sequential Components in SCOAP

Ex:

 


- $CC^0(Q) = \min\{CC^0(R), CC^1(R) + CC^0(D) + CC^0(C) + CC^1(C)\}$
- $CC^1(Q) = CC^1(R) + CC^1(D) + CC^0(C) + CC^1(C)$
- $SC^0(Q) = \min\{SC^0(R), SC^1(R) + SC^0(D) + SC^0(C) + SC^1(C)\} + 1$
- $SC^1(Q) = SC^1(R) + SC^1(D) + SC^0(C) + SC^1(C) + 1$

Observability in SCOAP

 

 - $CO(P) = CO(N) + CC^1(Q) + CC^1(R) + 1$
- $SO(P) = SO(N) + SC^1(Q) + SC^1(R)$



- $CO(R) = CO(Q) + CC^1(Q) + CC^0(R)$
- $SO(R) = SO(Q) + SC^1(Q) + SC^0(R) + 1$


Initial States

- **PI: $CC^0 = CC^1 = SC^0 = SC^1 = 1$**
- **PO: $CO = SO = 0$**
- **All other numbers are initially set to ∞**

Importance of Testability Measures

- **They can guide the designers to improve the testability of their circuits.**
- **Test generation algorithms using heuristics usually apply some kind of testability measures to their heuristic operations (e.g., in making search decisions), which greatly speed up the test generation process.**

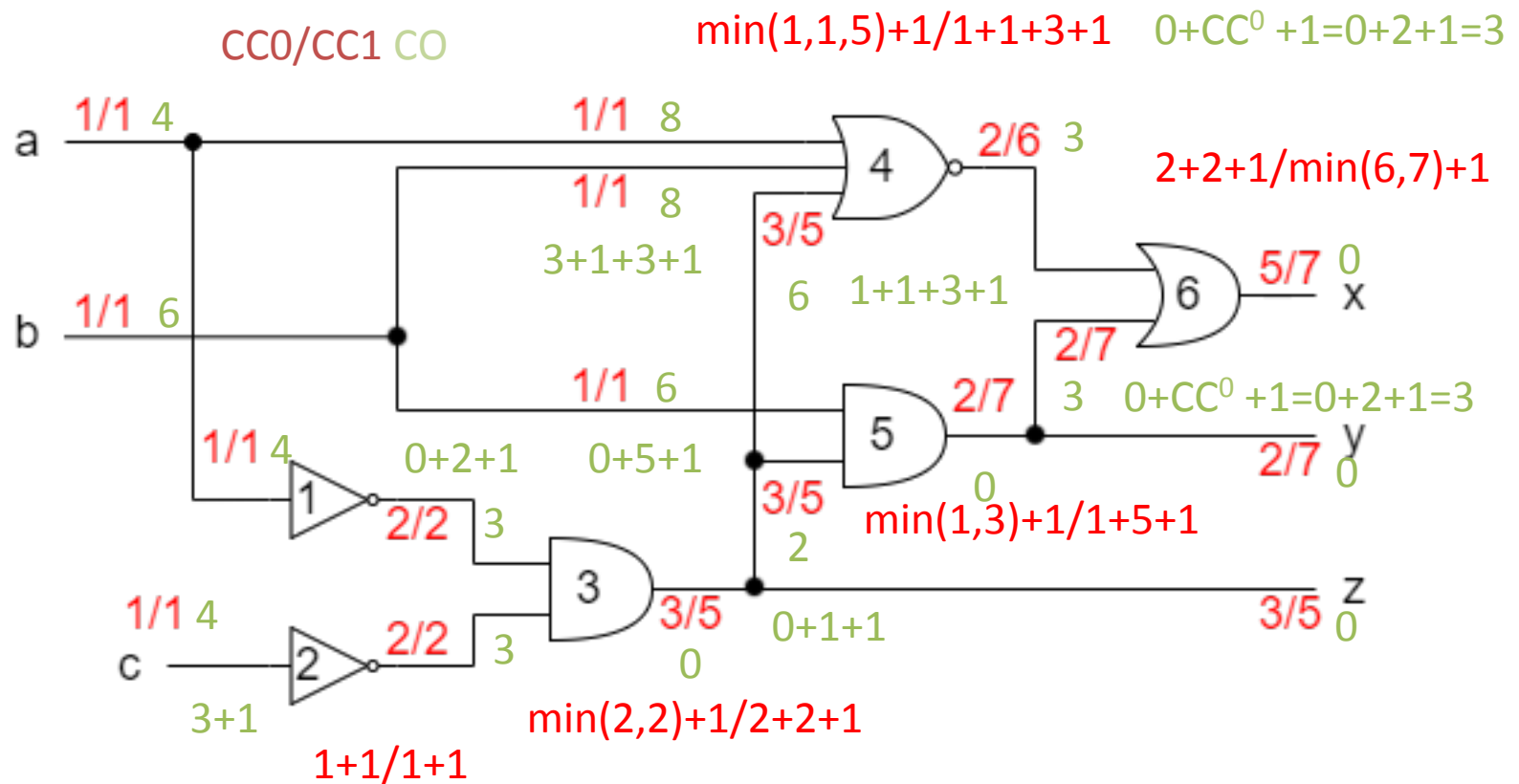Testability Measures Example (combinational)



Design for Testability (DFT)

- **Test Costs:**
 - Test Generation
 - Fault Simulation
 - Fault Location
 - Test Equipment
 - Test Application Time
- **Test Difficulties:**
 - Sequential > Combinational
 - Control Logic > Data Path
 - Random Logic > Structured Logic
 - Asynchronous > Synchronous
- **Testability**
 - Controllability
 - Observability

Design for Testability (DFT)

- **DFT techniques are design efforts specifically employed to ensure that a device is testable.**
- **In general, DFT is achieved by employing extra H/W.**
 - ⇒ **Conflict between design engineers and test engineers.**
 - ⇒ **Balanced between amount of DFT and gain achieved.**
- **Examples:**
 - **DFT**
 - ⇒ **Area ↑ & Logic complexity ↑**
 - ⇒ **Yield ↓**
 - ⇒ **For fixed fault coverage, defect level ↑**
 - **Therefore, DFT must guarantee to increase fault coverage.**

Benefits of DFT

- In general, DFT has the following benefits:
 - Fault coverage ↑
 - Test generation (development) time ↓
 - Test length
 - Test Memory } hope ↓
 - Test application time
 - Support a test hierarchy
 - Concurrent engineering
 - Reduce life-cycle costs
- ⇒ Pay less now and pay more later without DFT!

- Chips
- Boards
- Subsystems
- Systems

Costs Associated with DFTs

- **Pin Overhead**
- **Area / Yield**
- **Performance degradation**
- **Design Time**

⇒ There is no free lunch !

DFT Techniques


- **ad hoc DFT technology**
- **Scan-based design**
- **Built-In Self-Test (BIST)**
- **Boundary Scan**

Ad hoc Techniques

- **Test points**
- **Initialization**
- **Monostable multivibrators (one shot)**
- **Oscillators and clocks**
- **Counter / Shift registers**
- **Partitioning large circuits**
- **Logic redundancy**
- **Break global feedback paths**
- **⋮**


Example of *ad hoc* Techniques

- Insert test point

 

Test Points

 
- **Rule :** to enhance controllability and observability by inserting control points (cp) and observation points (op), respectively.
- **Ex:**



original circuit




testable circuit

 


can be done only for board

Test Points (Cont.)

 - Using a CP for 0-injection and an OP for observability:




- 0/1 Injection:

 

Test Points (Cont.)

- Using a MUX

 


CP2=0 : normal

CP2=1: G=1 if CP1=1


G=0 if CP2=0

Test Points (Cont.)

- **Multiplexing Observation Points:**

 

 - **Demultiplexing and Latching Control Points:**



Selection of CP


- **Control, address and data bus lines on bus-structured designs.**
- **Enable/hold inputs to microprocessors.**
- **Enable and Read/write inputs to memory.**
- **Clock and preset/reset inputs to F/Fs, counters, shift registers, etc.**
- **Data select inputs to multiplexers and demultiplexers.**
- **Control lines on tri-state devices.**

Selection of OP

- **Stem lines with high fanout.**
- **Global feedback path**
- **Redundant signal lines**
- **Outputs of devices with many inputs, e.g., multiplexers and parity generators.**
- **Outputs from state devices.**
- **Address, control, data buses**


Initialization

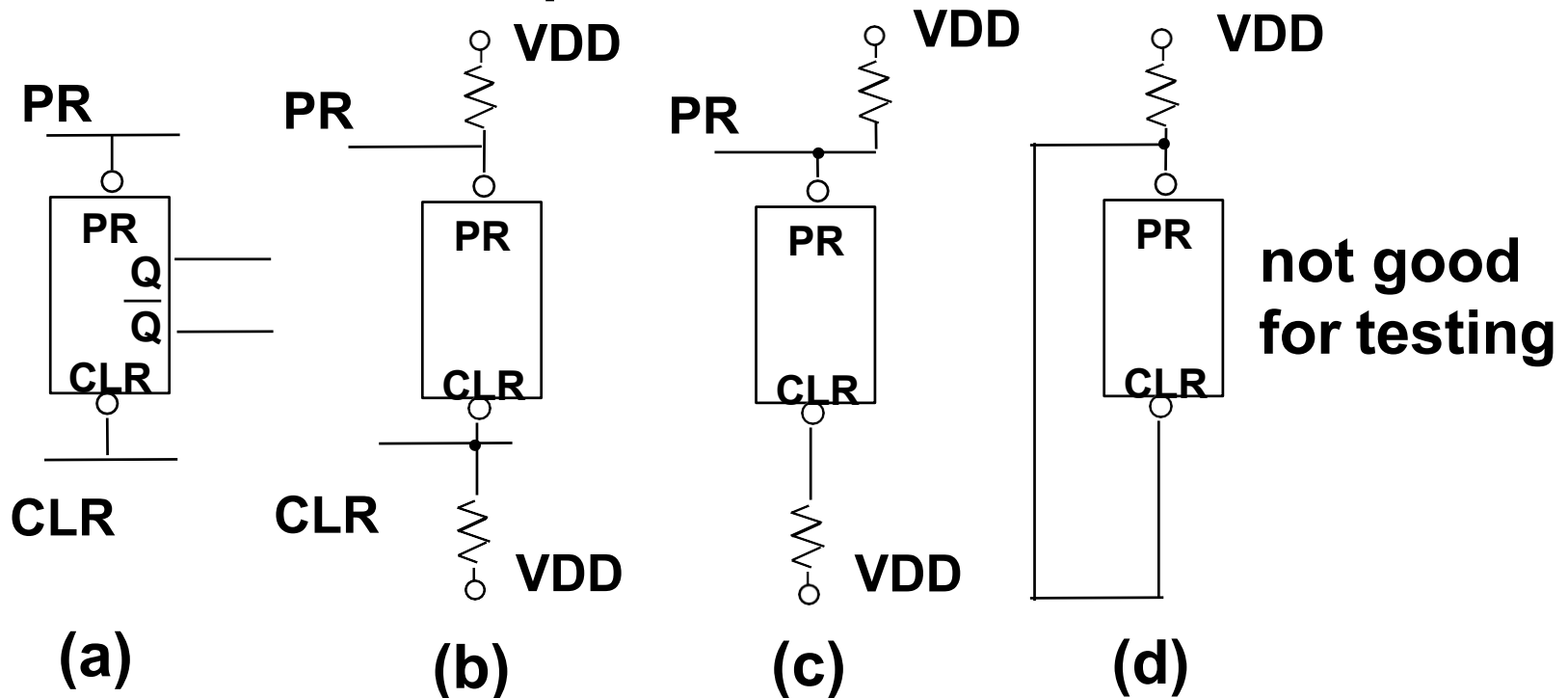- Rule: Design circuits to be easily initialized
 - Don't disable preset and clear lines





How to avoid 'x'

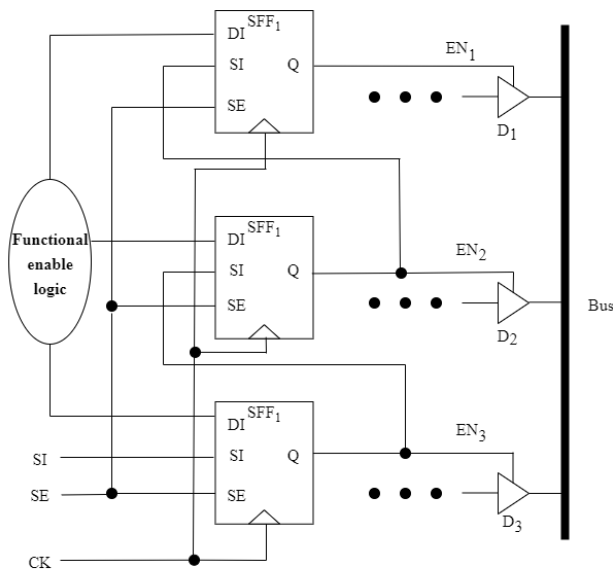Bus contention while doing scan shift or undriven bus



Original design

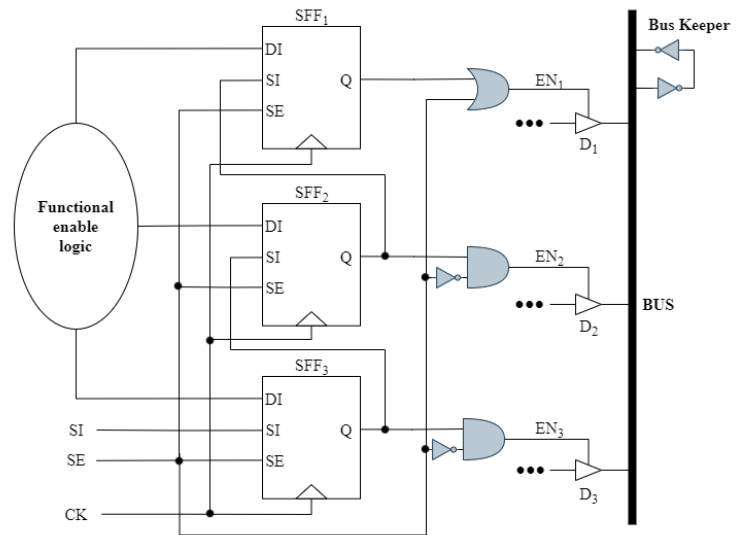 


Testable design


No bus contention when SE=1

No floatation bus

How to avoid 'x'

 


Mask Logic before MISR

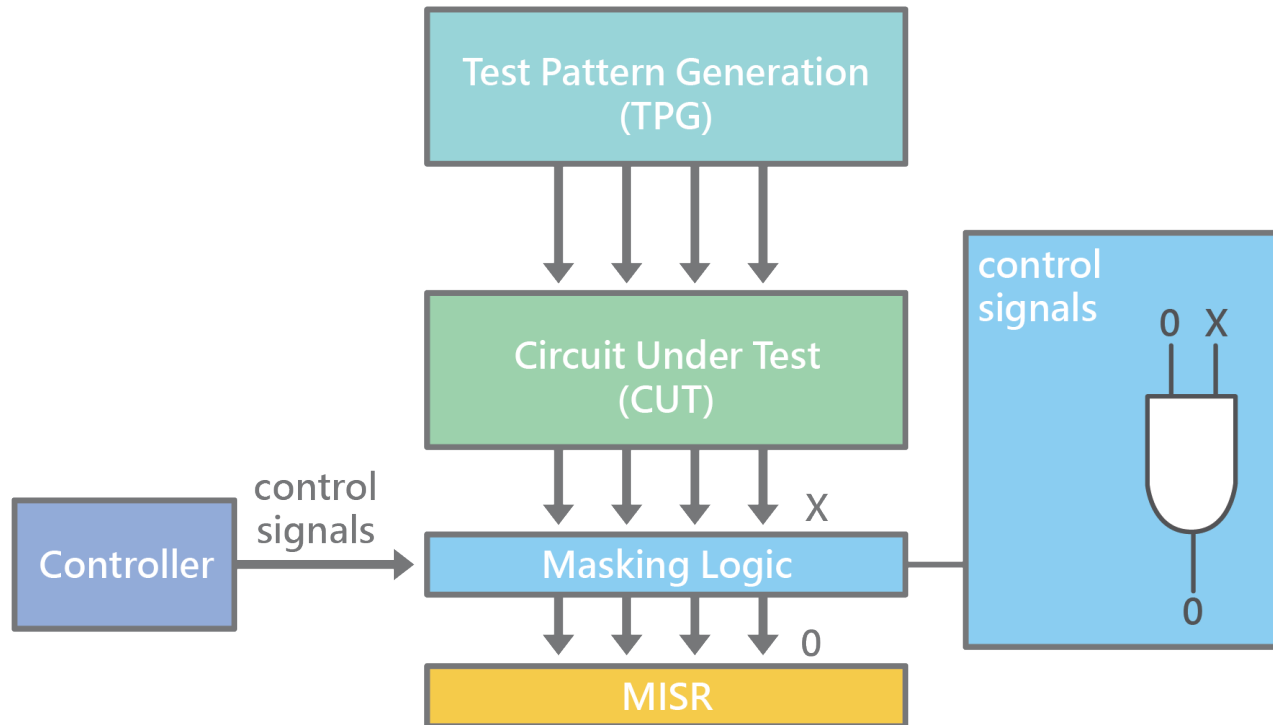


Control Random I/O Direction

Random I/O direction during scan shift

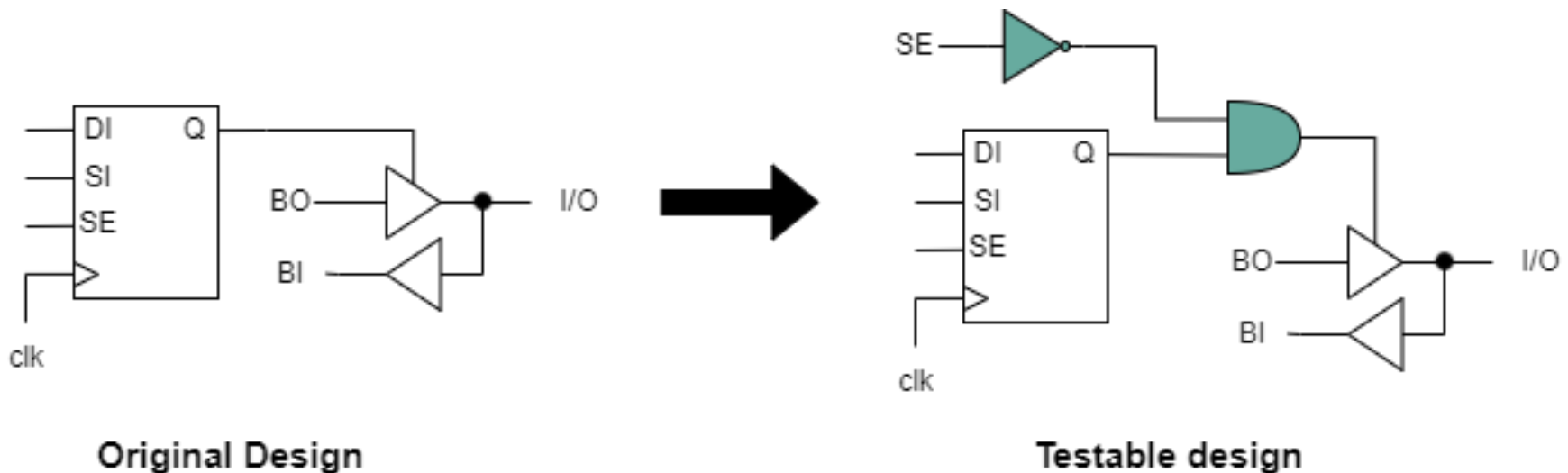


Monostable Multivibrator, Oscillators and Clocks

 - **Rule: Disable internal one shot, OSC and clocks**
 - inserting CP and/or OP while disabling these devices
- **Example:**




Gated Clock Enable Signal Noise


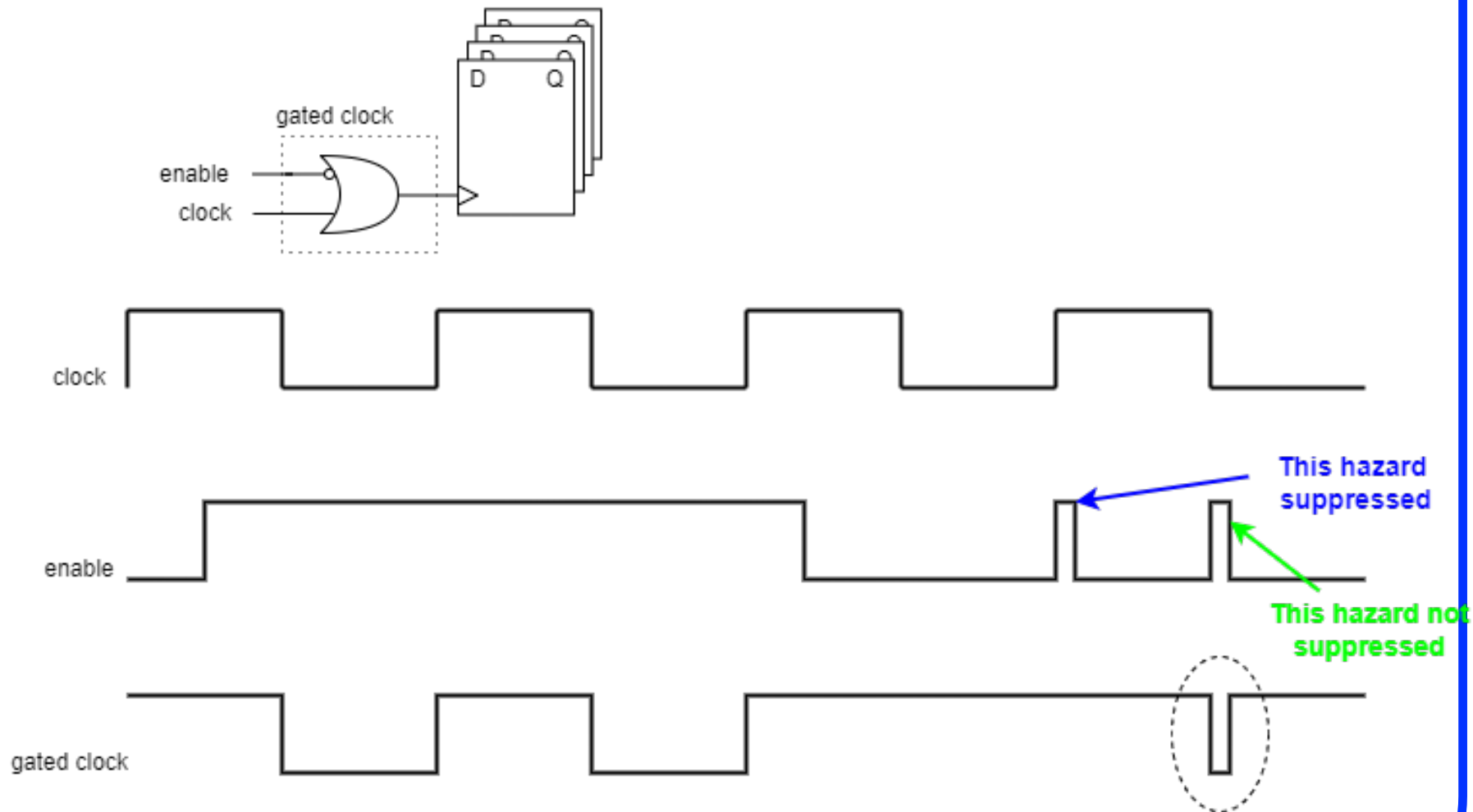


Cope With Enable Signal Noise(1)

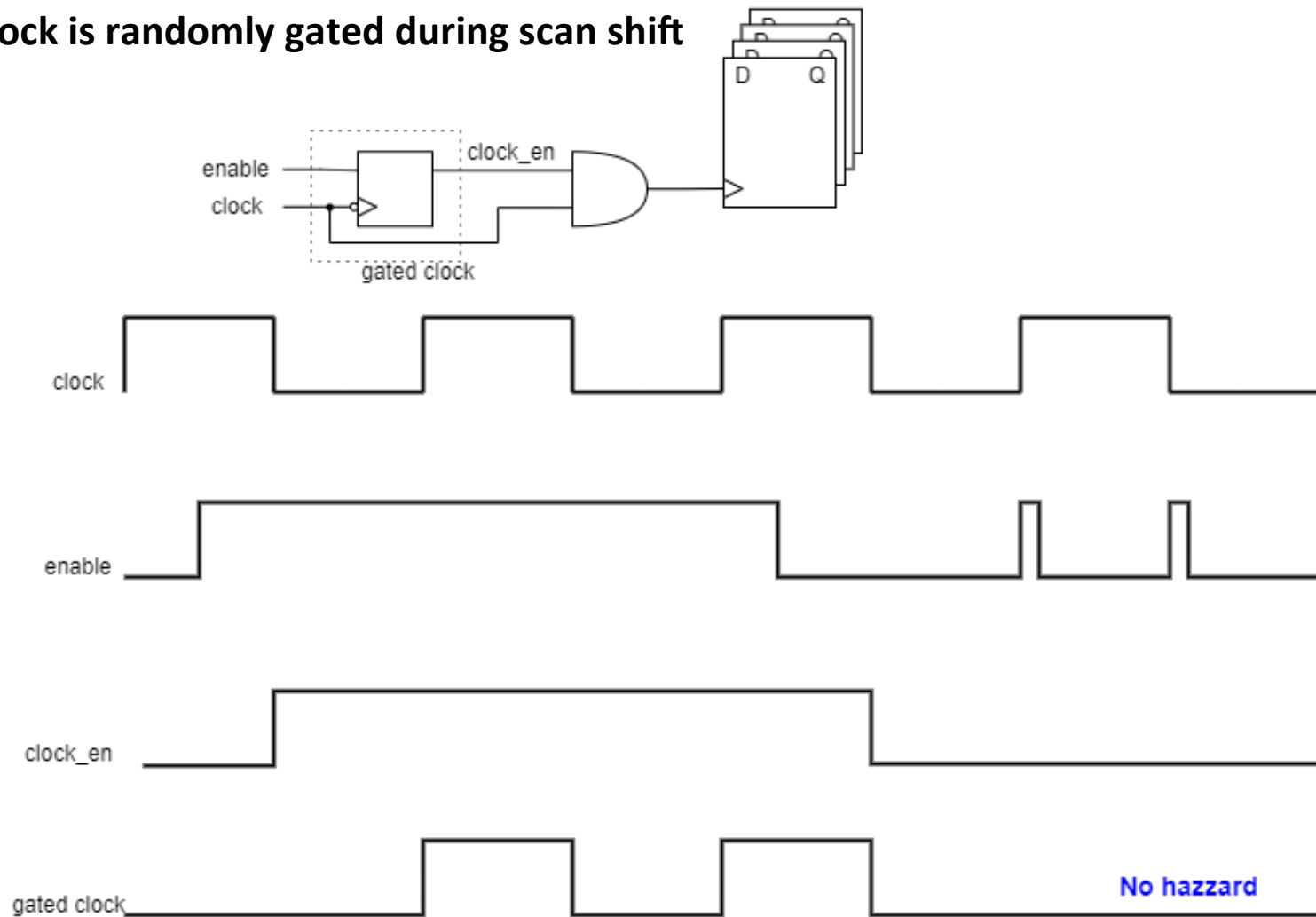- Clock is randomly gated during scan shift




Cope With Enable Signal Noise(2)

  


Partitioning Counters and Shift Registers

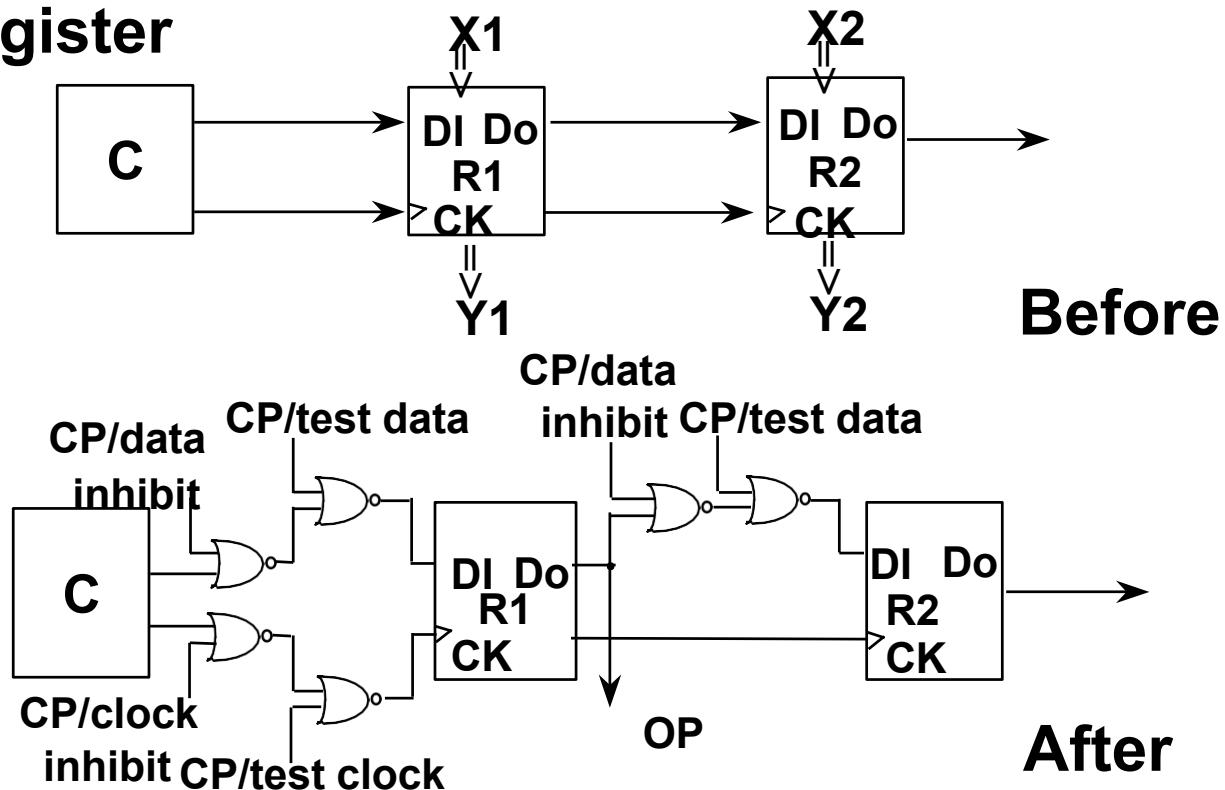
- Rule: Partition into small units
- Ex: Register



Partition of Large Combinational Circuits

 - Rule : To reduce test generation costs and/or test application time



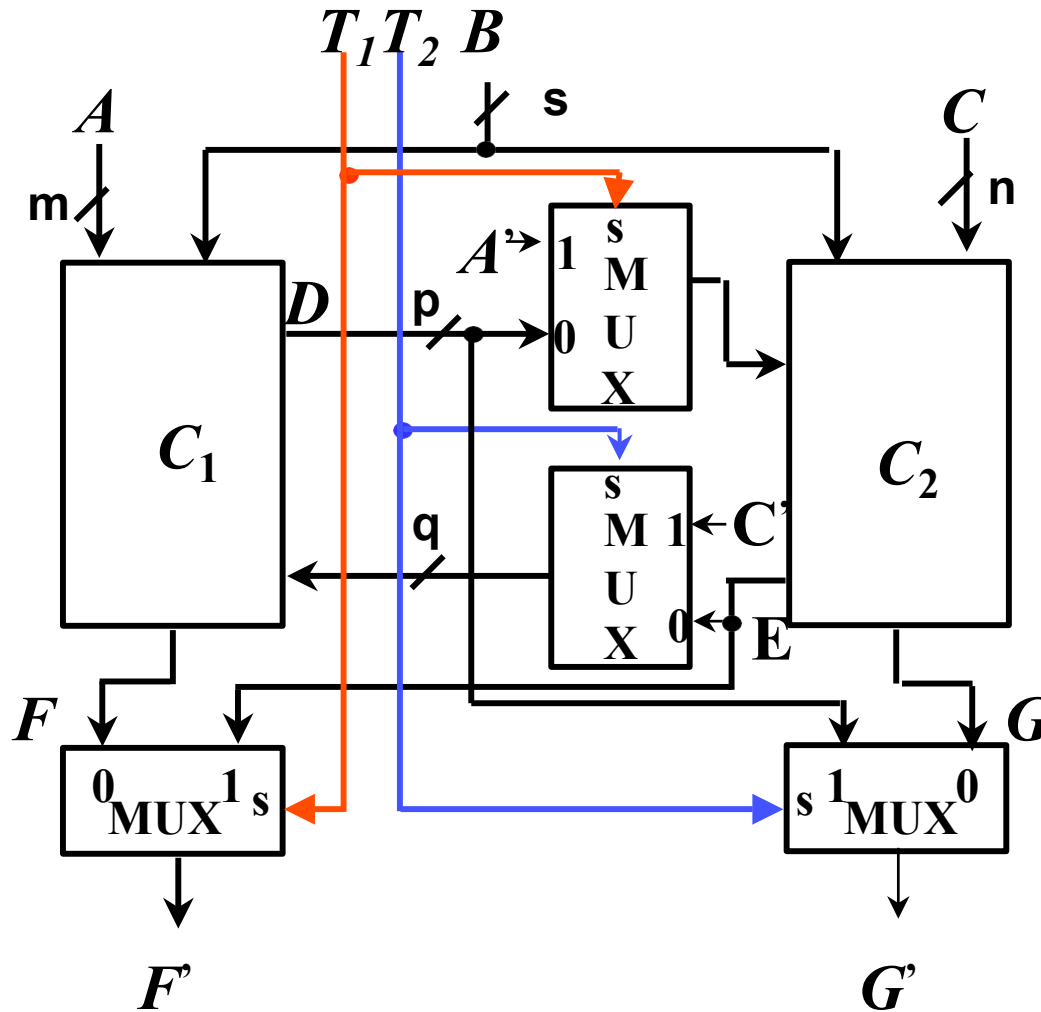

T_1	T_2	Mode
0	0	normal
0	1	test C_1
1	0	test C_2


If $2^{p+n} + 2^{q+m} < 2^{m+n}$ then test time can be reduced

Logic Redundancy

Rule: Avoid or eliminate redundancy ckt.


- **Design errors**
- **Undetectable faults**
- **Invalidation of some tests**
- **Bias fault coverage**

Example

 


Global Feedback Paths


Rule: break global feedback

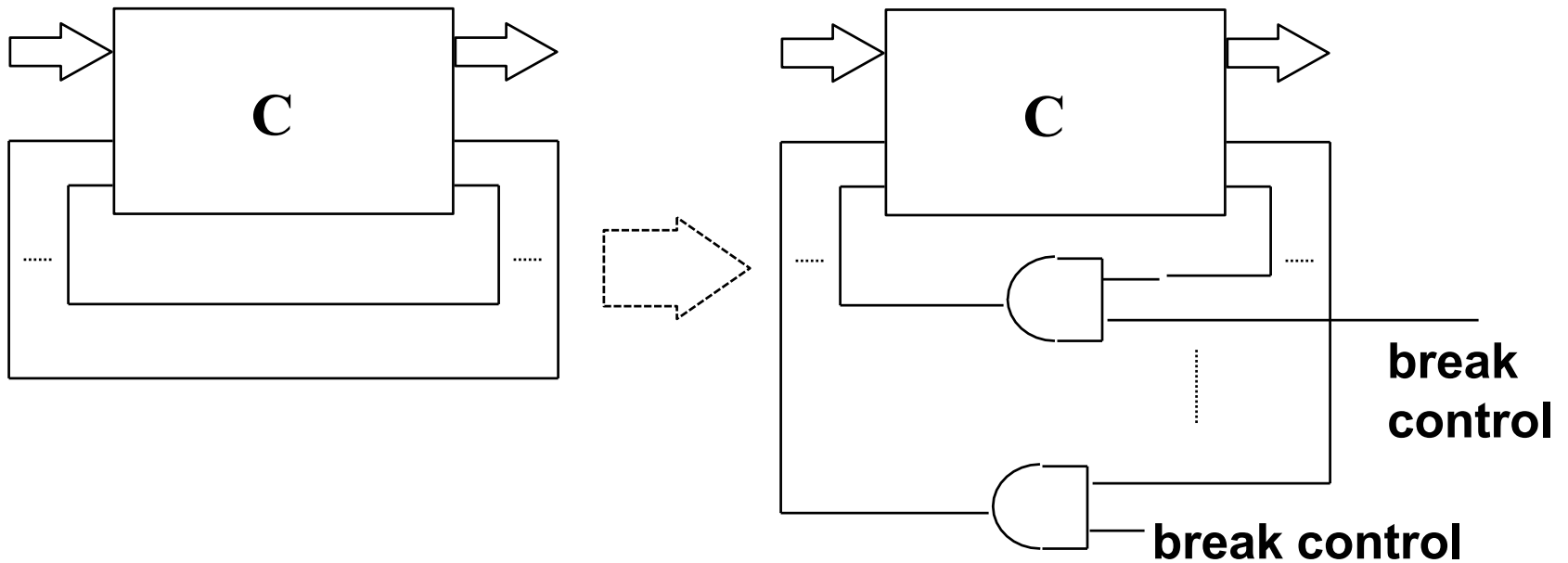

Scan System


 


Original design

 

SI
Modified circuit

Scan System

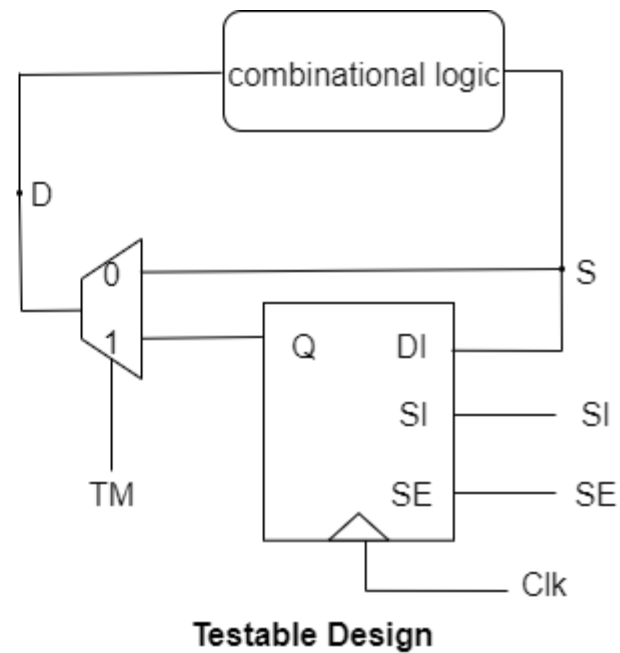 


Original design

Modified circuit

Scan System

- Long test time
- Large test data
- Too much overhead
- How to test DFT circuit itself

Scan Operation

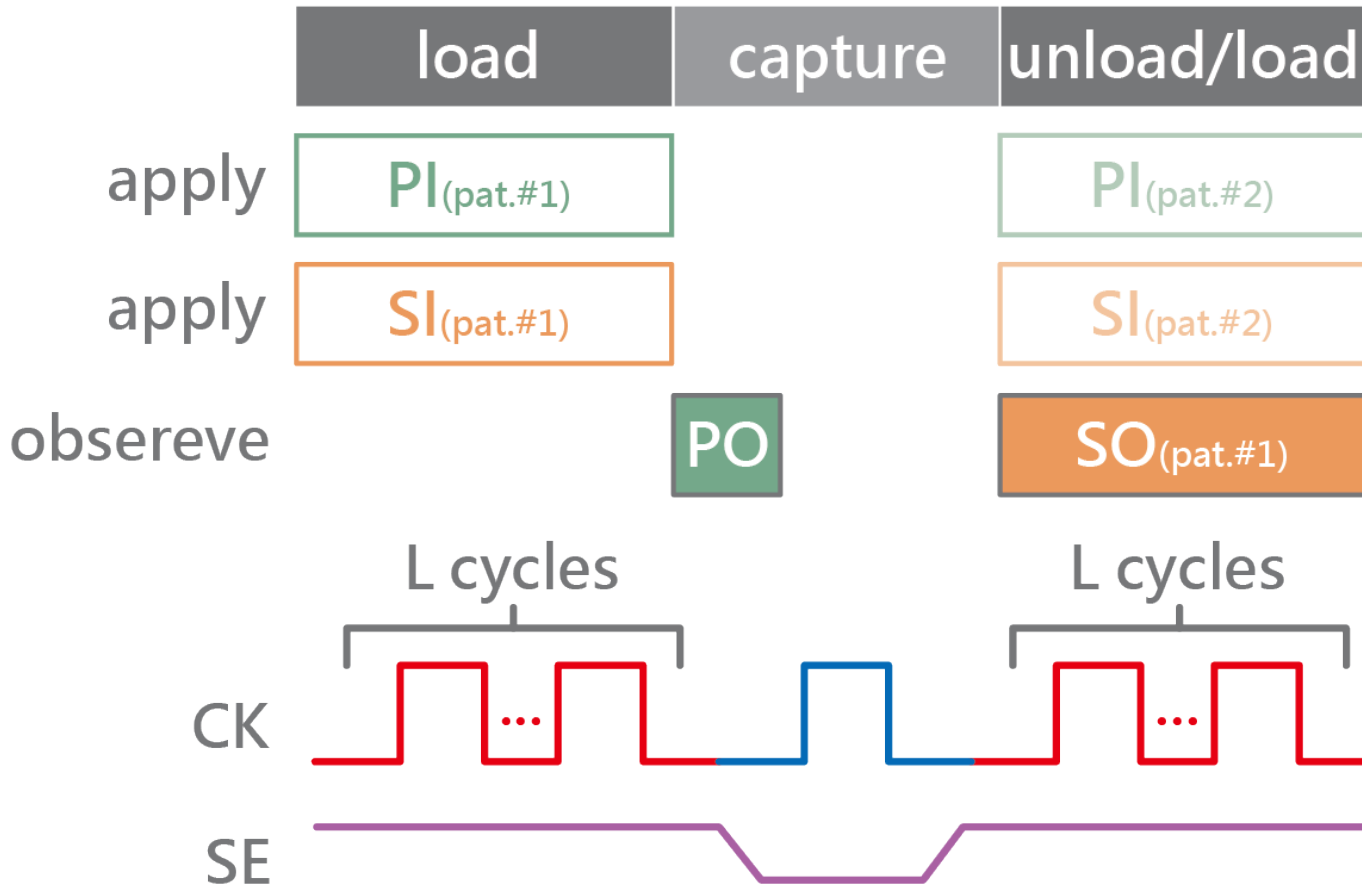


Scan System Performance



- How to calculate the test cycle:
 - L: Length of scan chain, N_{pattern}: Number of test patterns

$$\underbrace{(N_{\text{pattern}} + 1) \times L}_{\text{shift}} + \underbrace{N_{\text{pattern}}}_{\text{capture}}$$

 
- Example: Apply 5000 test patterns to a CUT with 10000 SFF
 - Total cycles = 50015000 cycles
(5000+1)x10000 shift cycles + 5000 capture cycles



Example

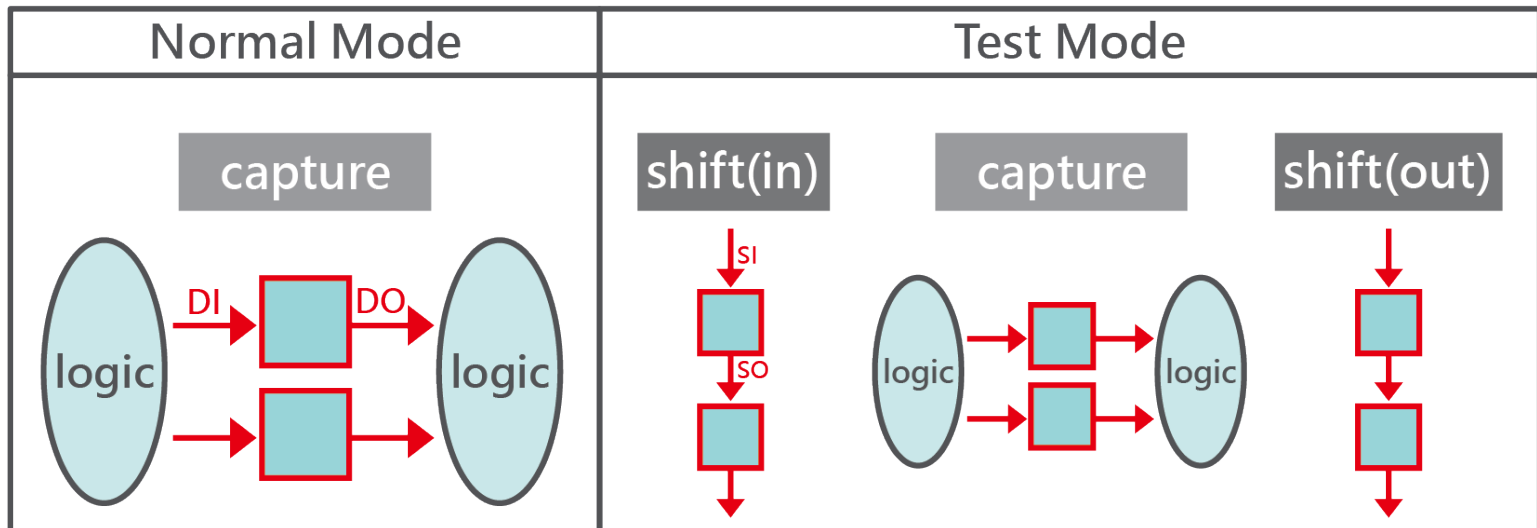 


Example

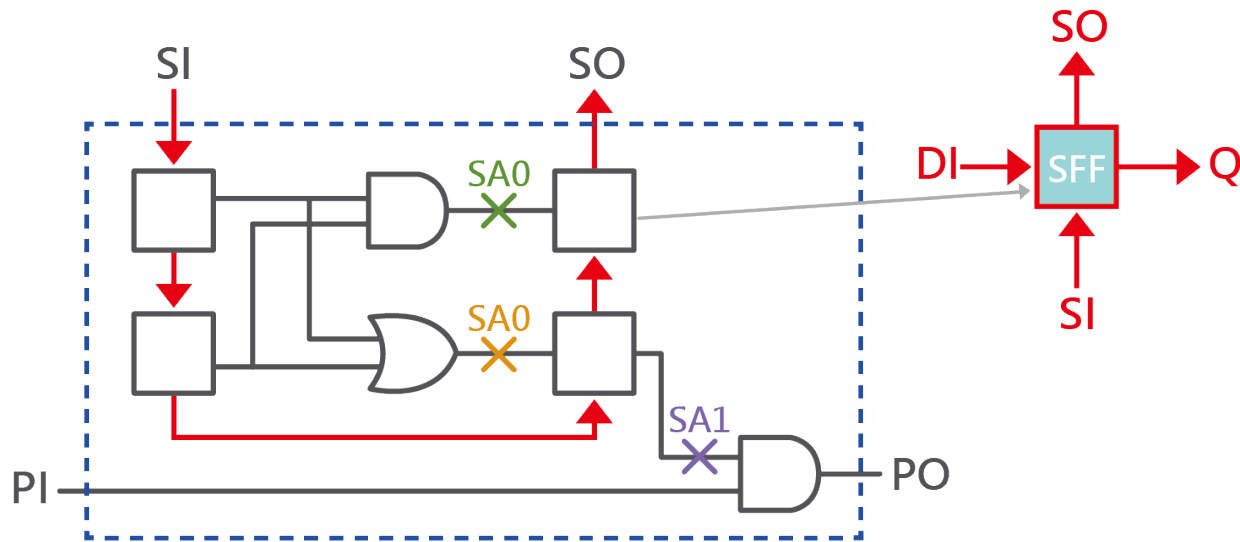


load		capture		unload
CK=PPPP		CK=P		CK=PPPP
SE=1111	SE 1→0	SE=0	SE 0→1	SE=1111
SI=X011				SO=HXX
PI=1	PO=L			

Scan DFT Overhead

 
- Performance Degradation
- Design overhead
- Hardware overhead
- Yield loss
- Power overhead



Example-Normal Mode

 


Example-Test Mode

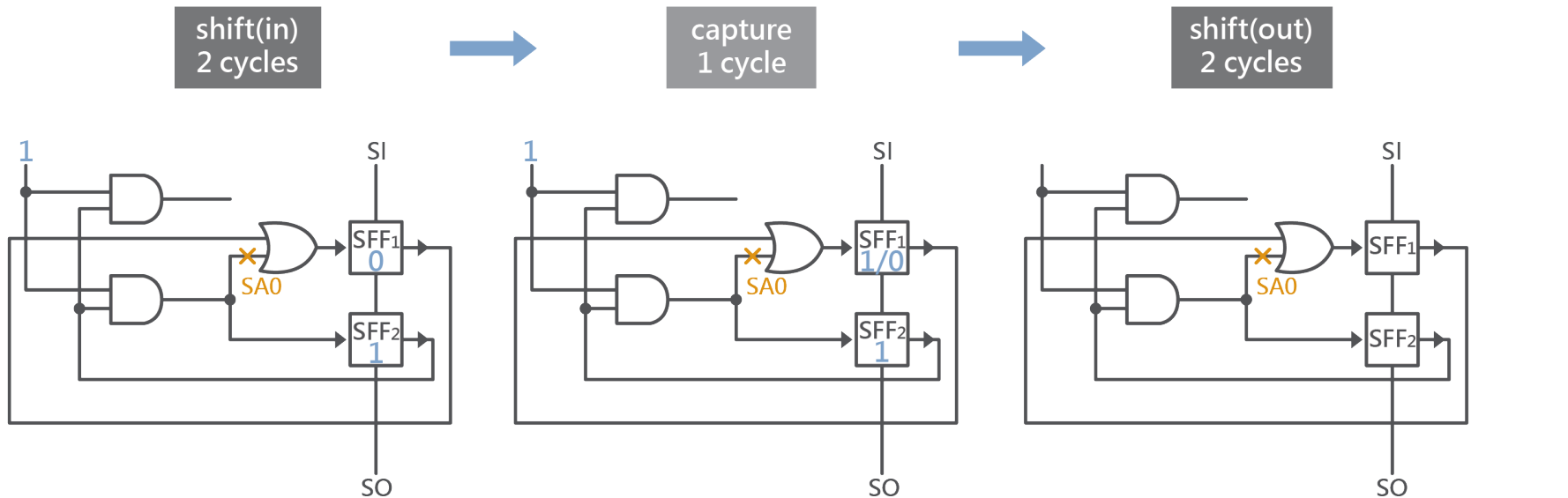


1/0 is observed at 2nd cycle

Full Serial Integrated Scan

 


CK
Normal

 


Scanned

Sequential ATPG → Combinational ATPG

Isolated Serial Scan (Scan/set)

 


Full Isolated Scan (Structured)

 



- Shadow register
- Real-time test support
- snapshot

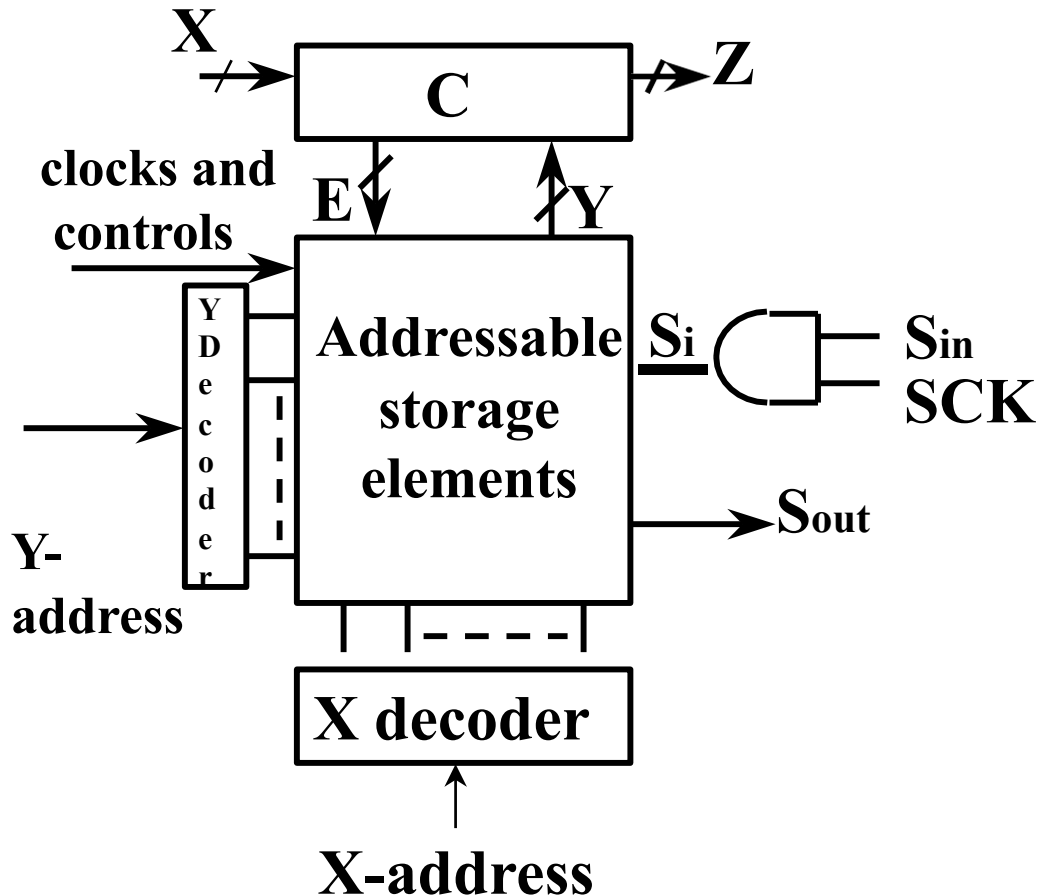Random-Access Scan (Non serial-structured)



- High area overhead
- Faster test application: only bit change
- Concept of crosscheck

  Random-Access Scan (Non serial-structured)



Scan Cell Design


- **Static / Dynamic**
- **Single / Double stages**
- **Latch / Flip-flop (Clocking Scheme)**

Usually Two Operation Modes

- **Functional mode**
- **Shift mode**

IBM LSSD Scan Cell

- **Gate Level**

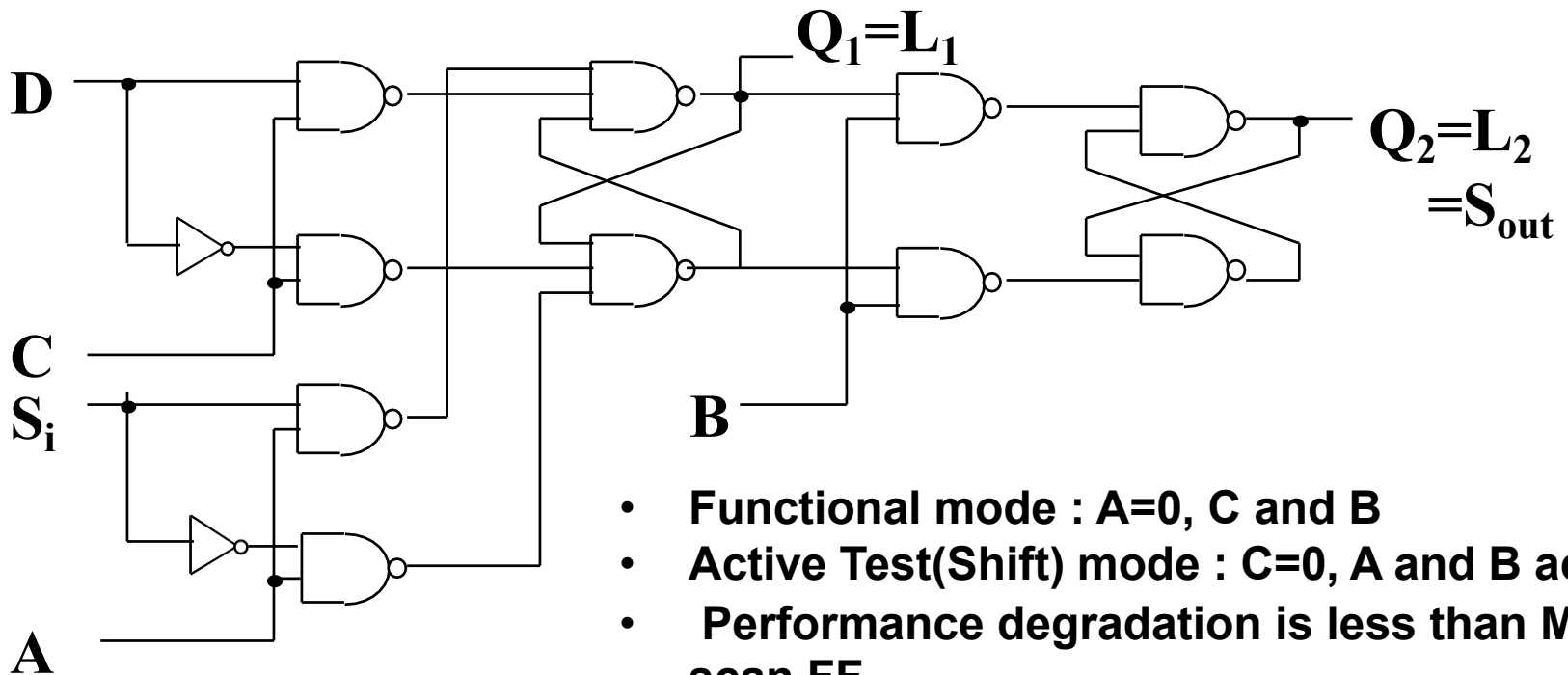

- **Functional mode** : **A=0**, **C** and **B**
- **Active Test(Shift) mode** : **C=0**, **A** and **B** active
- **Performance degradation is less than Mux-scan FF**
- **Non-overlap clock scheme**

IBM LSSD Scan Cell

Advantages


- It allows us to insert scan into a latch-based design.
- LSSD is guaranteed to be race free, which not case for the Muxed-D and Clocked-scan design.

Disadvantages


- It requires routing for the additional clocks, which increases routing complexity.

IBM LSSD Scan Cell (Cont.)

- Switch / Inverter level

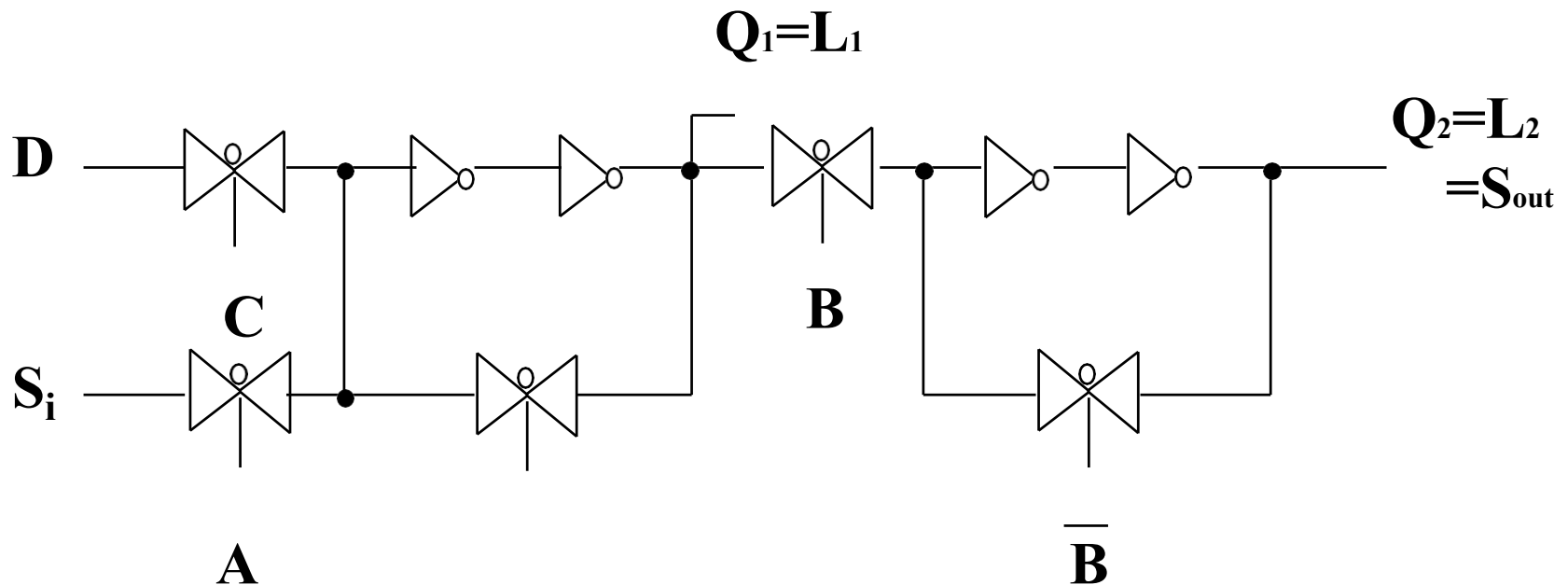


LSSD Double-Latch Design

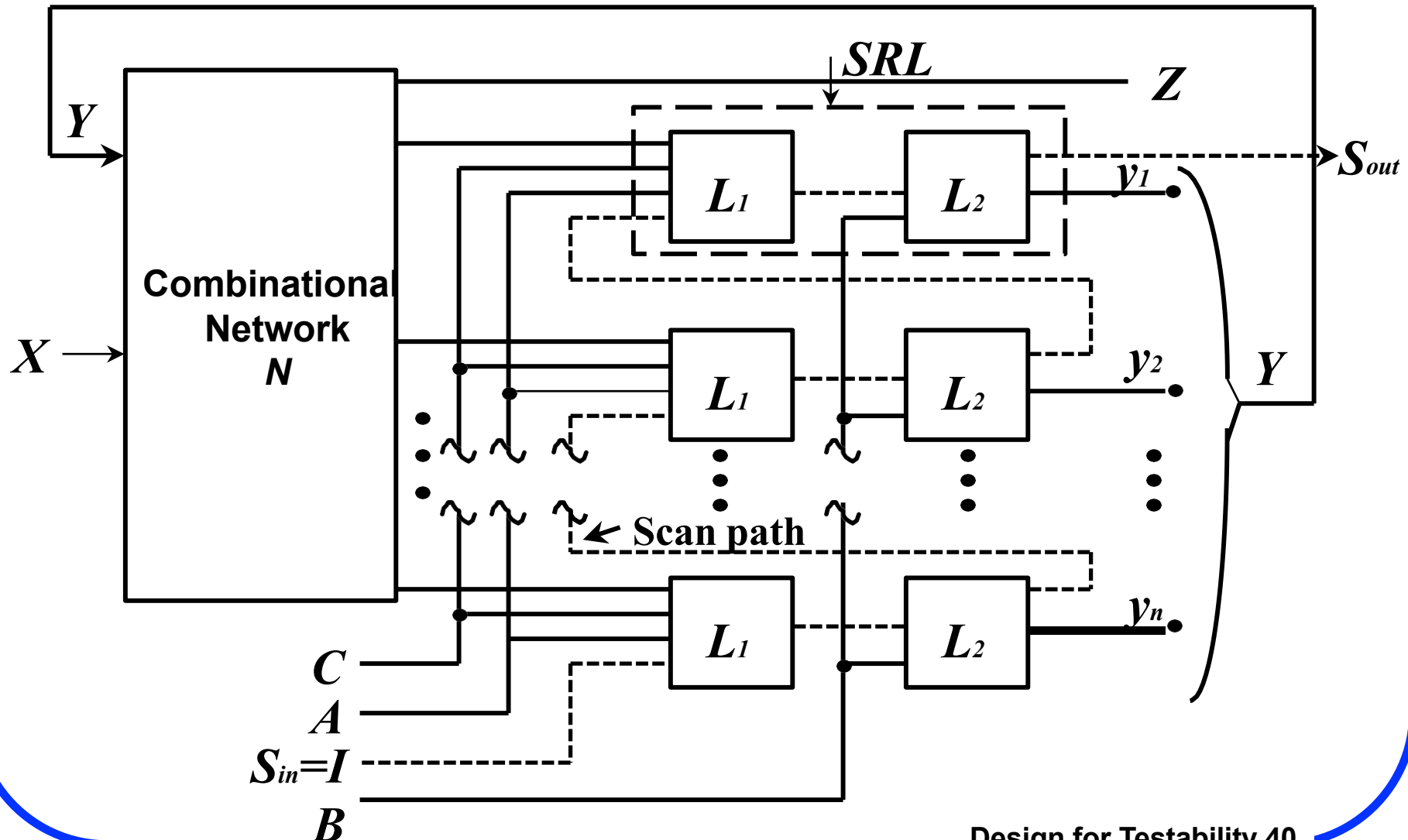


Clocking Scheme of LSSD Double-Latch


Normal mode:

 


Test mode:

 

LSSD Single-Latch Design

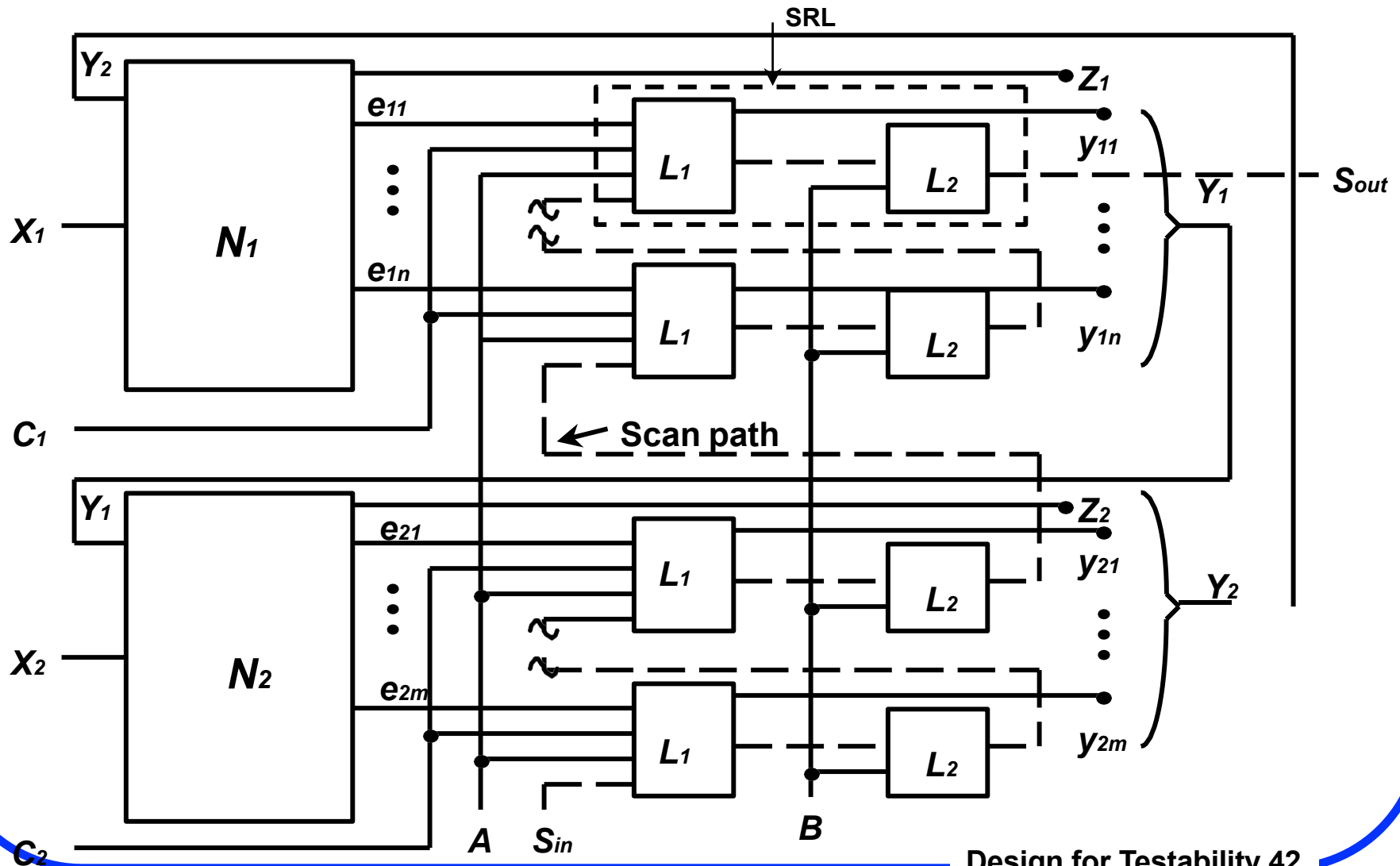


Example

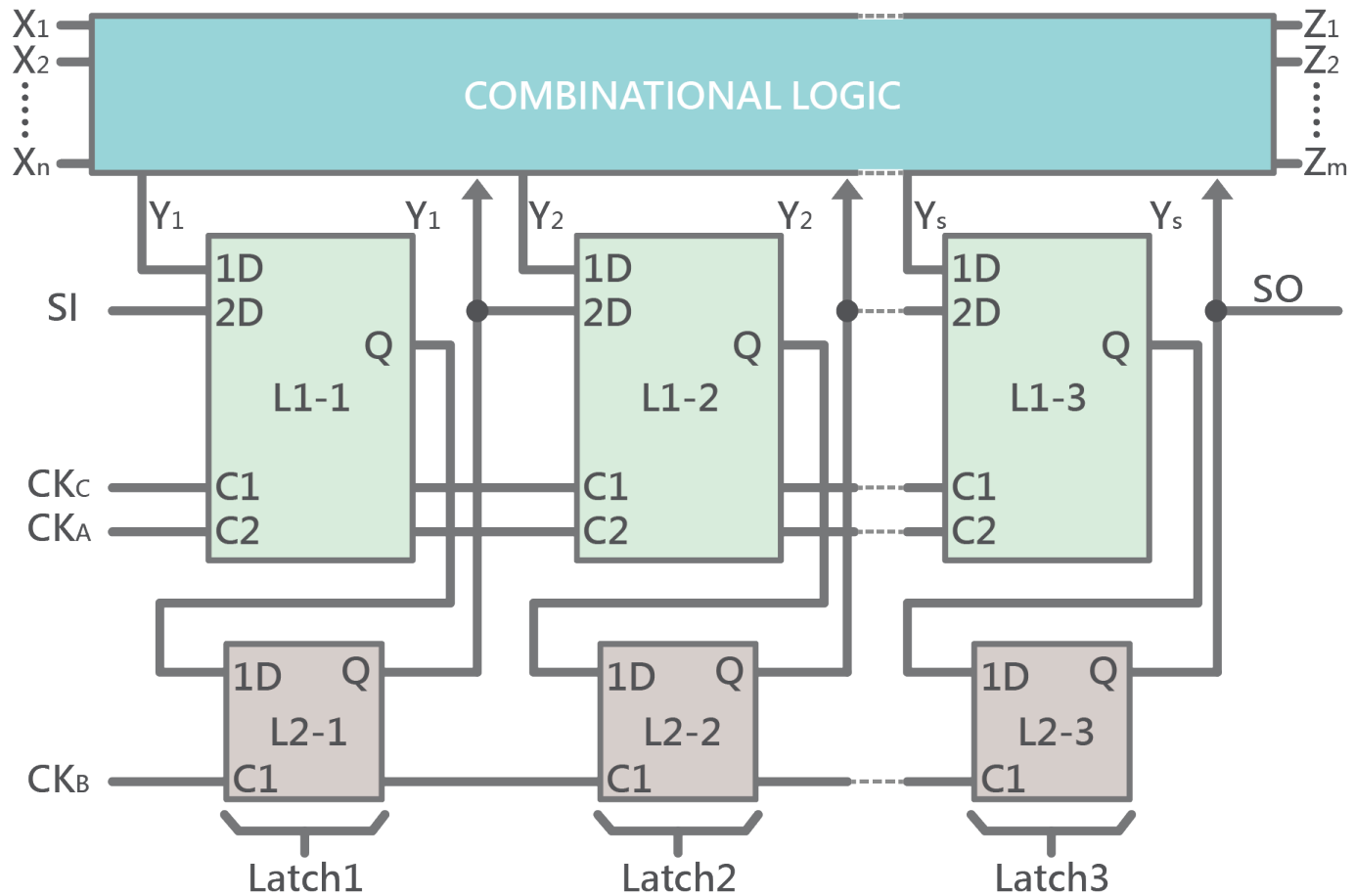

Scan Design Costs

- **Area overhead**
- **Possible performance degradation**
- **Extra pins**
- **High test time**
- **Extra clock control**

More Area OverHead

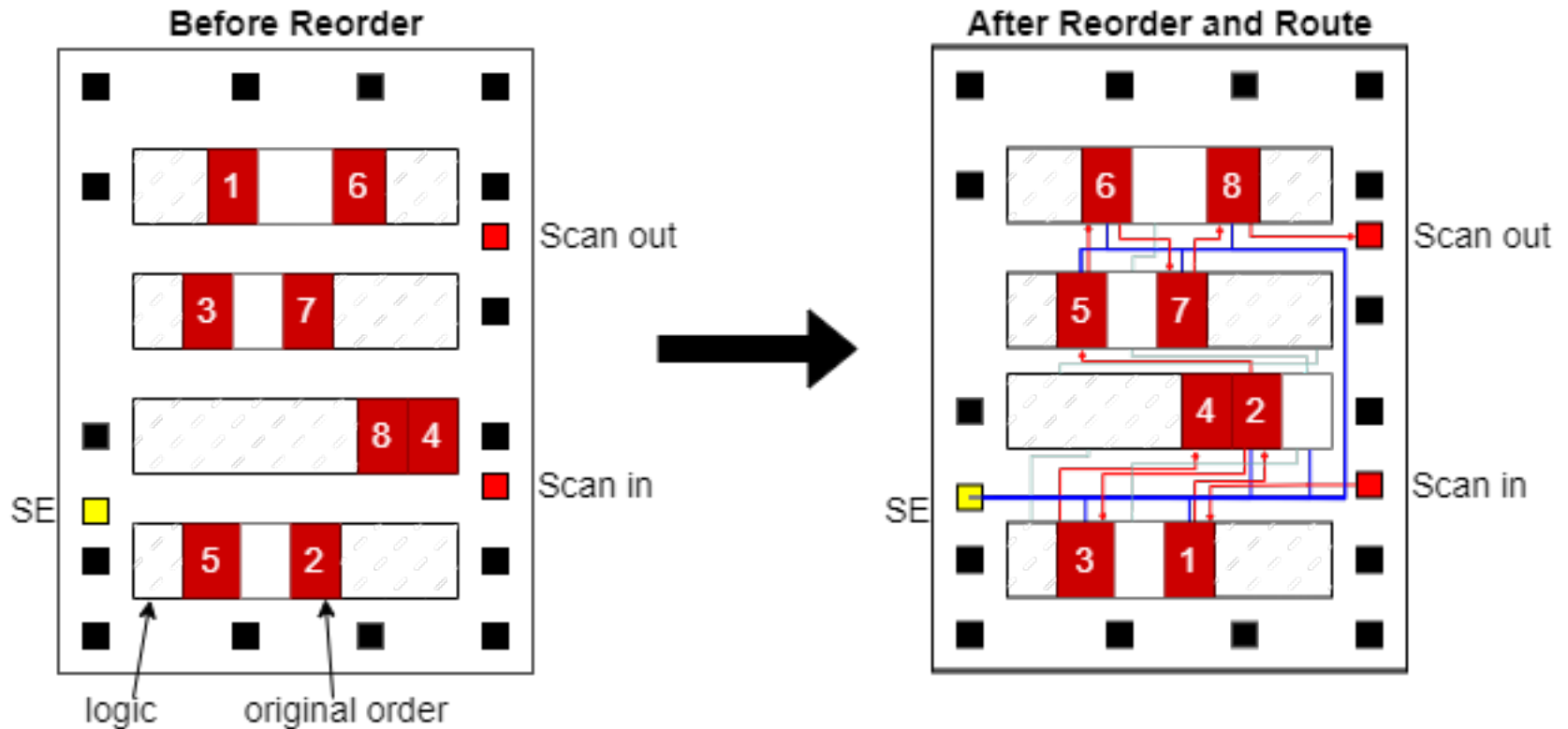


Advanced Scan Concepts

- Partial scan (P.S.)
- Multiple test session (M.T.S.)
- Multiple scan chains (M.S.C.)
- Broadcast scan chains (B.S.C.)

Method	P.S.	M.T.S.	M.S.C.	B.S.C.
Area overhead	↓	same	same or ↑	same
Performance Degradation	↓	same	same	same
Extra pins	same	same	same or ↑	↓
Extra clock control	same	same	same	same
Test application time	↓ or ↑	↓	↓	↓

 Partial Scan: Only a subset of all flip-flops are scanned




- Trade-off between
 - Area overhead
 - Test generation complexity


Partial Scan and Full Scan

- **Full scan**
 - Every flip-flop is scanable
 - More hardware overhead
 - Higher fault coverage
 - Longer test time
 - Shorter ATPG time required
- **Partial scan**
 - Not every flip-flop is scanable
 - Less hardware overhead
 - Less fault coverage
 - Shorter test time
 - Longer ATPG time required


Scan Design Flow

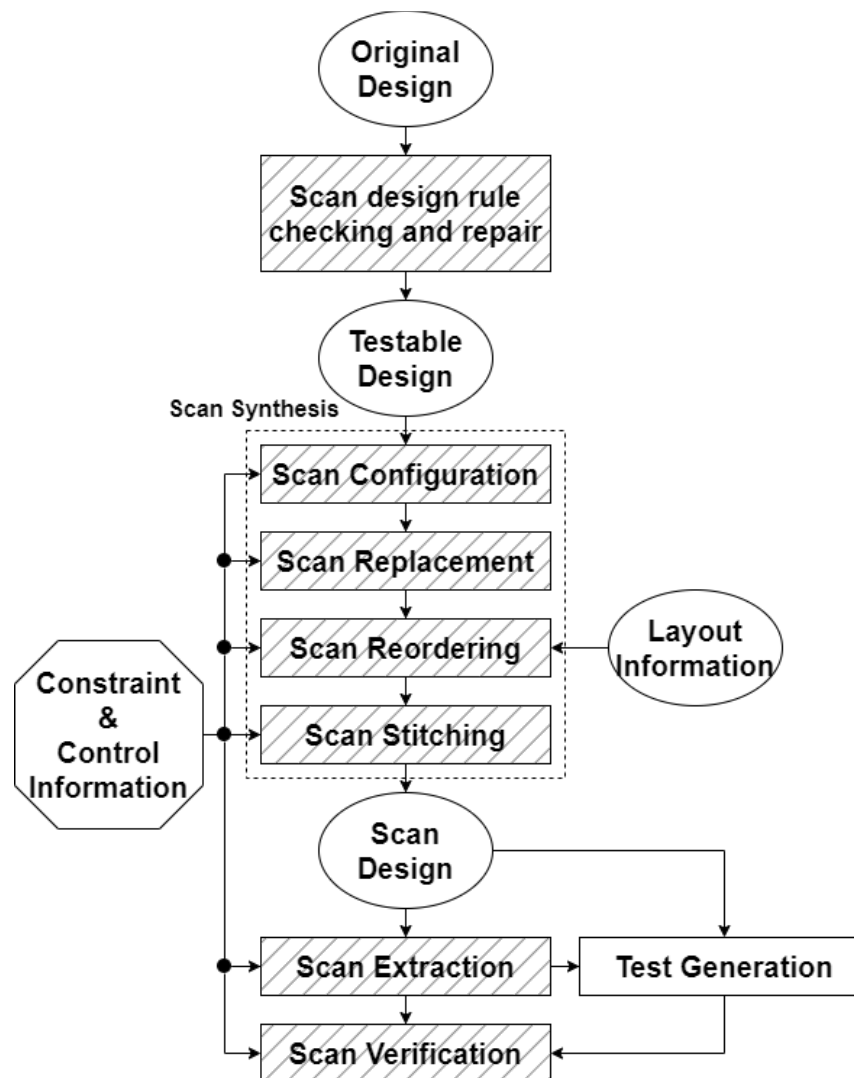



Scan Register Selection

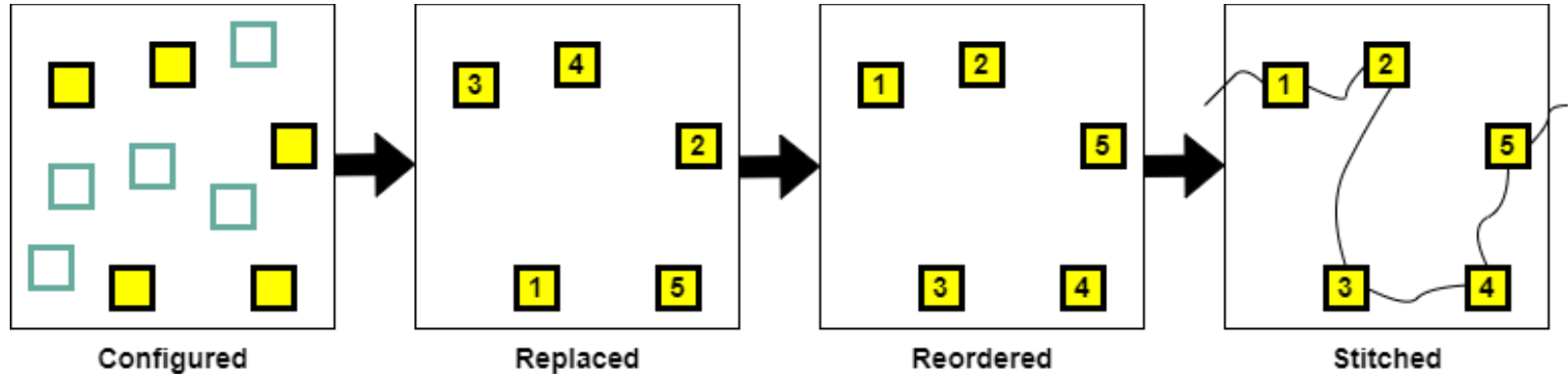


Clock Skew Between Two Clock Domains

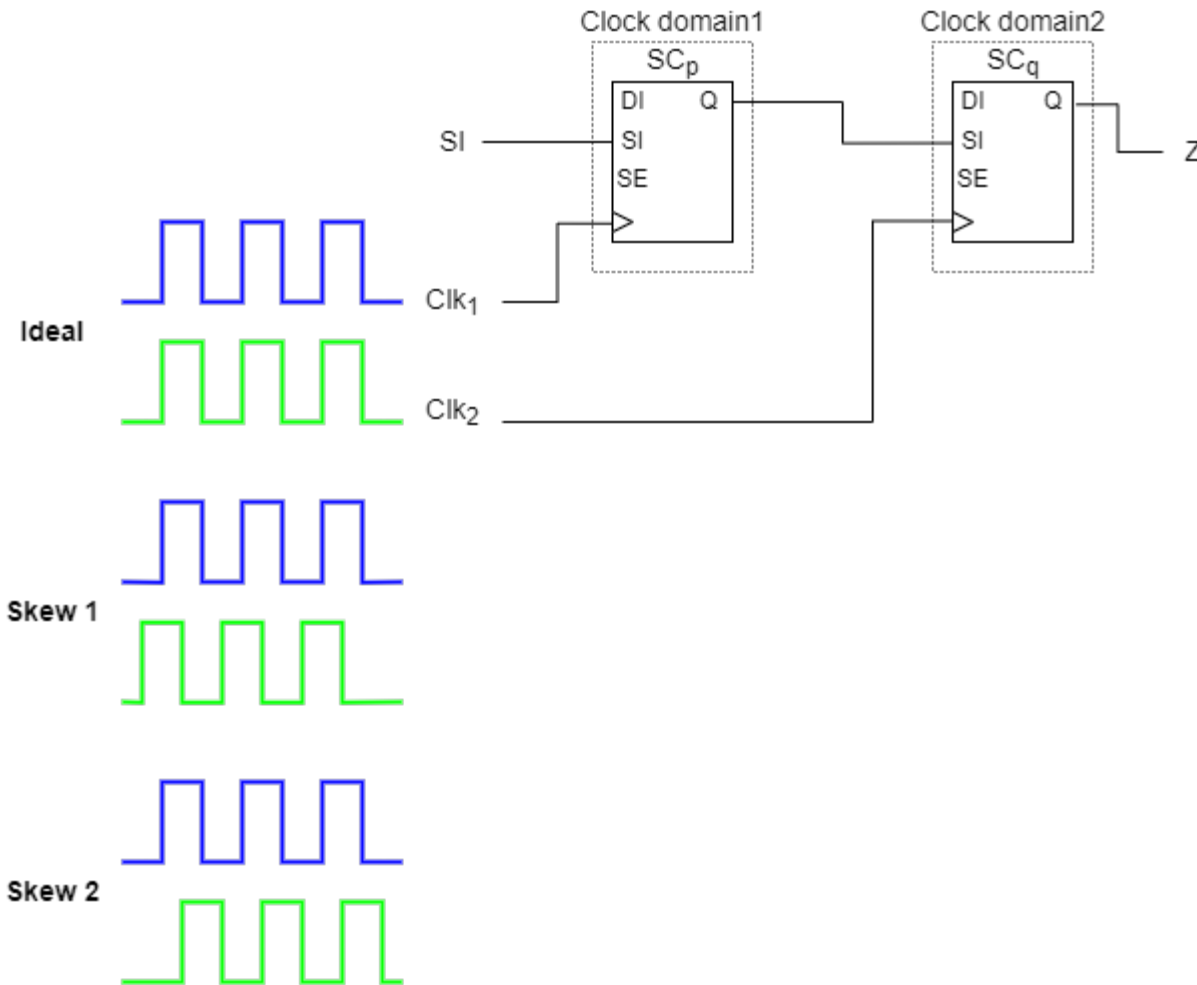

Lock-up Latch

 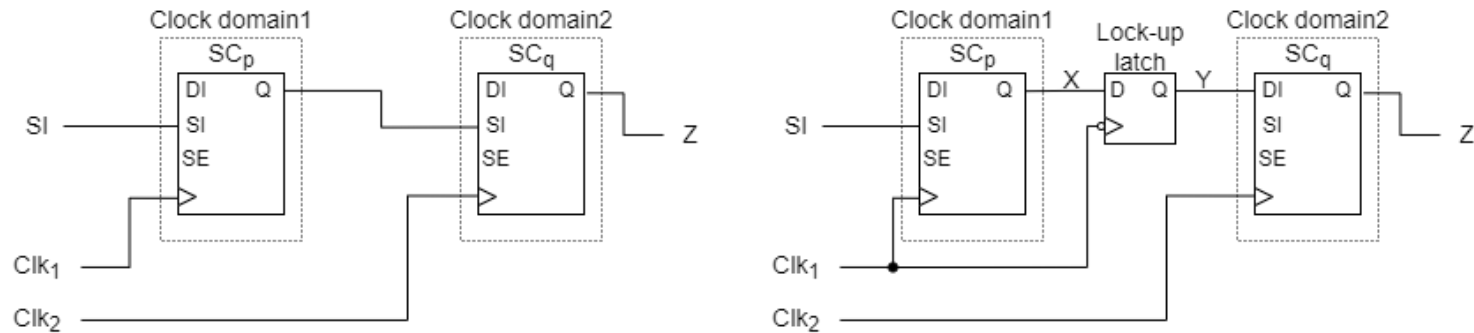


Clock Group

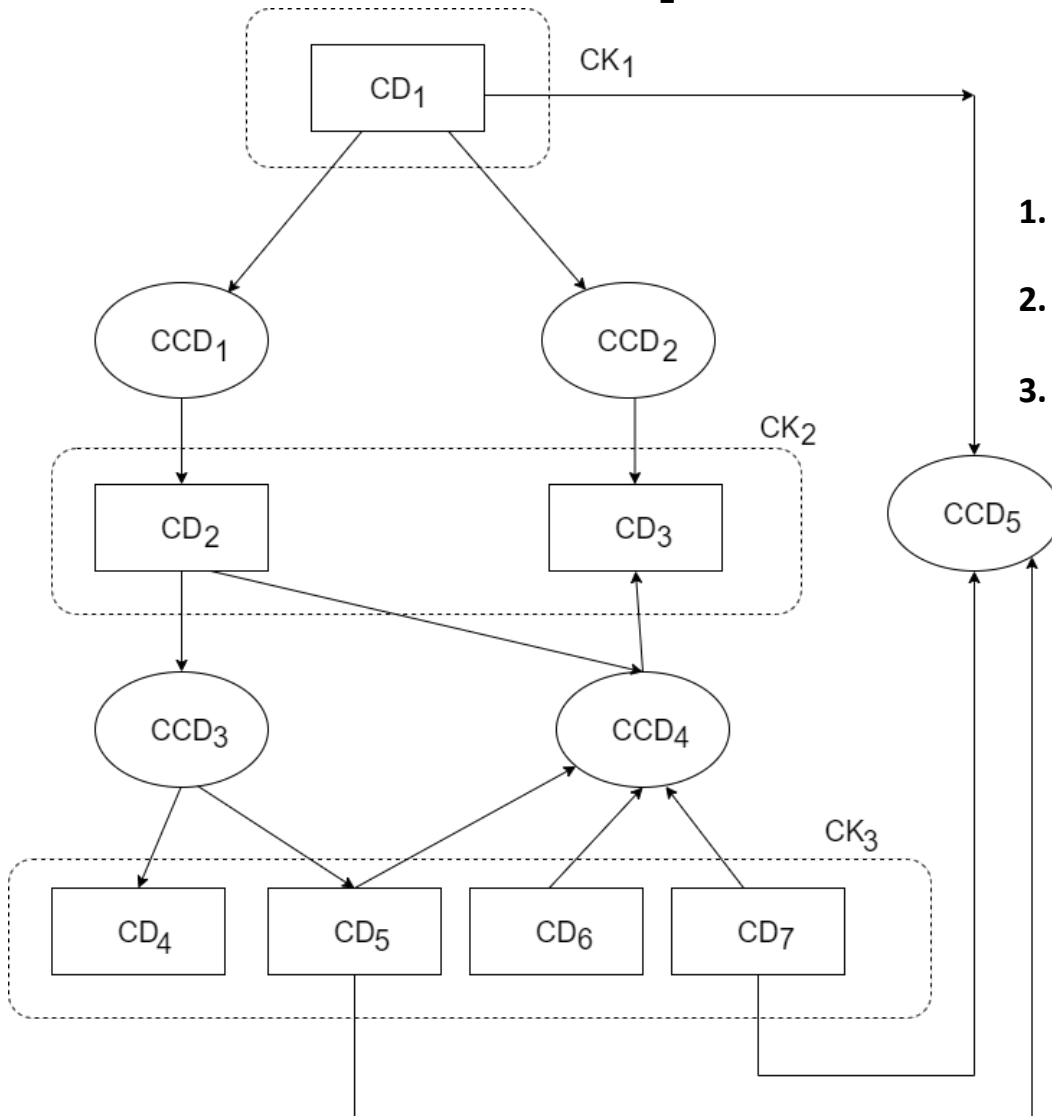


1. If there is clock skew between CD₁ and CD₂, then CD₁ and CD₂ can not form a scan chain.
2. CD₂ and CD₃ can form a scan chain if there is no interaction among them.
3. Three clock group required in this design

CD: Clock Domain
 CCD: Cross Clock Domain
 CK: Clock Group

Reorder and Route

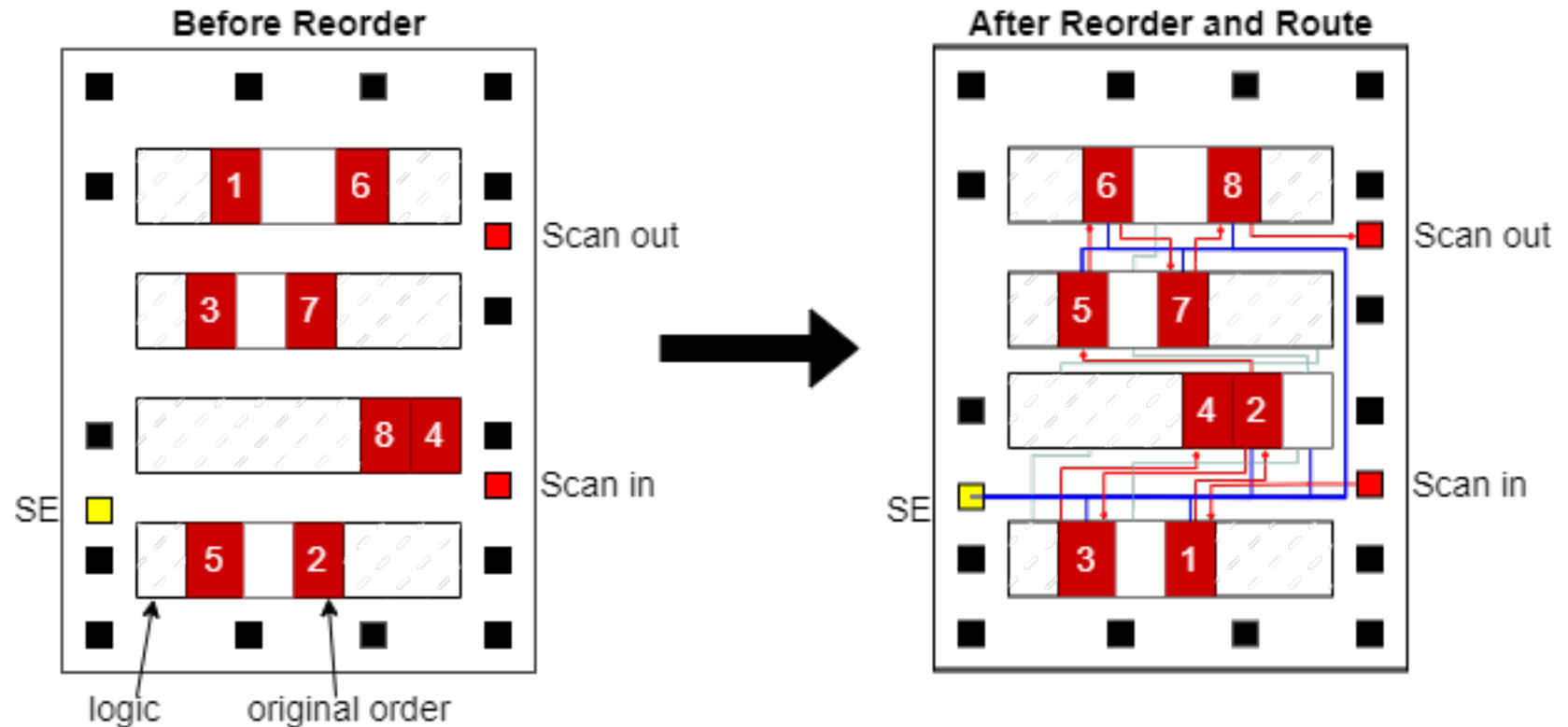


Negative/Positive edge

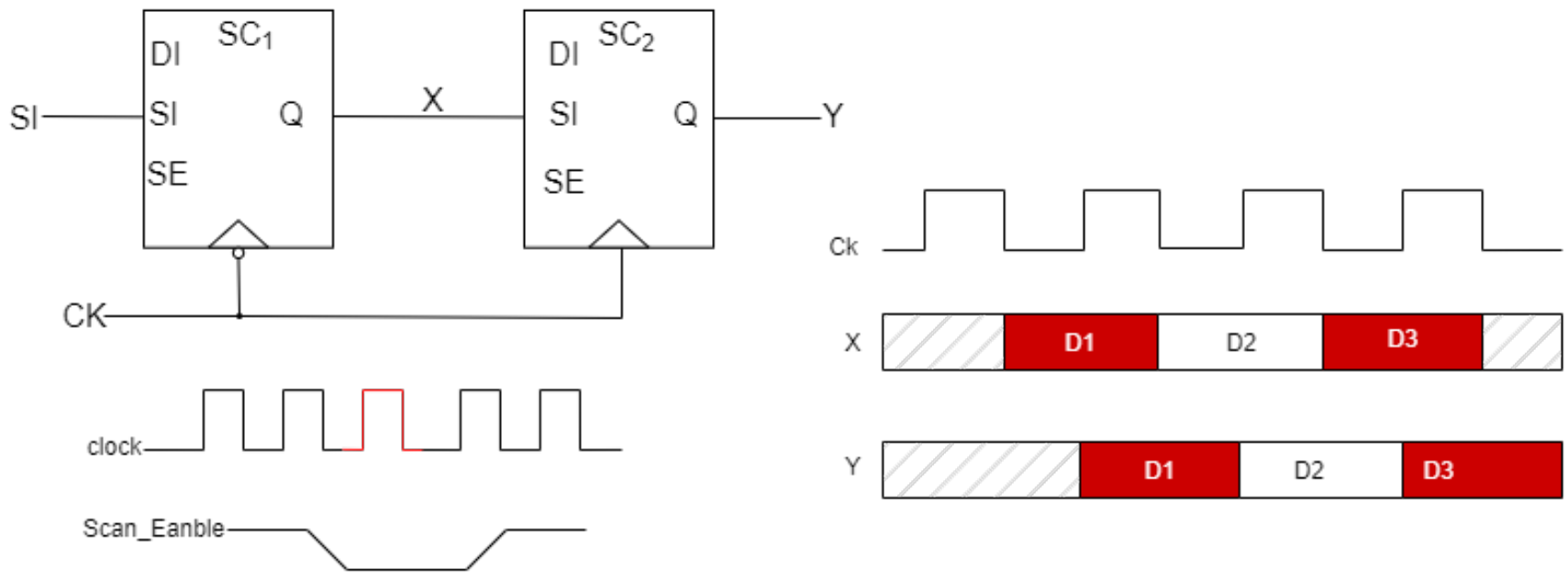

Scan Chain Integrity Test

 
- Scan chain requires to test itself
- Sequence 00110011...is shifted in and shifted out
- There is no capture operation
- Each scan FF undergo four transitions $0 \rightarrow 0$, $0 \rightarrow 1$, $1 \rightarrow 0$, $1 \rightarrow 1$
- Detect all stuck-at faults and transition faults in the scan chain




$$\underbrace{(N_{\text{pattern}} + 1) \times L}_{\text{shift}} + \underbrace{N_{\text{pattern}}}_{\text{capture}} + \underbrace{2L}_{\text{scan integrity}}$$

Scan Chain Flush Test

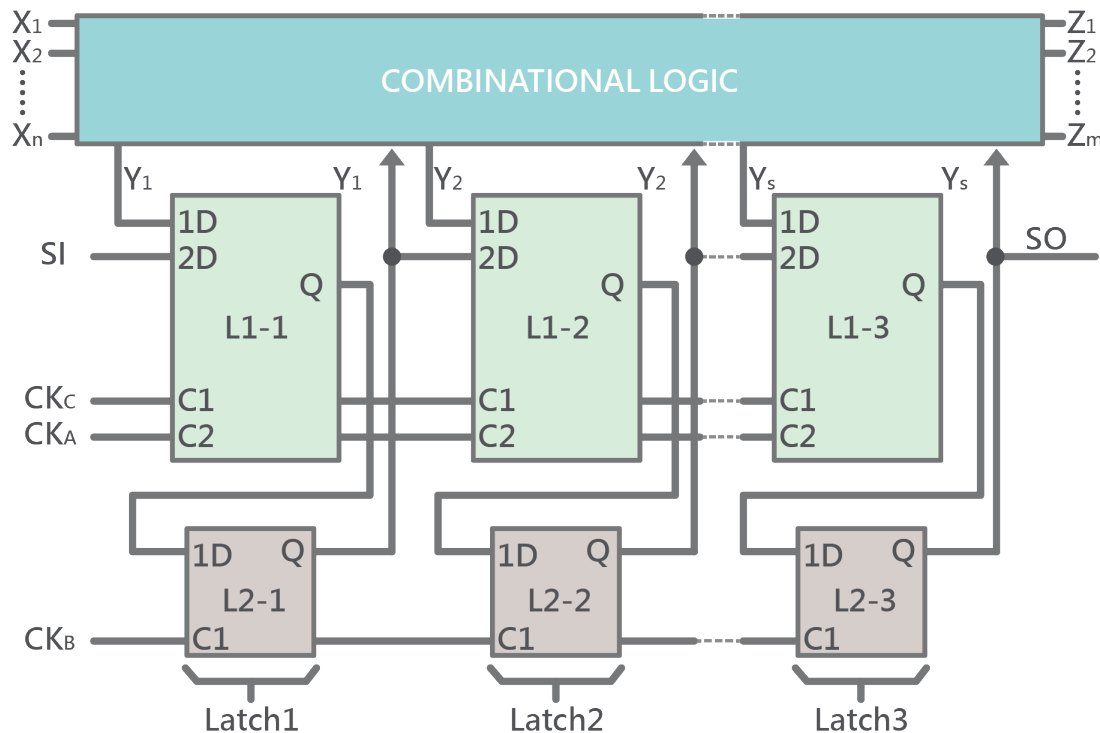
- LSSD Scan chain requires to test itself
- Apply $CK=0$, $CA=1$ and $CB=1$ to form the path from SI to SO
 - Apply $SI=0 \rightarrow 1$ at SI
 - Measure delay time form SI to SO



Scan Chain Low Power

 


(a)

 


(b)

Scan Chain Low Power

 


(a)

 

(b)

Example


Fig.1

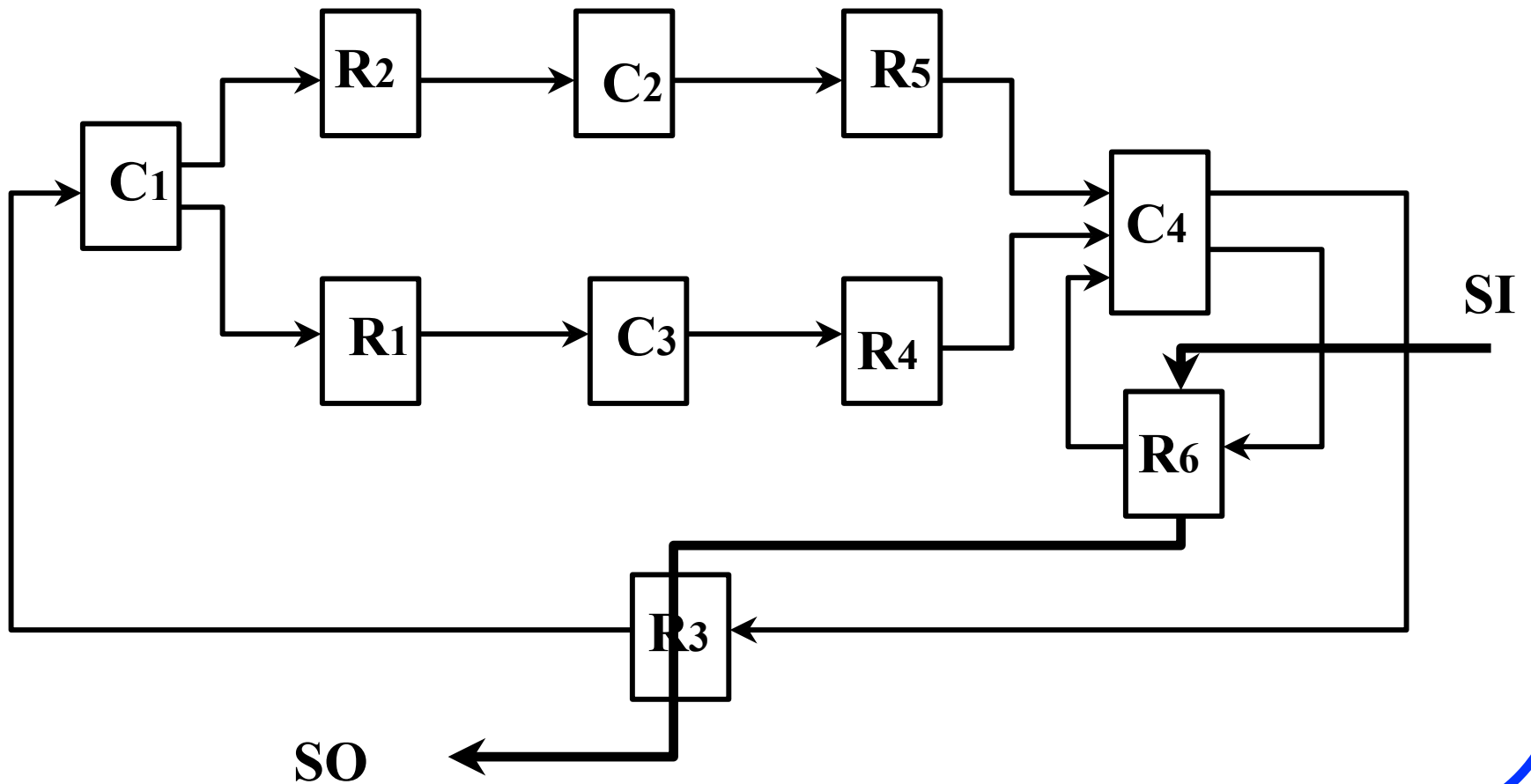

Example (Cont.)

- **Test procedure:**
 - **Scan in a test pattern to R3 and R6 .**
 - **Hold test pattern in R3, R6 for two clock cycles such that test response appears in R5 and R4.**
 - **Load data (from R5, R4) to R6, R3 and shift out**


Eliminate on HOLD mode of Scan Registers

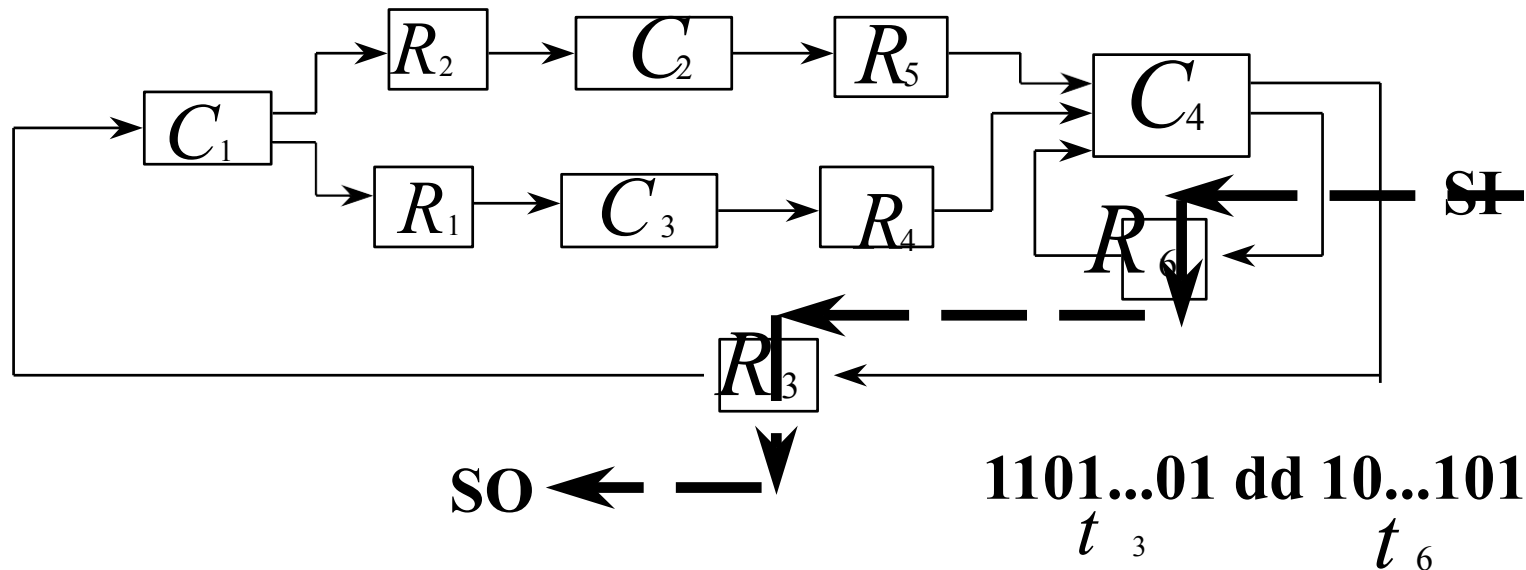


- By adding two dummy bits between the patterns to be scanned to R_3 and R_6 , the HOLD mode can be eliminated

Multiple Test Session

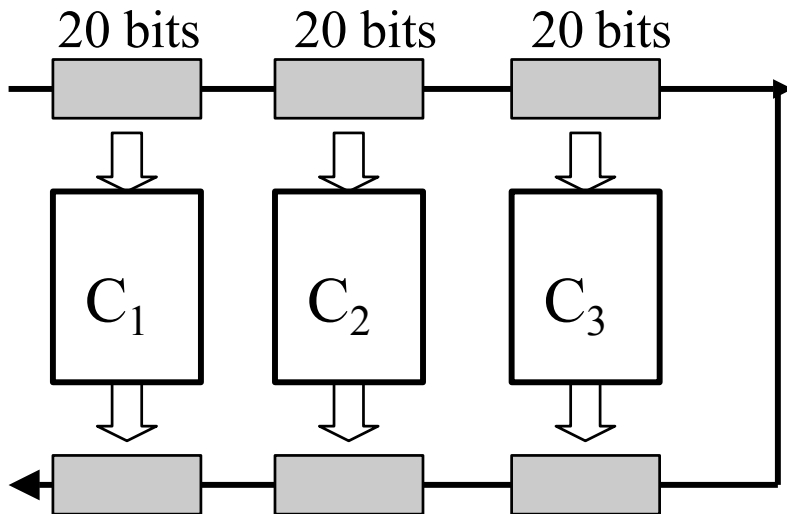- # patterns: C_1 :100, C_2 : 200 and C_3 : 300





Test Time
= 60 * 300
= 18,000 (cycles)

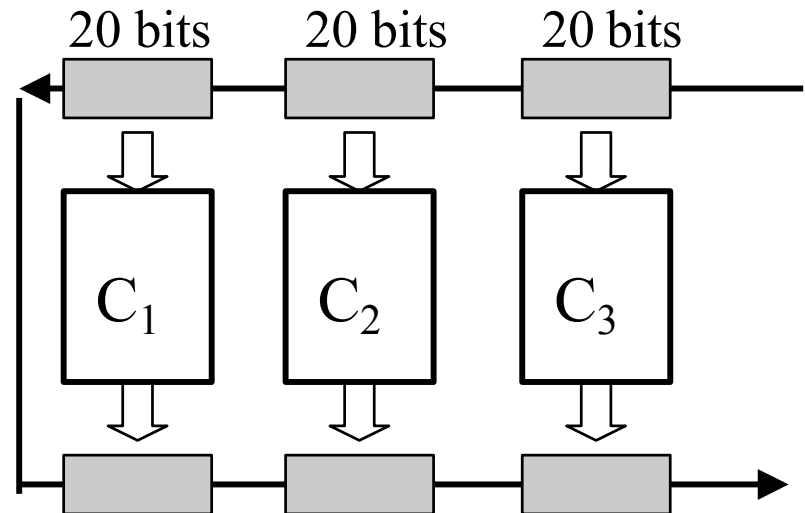

Test Time
= 60 * 100 + 40 * 100 + 20 * 100
= 12,000 (cycles)


Multiple Scan Chains

  

- Reduce test application time
- Usually test I/O will share the normal I/O

Broadcast Scan Chains- General Hardware Architecture

 - Using a single data input to support multiple scan chains




Multiple Scan Chain

Example : 10k SSF partitioned into three scan chains

- $L = \text{Max}\{3K, 3K, 4K\} = 4K$
- More I/O pin required
- 60% reduction in test time


Single scan chain

$n=1, N_{\text{SFF}}=10K, L=10K$

 

Three scan chains


$n=3, N_{\text{SFF}}=1K, L=4K$

 


Virtual Circuits

- The inputs of CUTs are connected in a 1-to-1 manner.

Example :

 

(a) i-to-i connection

 

(b) random connection

- ➔ The whole virtual circuit is considered as one circuit during ATPG.
- ➔ The resulting test patterns can be shared by all CUTs.